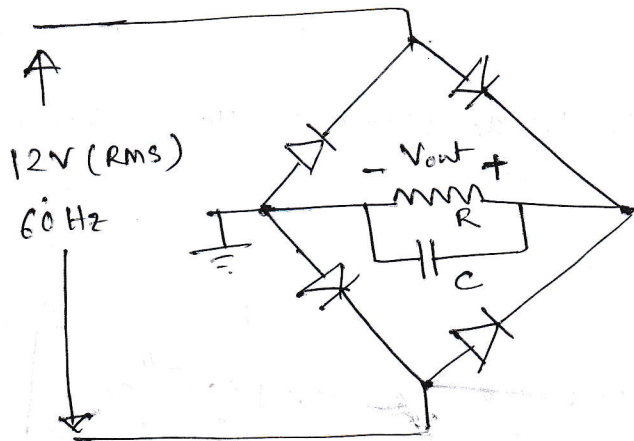


Q.1



$$V_\gamma = 0.7 \text{ V.}$$

$$\text{input} = 12 \text{ V (RMS)} = V_i$$

$$f_{\text{avg}} = 60 \text{ Hz.}$$

$$R = 100 \Omega$$

$$\text{Ripple voltage (P-P)} = 1 \text{ V.} = V_r$$


$$\text{peak i/p voltage, } V_i(\text{max}) = 12\sqrt{2} \text{ V.}$$

$$V_{\text{out-peak}} = 12\sqrt{2} - 2V_\gamma = (12\sqrt{2} - 1.4) \text{ V.} = V_m$$

$$V_r = \frac{V_m}{2fRC}$$

$$C = \frac{V_m}{2fR V_r} = \frac{12\sqrt{2} - 1.4}{2 \times 60 \times 100 \times 1} = 1.2975 \times 10^{-3} \text{ F} = 1297 \text{ } \mu\text{F} \quad (a)$$
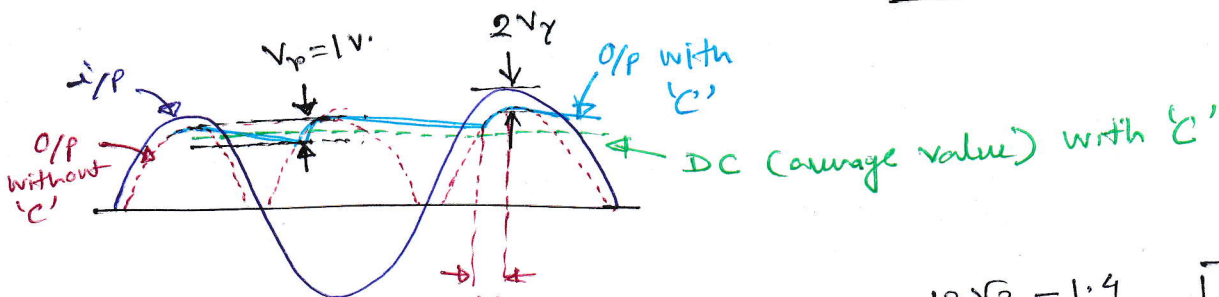
$$\text{DC at output (average)} = \left(V_m - \frac{1}{2} V_r \right) = 12\sqrt{2} - 1.4 - \frac{1}{2} \times 1 = 15.07 \text{ V.} \quad (b)$$



$$\text{Max. current through 'R'} = \frac{V_m}{R} = \frac{12\sqrt{2} - 1.4}{100} = 0.155 \text{ A.} \quad (c)$$

$$\text{PIV} = V_i(\text{max}) - V_\gamma = (12\sqrt{2} - 0.7) \text{ V} = 16.27 \text{ V} \quad (d)$$

In the previous page, Δt is time duration during which diode conducts.

$$\Delta t = \frac{1}{2\pi f} \sqrt{\frac{2V_p}{V_m}} \quad ; \quad (\text{for details please see Neaman's book}).$$


$$= \frac{1}{2\pi \times 60} \sqrt{\frac{2 \times 1}{12\sqrt{2} - 1.4}}$$

$$\Delta t = 951 \mu s \quad \text{or} \quad 0.951 \text{ ms} \quad \text{or} \quad 9.51 \times 10^{-4} \text{ Sec.}$$

(e)

Q.2

3

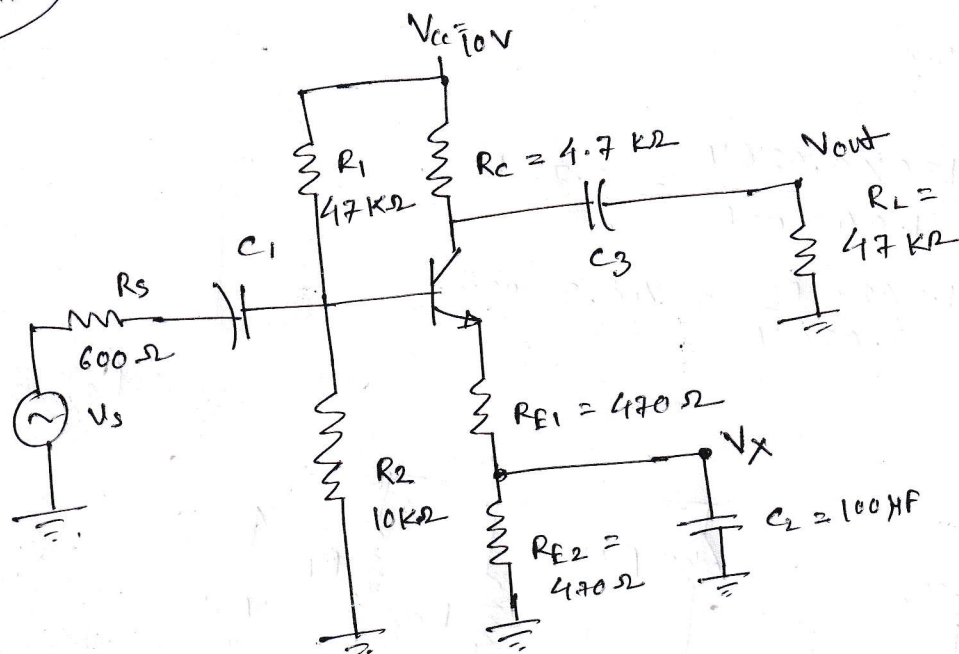

$$\beta = 150$$

Thevenin equivalent at the input,

$$R_{Th} = \frac{R_1 R_2}{R_1 + R_2} = \frac{(47\text{ k}\Omega)(10\text{ k}\Omega)}{(47 + 10)\text{ k}\Omega} = 8.245\text{ k}\Omega$$

$$V_{Th} = V_{CC} \cdot \frac{R_2}{R_1 + R_2} = 10 \times \frac{10\text{ k}\Omega}{(47 + 10)\text{ k}\Omega} = 1.75\text{ V}$$

$$I_B = \frac{V_{Th} - V_{BE(on)}}{R_{Th} + (1 + \beta)[R_{E1} + R_{E2}]} ; I_E = (1 + \beta)I_B$$

$$= \frac{1.75 - 0.7}{8.245 + (151)(0.470 + 0.470)} \text{ in k}\Omega$$


$$= 6.99 \text{ } \cancel{\mu\text{A}} \times 10^{-3} \text{ mA} = 6.99 \text{ } \mu\text{A}$$

$$I_E = (1 + \beta)I_B = (1 + 150) \times 6.99 \text{ } \mu\text{A} = \boxed{1.055 \text{ mA}} \quad (a)$$

$$I_C = \beta I_B = 150 \times 6.99 \text{ } \mu\text{A} = 1.048 \text{ mA}$$

$$V_C = V_{CC} - I_C R_C = 10 - 1.048 \text{ mA} \times 4.7\text{ k}\Omega$$
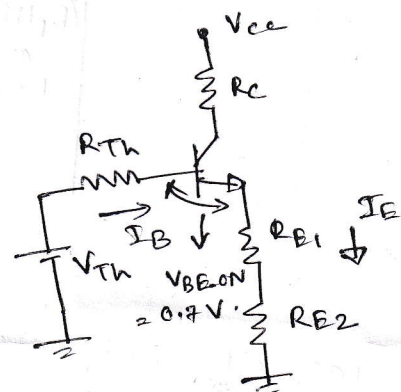
$$\boxed{V_C = 5.074 \text{ V}} \quad (a)$$




DC equivalent circuit.

AC analysis

Small signal parameters:

$$r_{\pi} = \frac{\beta V_T}{I_C} = \frac{150 \times 0.026 \text{ V}}{1.048 \text{ mA}} = 3.72 \text{ k}\Omega$$
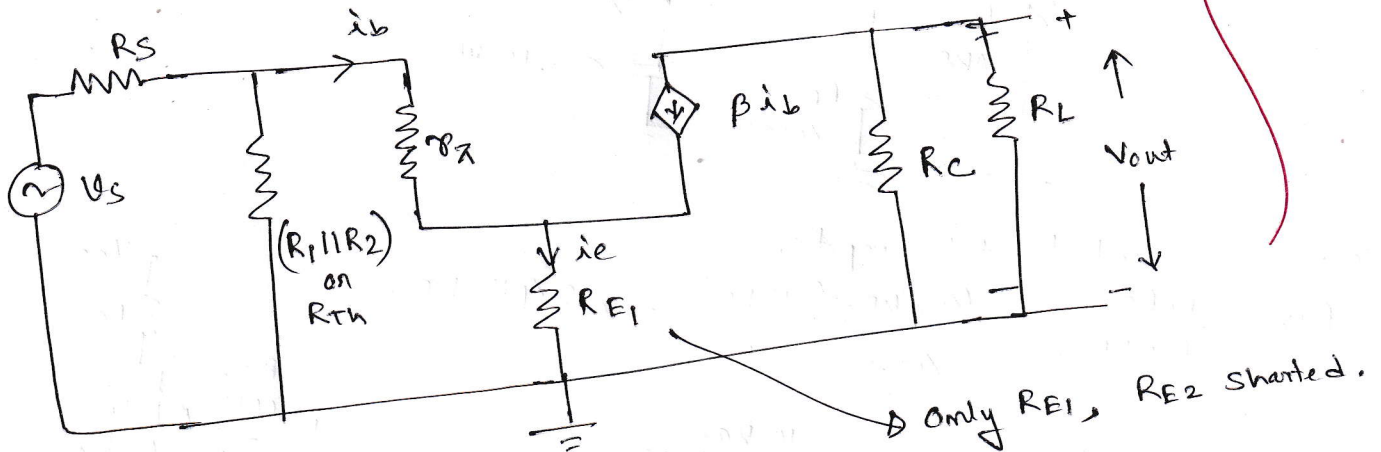
$$g_m = \frac{I_C}{V_T} = \frac{1.048 \text{ mA}}{0.026 \text{ V}} = 40.3 \text{ mS}$$




For CE Amplifier with emitter resistor,

$$\text{Small-signal voltage gain} = - \frac{R_C \parallel R_L}{R_{E1}} = - \frac{4.7 \text{ k}\Omega \parallel 47 \text{ k}\Omega}{0.47 \text{ k}\Omega} = - \frac{4.27}{0.470}$$

$$\text{Voltage gain} = -9.09$$

(c)

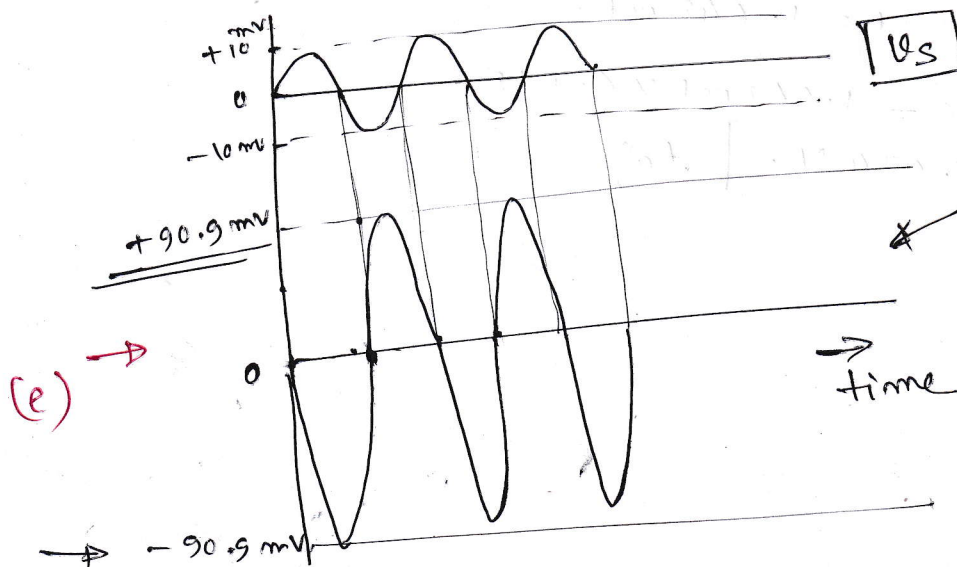(d) If C_2 is reduced to 10 nF , then for AC analysis C_2 can't be considered an short, we have to consider the impedance offered by C_2 , hence effective R_E increases. Gain reduces.
 Input (V_s) = 10 mV (peak)
 output (V_{out}) = $-10 \text{ mV} \times 9.09 = -90.9 \text{ mV}$; C_3 blocks the DC part.



Not in Scale

At, V_X only DC bias.

$$V_X = I_E \times R_{E2}$$


$$= 0.495 \text{ V}$$

(f)

Q.3

5

DC equivalent ckt:

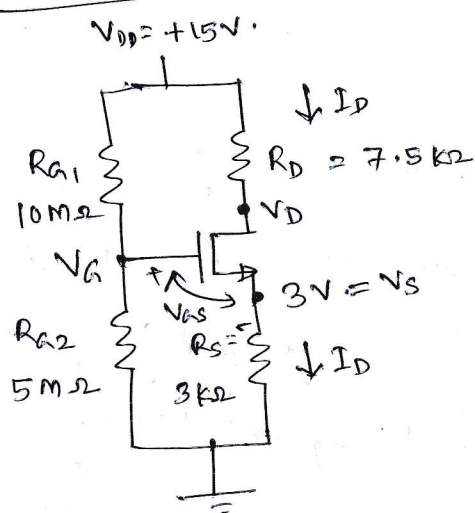Given, $V_{GS} = 2V$. $V_{TH} = 1V$.

$$V_G = V_{DD} \times \frac{R_{G2}}{R_{G1} + R_{G2}}$$

$$= 15 \times \frac{5}{10 + 5}$$

$$= 5V.$$

 $V_{GS} = 2V$. $V_G - V_S = 2V$.

$$V_S = (V_G - 2)V = (5 - 2) = 3V.$$

again, $V_S = I_D R_S$

$$3 = I_D \times 3k\Omega$$

$$\therefore I_D = 1mA$$

$$V_D = V_{DD} - I_D \times R_D$$

$$= 15 - 1mA \times 7.5k\Omega$$

$$\text{So, } V_{DS} = V_D - V_S$$

$$= (7.5 - 3)V = 4.5V.$$

$$V_D = 7.5V. \quad \text{--- (a)}$$

$$V_{DSat} = V_{GS} - V_{TH} = (2 - 1) = 1V.$$


 $V_{DS} > V_{DSat}$, so MOSFET is in saturation.

$$I_D = \frac{1}{2} \left(\frac{W}{L} \right) k_m' (V_{GS} - V_{TH})^2$$

$$1mA = \frac{1}{2} \times \frac{W}{L} \times 2mA/V^2 \times (2 - 1)^2$$

$$\therefore \frac{W}{L} = 1 \quad \text{--- (a)}$$

AC equivalent ckt:

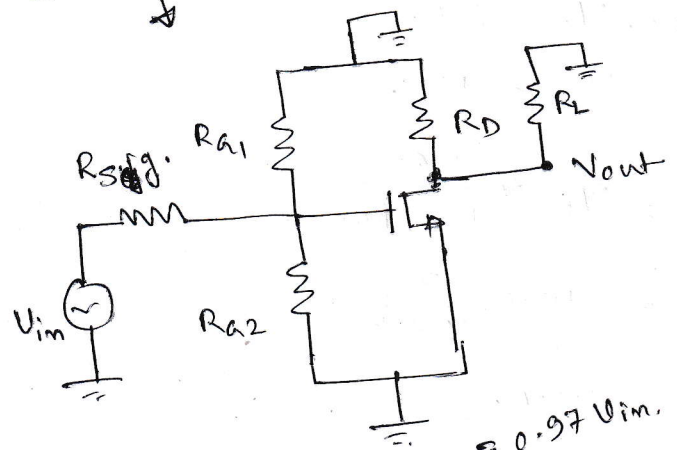

$$V_{gs} = \frac{(R_{A1} \parallel R_{A2})}{R_{sig} + (R_{A1} \parallel R_{A2})} \cdot V_{in} \approx 0.97 V_{in}$$

$$g_m = 2 K_m (V_{as} - V_{th})$$


$$= 2 \times 2 \text{ mA/V} \times (2 - 1) \text{ V}$$

$$= 2 \times 1 \times (2 - 1)$$

$$= 2 \text{ mA/V}$$

on
ms

g_m

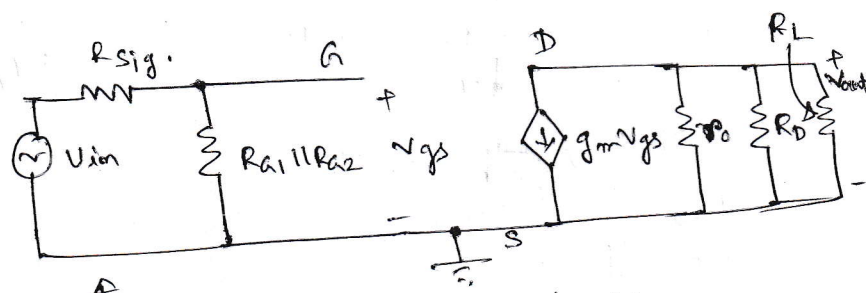

Small-signal equivalent ckt.

(b)

$$K_m = \frac{1}{2} \frac{W}{L} \cdot k_m'$$

$$= \frac{1}{2} \times 1 \times 2$$

$$= 1$$

$$r_o = \frac{1}{\lambda I_D} = \frac{1}{0.01 \times 1 \text{ mA}}$$

$$= 100 \text{ k}\Omega$$

~~Small-signal voltage gain = - g_m \cdot (r_o \parallel R_D \parallel R_L)~~

output voltage (V_out) = - g_m V_gs \cdot (r_o \parallel R_D \parallel R_L)

V_out = - g_m \cdot V_in \cdot (r_o \parallel R_D \parallel R_L)

Voltage Gain = $\frac{V_{out}}{V_{in}} = - g_m (r_o \parallel R_D \parallel R_L) = - 2 \times (7.5 \text{ k}\Omega \parallel 10 \text{ k}\Omega \parallel 100 \text{ k}\Omega)$



$$= - 2 \times 4.109$$

(b) $\boxed{= - 8.218}$ if $V_{in} \approx V_{gs}$ is considered

OR $\boxed{= - 7.97}$ if $V_{gs} = 0.97 V_{in}$ is considered.

If C_s is removed.

then equiv. ac. ckt.

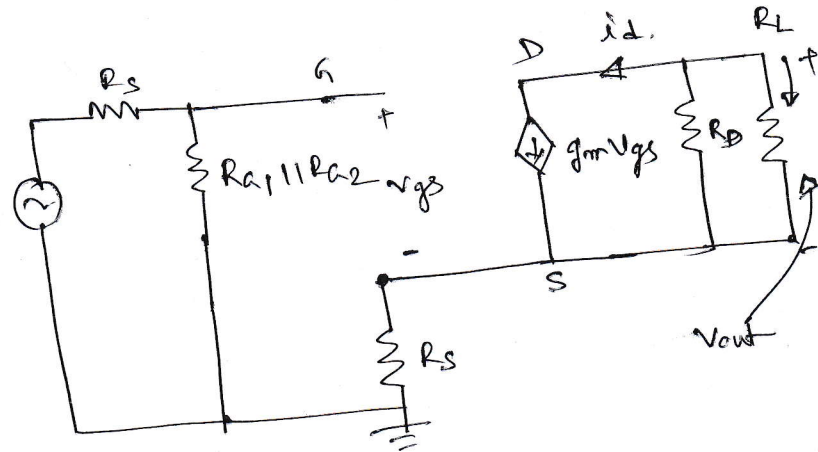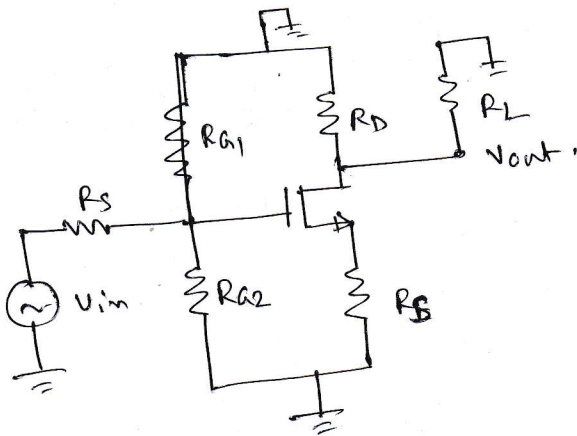

Small-signal equiv. ckt.

Considering, $\lambda = 0$, $r_o \Rightarrow \infty$.

$$\text{Voltage Gain} = -\frac{R_D}{R_S} = -\frac{7.5}{3} = \boxed{-2.5} \quad (c)$$

If C_1 is reduced drastically, then for the signal freq. C_1 can't be considered as short-ckt. Impedance of C_1 then should be considered and $V_{gs} < V_{in}$, so, small-signal gain reduces. (d)