

EXPERIMENT 4

NISARG UPADHYAYA
19CS30031 Nisarg..

ACTIVE LOW PASS FILTERS

AIM


To familiarize with 2nd order Sallen Key active low pass filters and to measure their frequency responses.

REPORT

① LT Spice Circuit Diagram

Attached below.

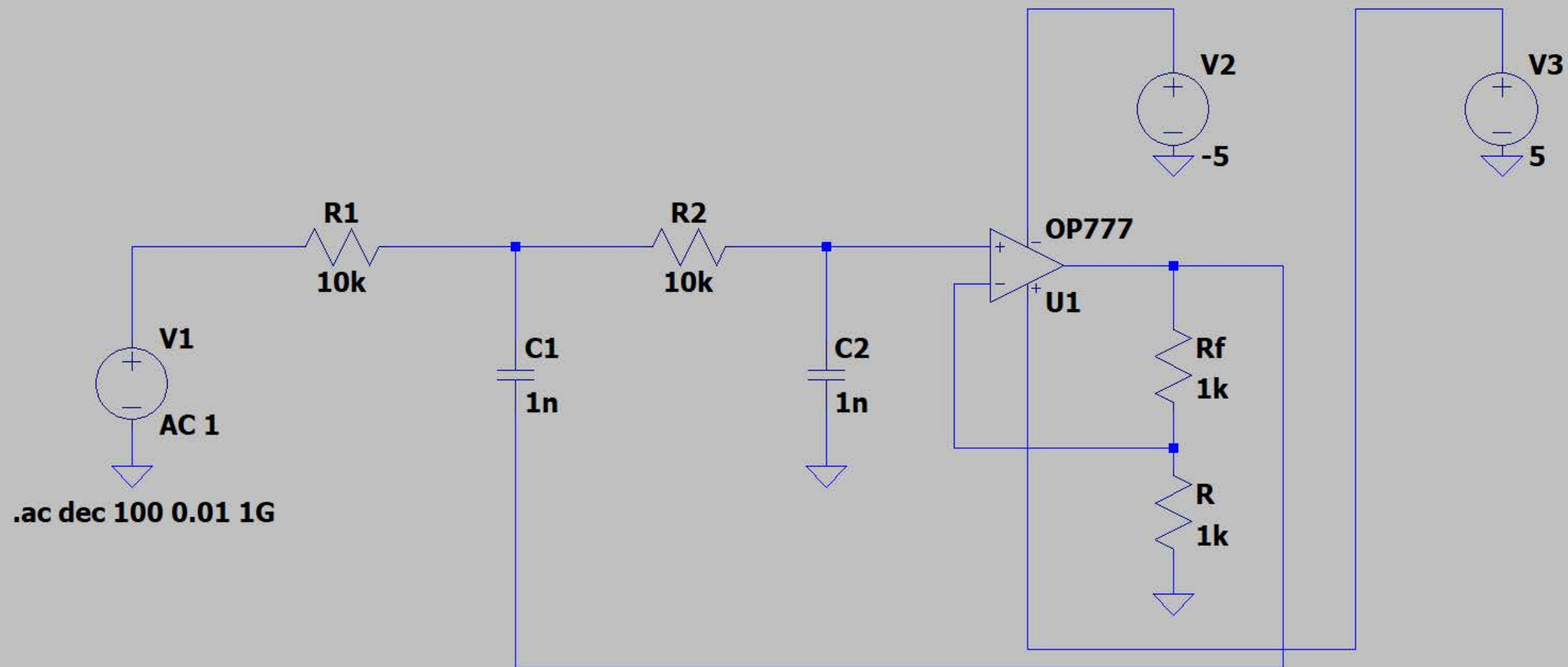Name: Nisarg Upadhyaya
Roll No: 19CS30031




$$(2) \quad R_1 = R_2 = 10 \text{ k}\Omega, \quad C_1 = C_2 = 1 \text{ nF}, \quad Q = 1$$

$$\Rightarrow Q = \frac{1}{3-K} = 1 \Rightarrow K=2 \Rightarrow 1 + \frac{R_b}{R} = 2 \Rightarrow \frac{R_b}{R} = 1$$

Hence, we can choose $R = R_b = 1 \text{ k}\Omega$.

$$\Rightarrow f_0 = \frac{1}{2\pi\sqrt{C_1 R C_2 R_2}} \text{ Hz} = \frac{1}{2\pi \times 10^{-9} \times 10^{-9}} \text{ Hz} = \frac{10^5}{2\pi} \text{ Hz} = 15915 \text{ Hz}$$

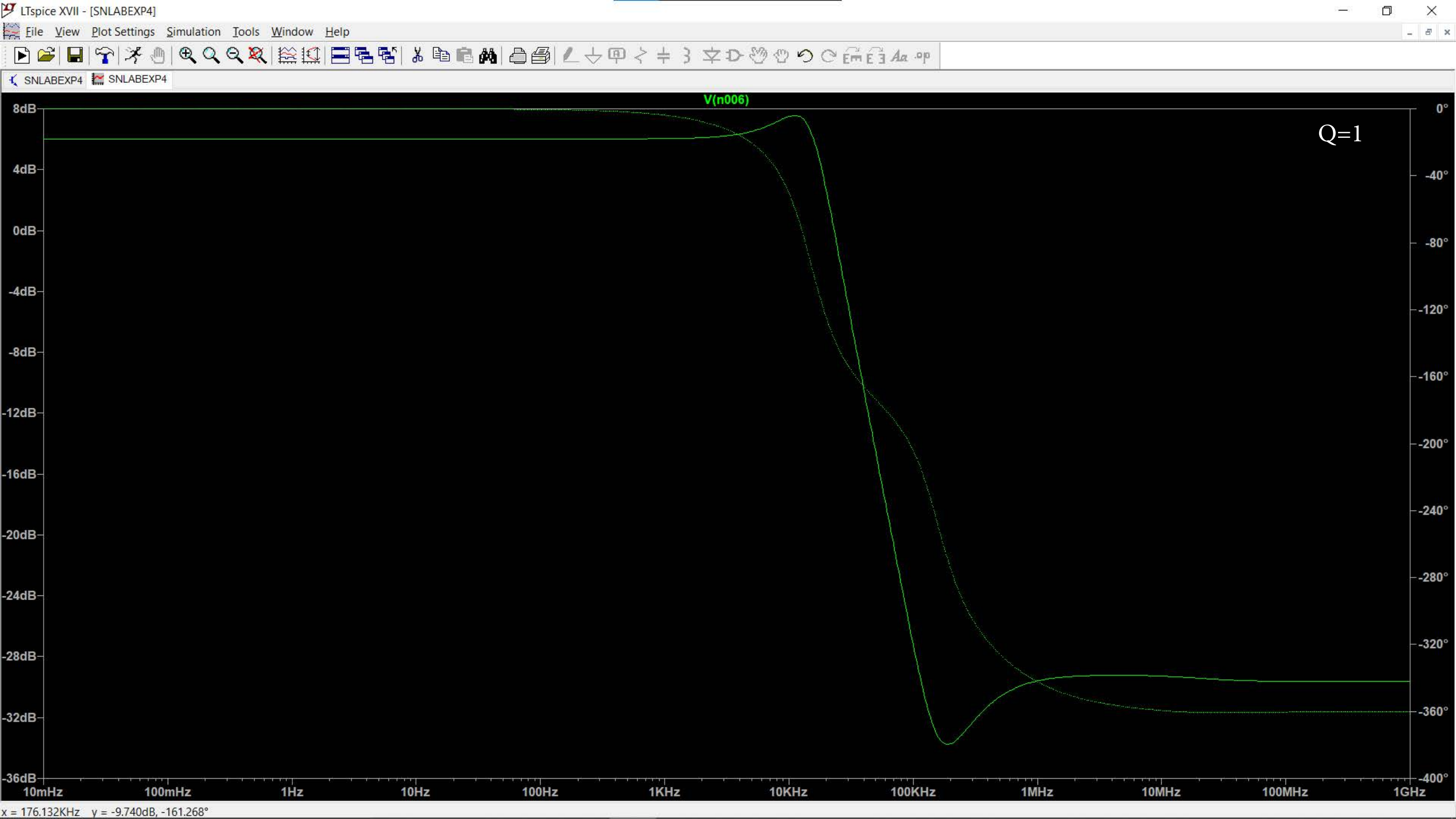Experimentally the peak in gain is obtained around 11.3 kHz. The peak is not very sharp though owing to the low Q-factor. The transition is not very sharp.



③ $Q = 1.5, 2.5$


$$\Rightarrow Q = \frac{1}{3-K} = \frac{3}{2} \Rightarrow K = \frac{7}{3} \Rightarrow 1 + \frac{R_f}{R} = \frac{7}{3} \Rightarrow \frac{R_f}{R} = \frac{4}{3}$$


Hence, we can choose $R_f = 2k\Omega$ and $R = 1.5k\Omega$

$$\Rightarrow Q = \frac{1}{3-K} = \frac{5}{2} \Rightarrow K = \frac{13}{5} \Rightarrow 1 + \frac{R_f}{R} = \frac{13}{5} \Rightarrow \frac{R_f}{R} = \frac{8}{5}$$

Hence, we can choose $R_f = 2k\Omega$ and $R = 1.25k\Omega$.

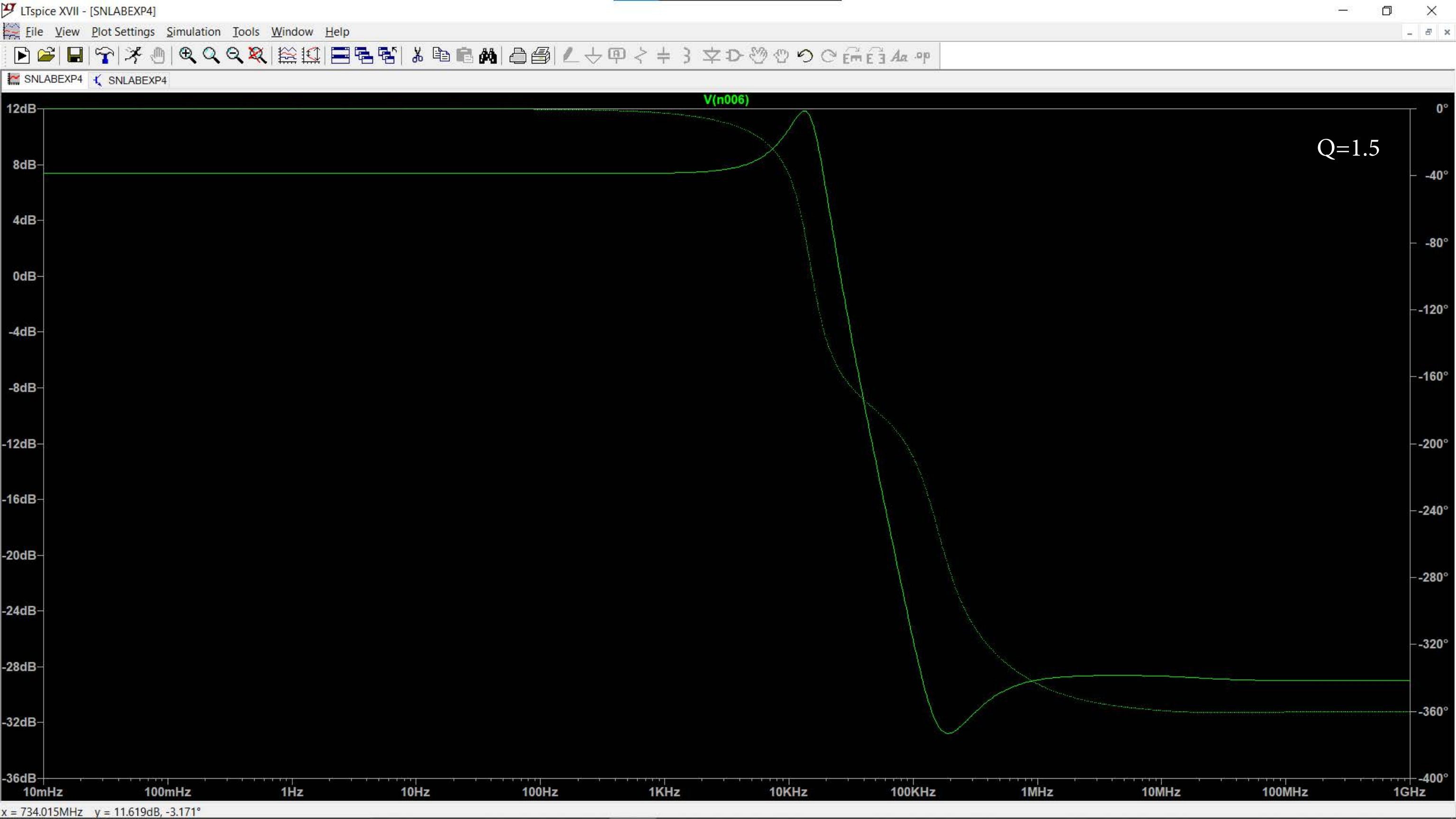As expected, when we increase the Q -factor the sharpness of the peak increases. The filter now offers a much sharper transition. The peak in gain now occurs around a frequency of $14.5kHz$. Also the initial fall (roll off) after the peak is much steeper than for $Q=1$. Thus this offers a comparatively higher selectivity.



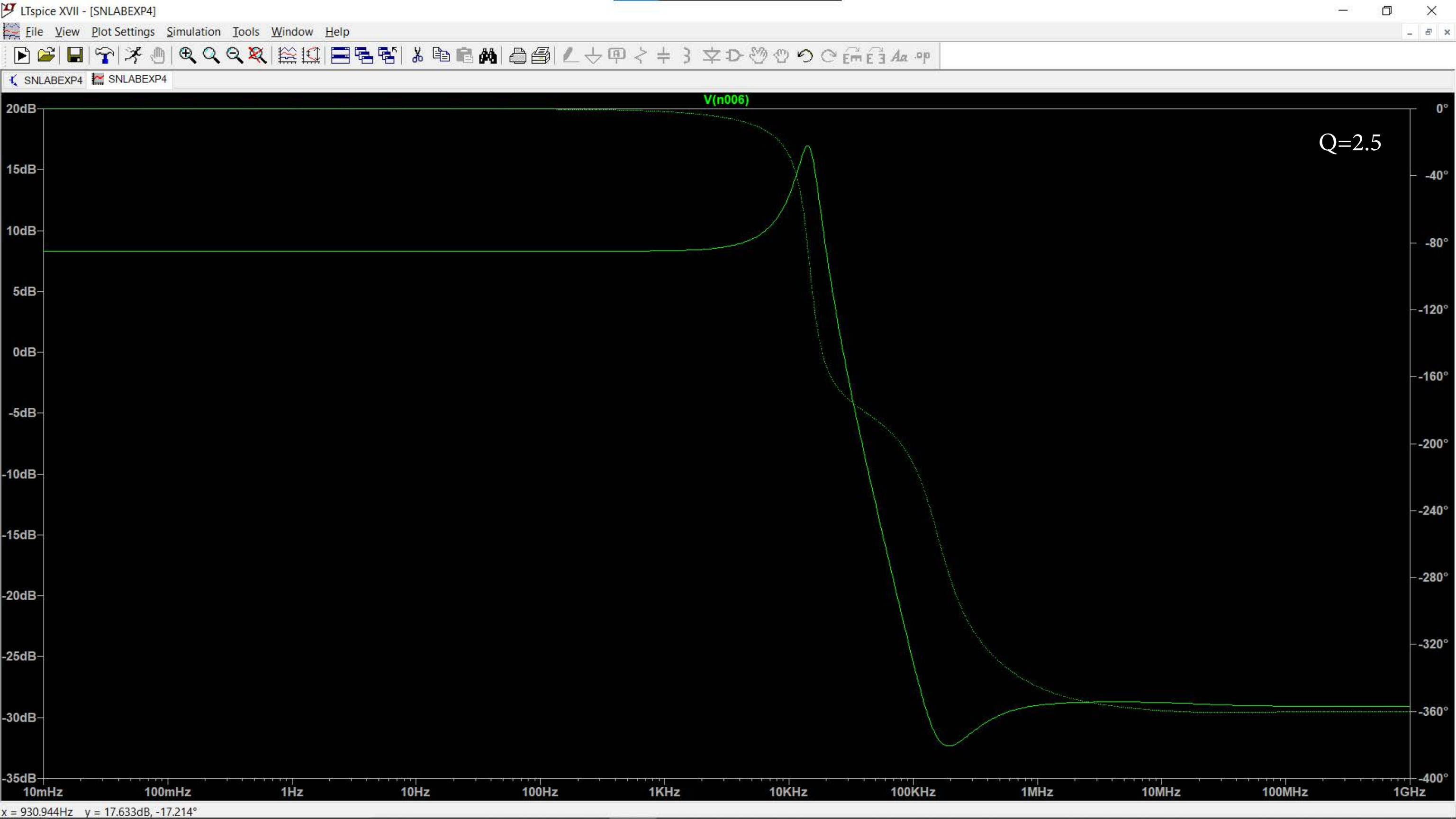

(4) $R_1 = R_2 = 10 \text{ k}\Omega$, $C_1 = C_2 = 1 \mu\text{F}$, $Q = 2.5$

NISARG UPADHYAYA
19CS30031 Nimg.

$$\Rightarrow Q = \frac{1}{3-K} = \frac{5}{2} \Rightarrow K = \frac{13}{5} \Rightarrow 1 + \frac{R_f}{R} = \frac{13}{5} \Rightarrow \frac{R_f}{R} = \frac{8}{5}$$

Hence we can choose $R_f = 2 \text{ k}\Omega$ and $R = 1.25 \text{ k}\Omega$

$$\Rightarrow f_0 = \frac{1}{2\pi\sqrt{R_1 R_2}} \text{ Hz} = \frac{1}{2\pi RC} \text{ Hz} = \frac{10^8}{2\pi} \text{ Hz} = 15915 \text{ kHz}$$

Experimentally the gain starts to drop around 150 kHz and reaches -3dB value near 300 kHz. The huge difference between theoretical and experimental value stems from the fact that the op-amp used (OP-777) has a finite bandwidth. (non ideal) Moreover this bandwidth is much lesser (for the OP-AMP used) than 15915 kHz. Due to this the OP-AMP deviates from its ideal behaviour. It can be observed by using a different OP-AMP such as LT-1226 the roll-off occurs near the expected value.

