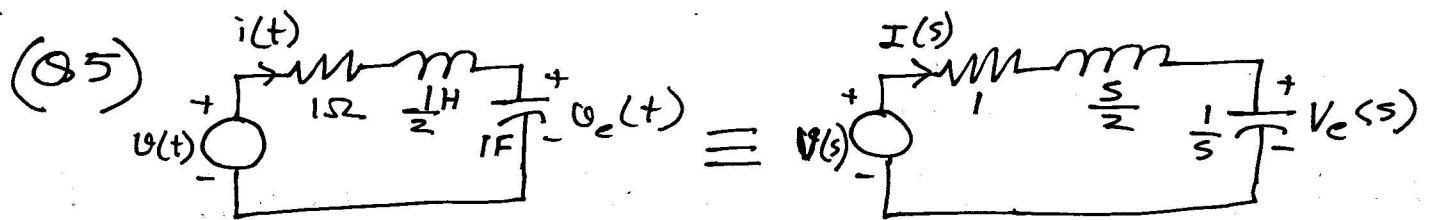


Tutorial Solution



(Since all initial conditions are relaxed / zero)

$$\therefore V(s) = I(s) \left(1 + \frac{s}{2} + \frac{1}{s} \right) = I(s) \left(\frac{s^2 + 2s + 2}{2s} \right)$$

$$\Rightarrow I(s) = \frac{2s V(s)}{s^2 + 2s + 2}$$

$$\text{and } V_c(s) = \frac{1}{s} I(s) = \frac{2 V(s)}{s^2 + 2s + 2}$$

$$(a) u(t) = u(t) \Rightarrow V(s) = \frac{1}{s}$$

$$\therefore I(s) = \frac{2s \frac{1}{s}}{s^2 + 2s + 2} = \frac{2}{s^2 + 2s + 2} = \frac{2}{(s+1)^2 + 1^2}$$

$$\therefore i(t) = \mathcal{L}^{-1}\{I(s)\} = 2e^{-t} \sin(t) u(t)$$

$$V_c(s) = \frac{2}{s(s^2 + 2s + 2)} = \frac{A}{s} + \frac{Bs + C}{s^2 + 2s + 2}$$

(for some real values of A, B and C)

$$\text{Now } As^2 + 2As + 2A + Bs^2 + Cs = 2$$

$$\Rightarrow A = 1, \quad A + B = 0 \text{ or } B = -1$$

$$\text{and } 2A + C = 0 \text{ or } C = -2$$

$$\therefore V_c(s) = \frac{1}{s} - \frac{s}{s^2 + 2s + 2} - \frac{2}{s^2 + 2s + 2}$$

$$= \frac{1}{s} - \frac{(s+1)}{(s+1)^2 + 1^2} - \frac{1}{(s+1)^2 + 1^2}$$

$$\therefore v_c(t) = \mathcal{L}^{-1}\{V_c(s)\} = u(t) [1 - e^{-t}(\cos t + \sin t)]$$

$$(b) \quad U(t) = t u(t) \Rightarrow V(s) = \frac{1}{s^2}$$

$$\therefore I(s) = \frac{2}{s(s^2+2s+2)}$$

$$\therefore i(t) = \mathcal{L}^{-1}\{I(s)\} = (1 - e^{-t}(\cos t + \sin t)) u(t)$$

$$\text{And } V_c(s) = \frac{2}{s^2(s^2+2s+2)} = \frac{A}{s} + \frac{B}{s^2} + \frac{Cs+D}{s^2+2s+2}$$

Such that

$$As^3 + 2As^2 + 2As + Bs^2 + 2Bs + 2B + Cs^3 + Ds^2 = 2$$

$$\Rightarrow (A+C)s^3 + (2A+B+D)s^2 + (2A+2B)s + 2B = 2$$

$$\Rightarrow B = 1$$

$$2A+2B=0 \Rightarrow A = -1$$

$$A+C=0 \Rightarrow C = +1$$

$$2A+B+D=0 \Rightarrow D = 1$$

$$\therefore V_c(s) = \frac{-1}{s} + \frac{1}{s^2} + \frac{s}{s^2+2s+2} + \frac{1}{s^2+2s+2}$$

$$= -\frac{1}{s} + \frac{1}{s^2} + \frac{s+1}{(s^2+2s+2)}$$

$$\therefore V_c(t) = u(t) \left[-1 + t + e^{-t} \cos(t) \right]$$

$$(Q4)(a) \mathcal{L}^{-1} \left\{ \frac{Js}{s+1+Js} - \frac{Js}{s+1-Js} - \frac{1}{(s+1+Js)^2} - \frac{1}{(s+1-Js)^2} \right\}$$

$$= (Js e^{-(1+J)t} - Js e^{-(1-J)t}$$

$$- t e^{-(1+J)t} - t e^{-(1-J)t}) u(t)$$

$$= (e^{-t} J (e^{-Jt} - e^{Jt}) - t e^{-t} (e^{-Jt} + e^{Jt})) u(t)$$

$$= \left(e^{-t} 2 \frac{(e^{Jt} - e^{-Jt})}{2J} - t e^{-t} 2 \frac{(e^{Jt} + e^{-Jt})}{2} \right) u(t)$$

$$= 2e^{-t} (\sin t - t \cos t) u(t)$$

$$(b) \mathcal{L}^{-1} \left\{ \frac{Jb}{(s-J)^2} - \frac{Jb}{(s+J)^2} \right\}$$

$$= Jb (t u(t) (e^{Jt} - e^{-Jt}))$$

$$= b t u(t) \frac{e^{Jt} - e^{-Jt}}{2J} \times 2J^2$$

$$= -2bt \sin t u(t)$$

$$\begin{aligned}
 (Q3)(a) \quad \frac{s^3}{(s+2)(s+3)(s+4)} &= \frac{s^3}{(s+2)(s^2+7s+12)} \\
 &= \frac{s^3}{s^3+9s^2+26s+24} = 1 - \frac{9s^2+26s+24}{s^3+9s^2+26s+24} \\
 &= 1 - \left(\frac{A}{s+2} + \frac{B}{s+3} + \frac{C}{s+4} \right)
 \end{aligned}$$

such that

$$\begin{aligned}
 A(s+3)(s+4) + B(s+2)(s+4) + C(s+2)(s+3) \\
 = 9s^2 + 26s + 24
 \end{aligned}$$

for putting $s = -2$

$$A(-1) = 8 \Rightarrow A = -8$$

putting $s = -3$

$$B(-1) = 27 \Rightarrow B = -27$$

putting $s = -4$

$$C(2) = 64 \Rightarrow C = 32$$

\therefore Given expression

$$= 1 - \frac{8}{s+2} + \frac{27}{s+3} - \frac{32}{s+4}$$

\therefore Required Laplace inverse

$$= \delta(t) - 8e^{-2t}u(t) + 27e^{-3t}u(t) - 32e^{-4t}u(t)$$

$$(b) X(s) = \frac{3s^2 + 2s + 2}{(s+2)^2(s+3)} = \frac{A}{s+3} + \frac{B}{s+2} + \frac{C}{(s+2)^2}$$

such that

$$A(s+2)^2 + B(s+3)(s+2) + C(s+3) = 3s^2 + 2s + 2$$

putting $s = -3$, $A = 23$

$\therefore (A+B) = 3$ (equating the coefficient of s^2)

$$\Rightarrow B = -20$$

$\therefore 4A + 6B + 3C = 2$ (equating the constant term)

$$\Rightarrow 92 - 120 + 3C = 2 \Rightarrow C = 10$$

$$\therefore X(s) = \frac{23}{s+3} - \frac{20}{s+2} + \frac{10}{(s+2)^2}$$

$$\therefore \mathcal{L}^{-1}\{X(s)\} = 23e^{-3t}u(t) - 20e^{-2t}u(t) + 10te^{-2t}u(t)$$

$$(c) X(s) = \frac{4s^2 - 3s + 5}{s(s^2 + 2s + 5)} = \frac{4s^2 - 3s + 5}{s(s - (-1 + 2j))(s - (-1 - 2j))}$$

$$= \frac{A}{s} + \frac{B}{s+1-2j} + \frac{C}{s+1+2j}$$

such that

$$A(s+1-2j)(s+1+2j) + Bs(s+1+2j) + Cs(s+1-2j) = 4s^2 - 3s + 5$$

putting $s = 0$, $A(5) = 5 \Rightarrow A = 1$

putting $s = -1 + 2j$, $B(-1+2j)(4j) = 4(1-4-4j) - 3(-1+2j) + 5$

$$\Rightarrow B(-8-4j) = -12-16j+3-6j+5$$

$$= -4-22j$$

$$\Rightarrow B = \frac{4+22j}{-8-4j} = \frac{(4+22j)(8-4j)}{80} = \frac{120+160j}{80}$$

$$= \frac{3+4j}{2}$$

$$\therefore e = B^* = \frac{3-4j}{2}$$

$$\therefore X(s) = \frac{1}{s} + \frac{3+4j}{2(s+1-2j)} + \frac{3-4j}{2(s+1+2j)}$$

$$\therefore \mathcal{L}^{-1}\{X(s)\} = u(t) + \frac{3+4j}{2} e^{-(1-2j)t} u(t) + \frac{3-4j}{2} e^{-(1+2j)t} u(t)$$


$$= \left(1 + \frac{5}{2} e^{j\theta} e^{-t} e^{2jt} + \frac{5}{2} e^{-j\theta} e^{-t} e^{-2jt} \right) u(t)$$

$$\text{where } \theta = \tan^{-1}\left(\frac{4}{3}\right)$$

$$= \left(1 + \frac{5}{2} e^{-t} \left(e^{j(2t+\theta)} + e^{-j(\theta+2t)} \right) \right) u(t)$$

$$= \left(1 + \frac{5}{2} e^{-t} \times 2 \cos(2t+\theta) \right) u(t)$$
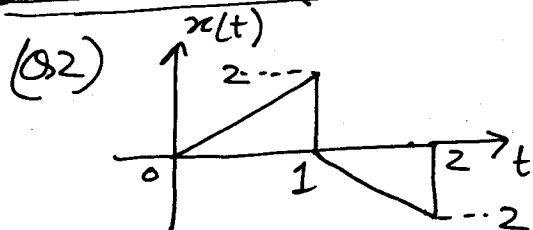
$$= \left(1 + 5e^{-t} \cos\left(2t + \tan^{-1}\left(\frac{4}{3}\right)\right) \right) u(t)$$



$$\begin{aligned} x(t) &= 2r(t) - 2r(t-1) - 2u(t-1) \\ &\quad - 2r(t-1) + 2r(t-2) + 2u(t-2) \\ &= 2r(t) - (4r(t-1) + 2u(t-1)) \\ &\quad + (2r(t-2) + 2u(t-2)) \end{aligned}$$


$$\therefore X(s) = \frac{2}{s^2} - \left(\frac{4}{s^2} + \frac{2}{s} \right) e^{-s} + \left(\frac{2}{s^2} + \frac{2}{s} \right) e^{-2s}$$

$$= X_1(s) + X_2(s) e^{-s} + X_3(s) e^{-2s} \quad (\text{as given})$$


$$\therefore X_1(s) = \frac{2}{s^2}$$

$$X_2(s) = -\left(\frac{4}{s^2} + \frac{2}{s} \right)$$
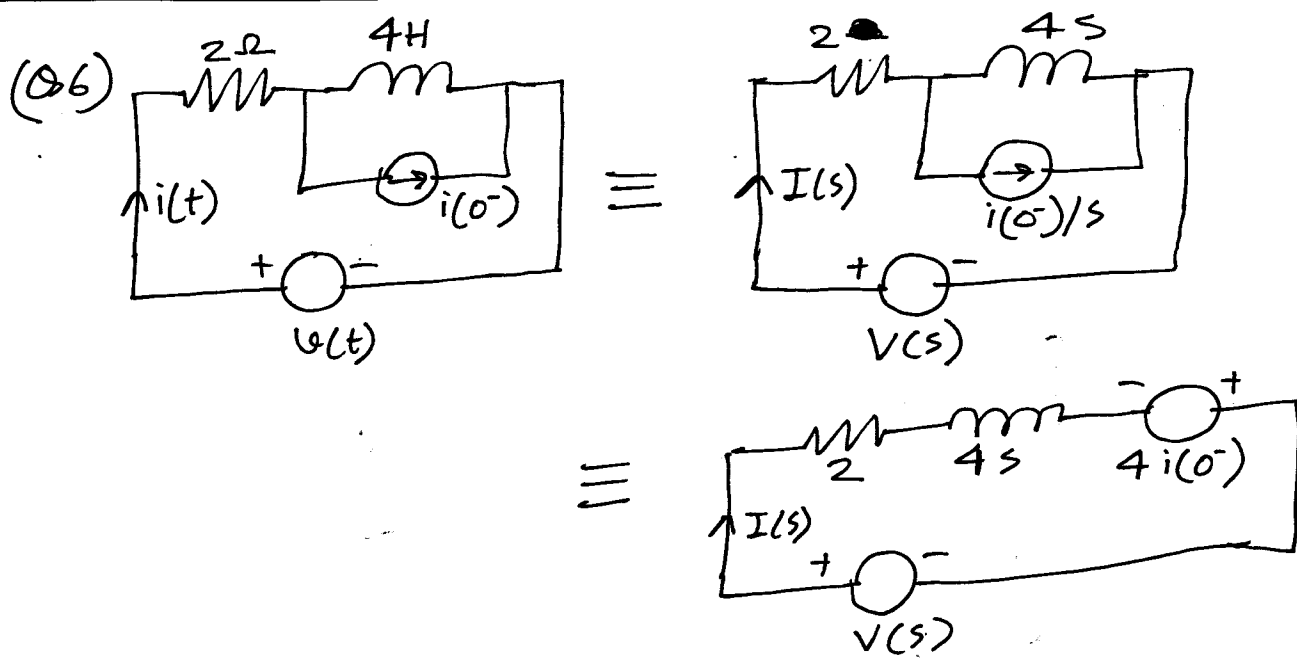
$$X_3(s) = \left(\frac{2}{s^2} + \frac{2}{s} \right)$$


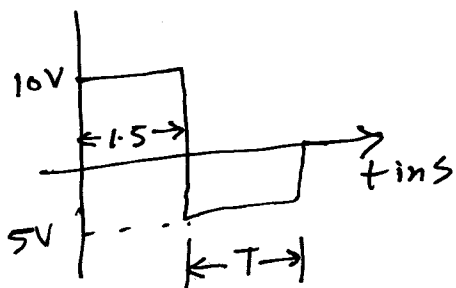
$$\therefore I(s) = \frac{V(s) + 4i(0^-)}{2 + 4s}$$



$$\therefore v(t) = 10u(t) - 5u(t-1.5) + 5u(t-T-1.5)$$

$$\therefore V(s) = \frac{10 - 5e^{-1.5s} + 5e^{-(T+1.5)s}}{s}$$

(a) $T = 4$ and $i(0^-) = 0$

$$\therefore I(s) = \frac{V(s)}{2 + 4s} = \frac{10 - 5e^{-1.5s} + 5e^{-(T+1.5)s}}{s} \times \frac{1}{2 + 4s}$$


$$= \frac{(10 - 5e^{-1.5s} + 5e^{-5.5s})}{2} \times \left(\frac{1}{s} - \frac{1}{s + 1/2} \right)$$

$$\therefore i(t) = \mathcal{L}^{-1}(I(s))$$

$$= 5u(t) - 5e^{-1/2 t} u(t) - 7.5u(t-1.5) + 7.5e^{-1/2(t-1.5)} u(t-1.5) + 2.5u(t-5.5) - 2.5e^{-1/2(t-5.5)} u(t-5.5)$$

$$= 5(1 - e^{-t/2})u(t) - 7.5(1 - e^{-\frac{(t-1.5)}{2}})u(t-1.5) + 2.5(1 - e^{-\frac{(t-5.5)}{2}})u(t-5.5)$$

Sketch

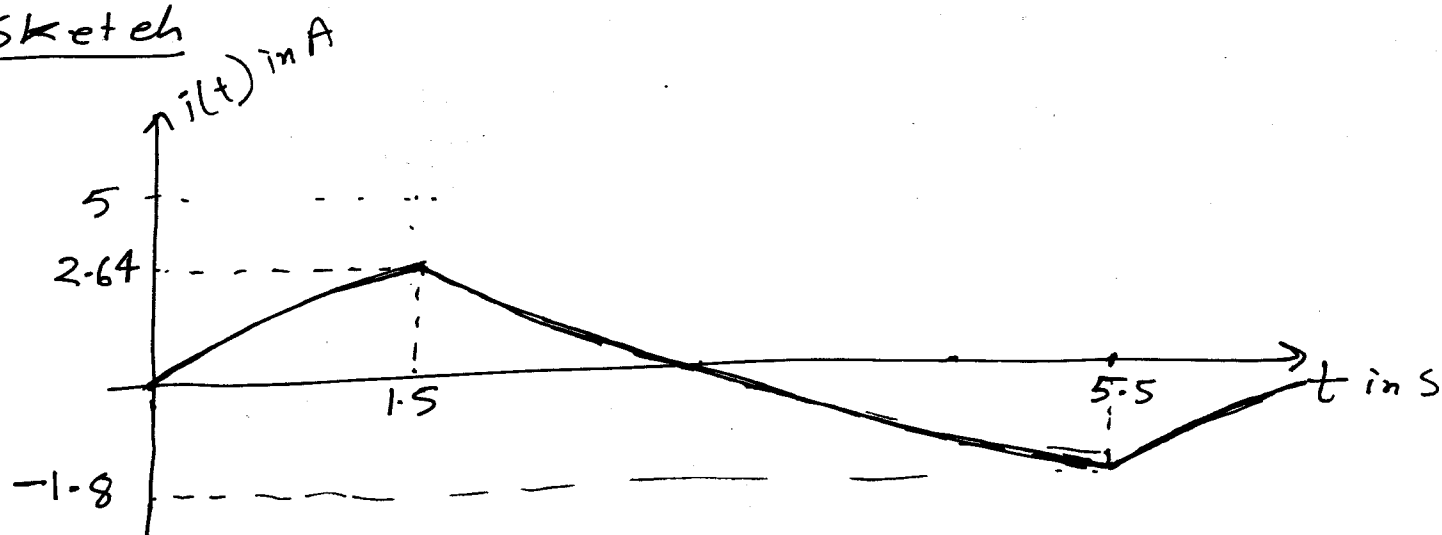

(b) $T=1$, $i(0^-)=0$


$$\therefore I(s) = \frac{V(s)}{2+4s} = \frac{10-15e^{-1.5s} + 5e^{-2.5s}}{s} \times \frac{1}{2+4s}$$

$$= \frac{(10-15e^{-1.5s} + 5e^{-2.5s})}{2} \times \left(\frac{1}{s} - \frac{1}{s+1/2} \right)$$

$$\therefore i(t) = \mathcal{L}^{-1}\{I(s)\}$$

$$= 5(1-e^{-t/2})u(t) - 7.5(1-e^{-(t-1.5)/2})u(t-1.5) + 2.5(1-e^{-(t-2.5)/2})u(t-2.5)$$

Sketch

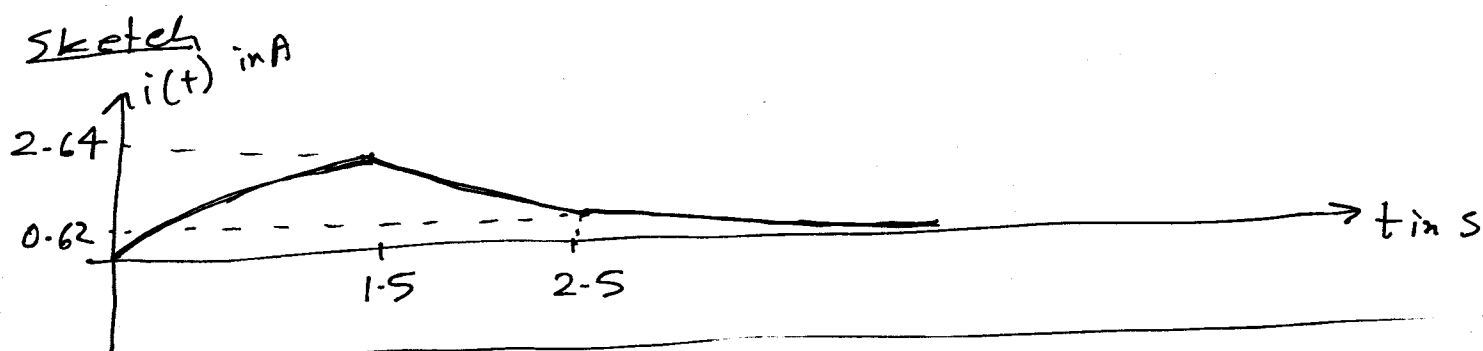

(c) $T=2$, $i(0^-)=1$


$$\therefore I(s) = \frac{V(s) + 4i(0^-)}{4s+2} = \frac{V(s)}{4s+2} + \frac{i(0^-)}{s+1/2}$$

$$= \frac{10-15e^{-1.5s} + 5e^{-3.5s}}{s} \times \frac{1}{4s+2} + \frac{1}{s+1/2}$$

$$= \frac{10 - 15e^{-1.5s} + 5e^{-3.5s}}{2} \times \left(\frac{1}{s} - \frac{1}{s+1/2} \right) + \frac{1}{s+1/2}$$

$$\therefore i(t) = \mathcal{L}^{-1}\{I(s)\}$$
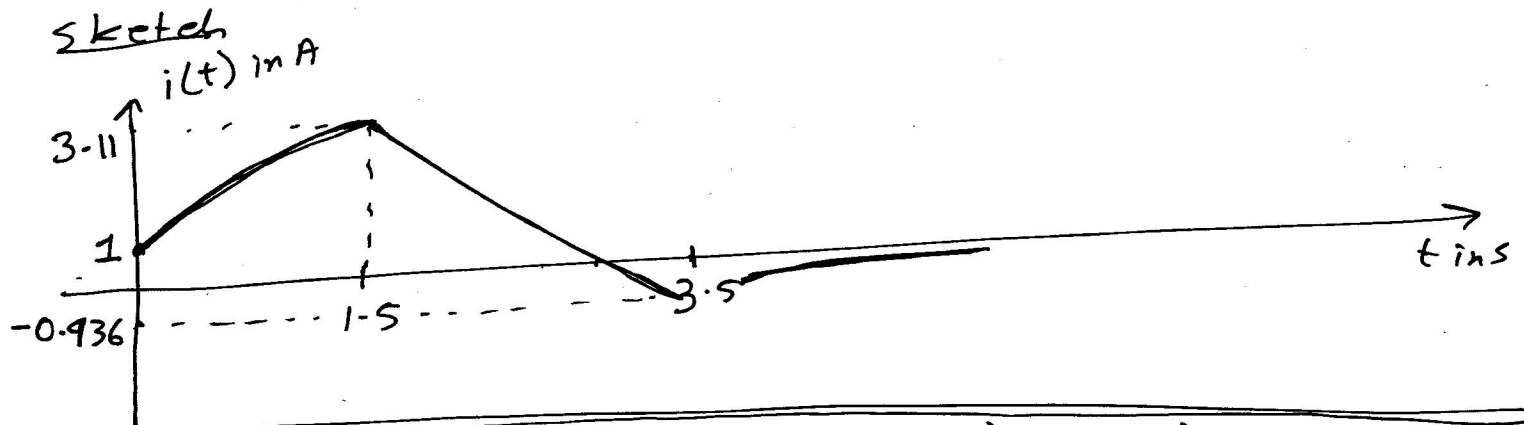
$$= 5(1 - e^{-t/2})u(t) - 7.5(1 - e^{-(t-1.5)/2})u(t-1.5) + 2.5(1 - e^{-(t-3.5)/2})u(t-3.5) + e^{-t/2}u(t)$$



(Q7) If $R=0$ then $I(s) = \frac{V(s) + 4i(0^-)}{4s}$


The circuit diagram, $v(t)$, $V(s)$ are all same as Q6

(a) $T=4$ and $i(0^-)=0$

$$\therefore I(s) = \frac{V(s)}{4s} = \frac{10 - 15e^{-1.5s} + 5e^{-5.5s}}{4s^2}$$

$$\therefore i(t) = \mathcal{L}^{-1}\{I(s)\} = 2.5t u(t) - 3.75(t-1.5)u(t-1.5) + 1.25(t-5.5)u(t-5.5)$$

Sketch

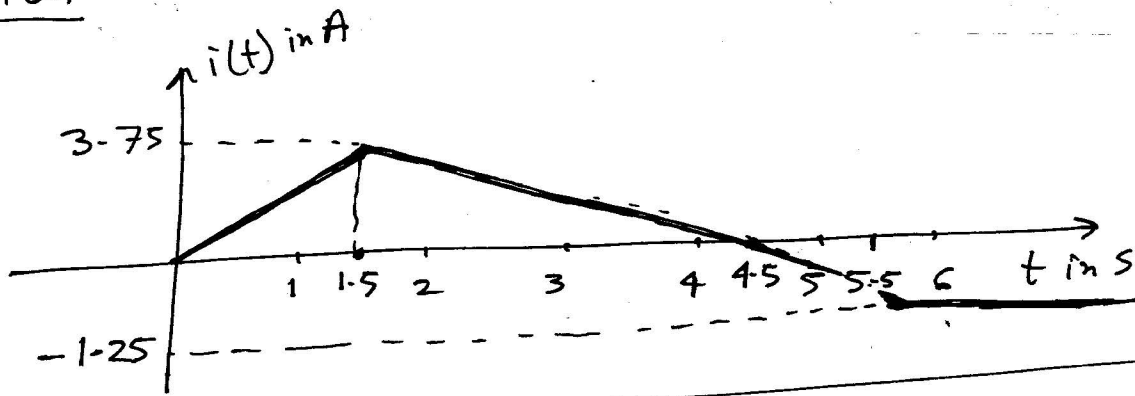


(b) $T=1$ $i(0^-)=0$

$$\therefore I(s) = \frac{V(s)}{4s} = \frac{10 - 15e^{-1.5s} + 5e^{-2.5s}}{4s^2}$$

$$\therefore i(t) = 2.5t u(t) - 3.75(t-1.5)u(t-1.5) + 1.25(t-2.5)u(t-2.5)$$


Sketch

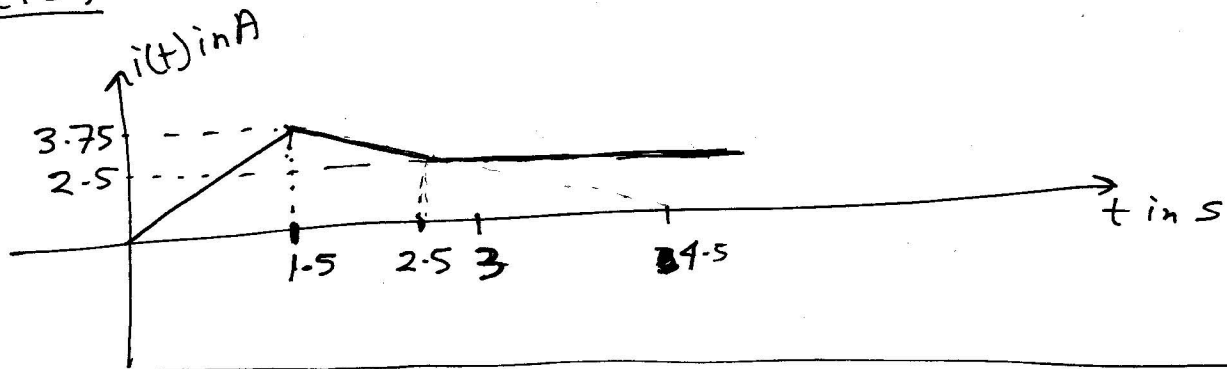

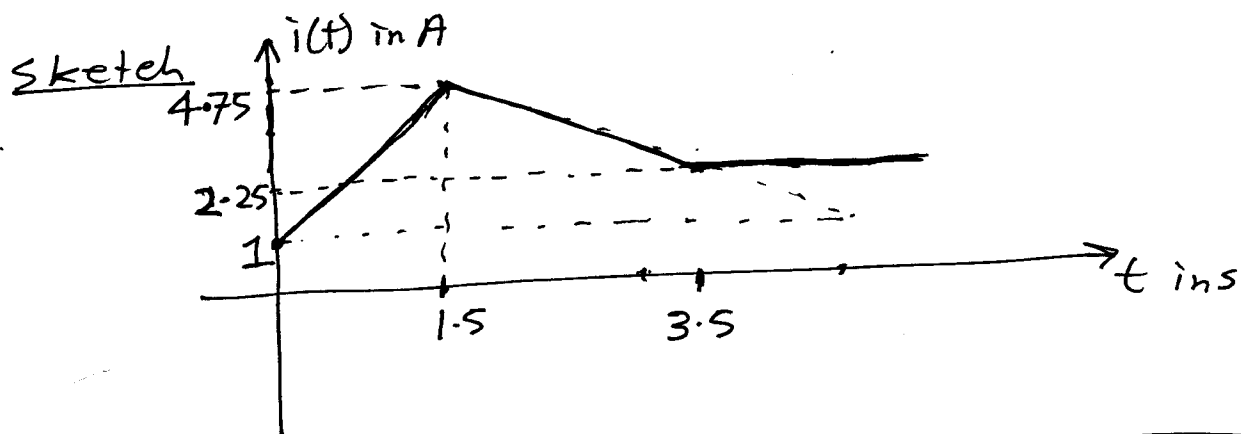(c) $T=2$, $i(0^-)=1$

$$\begin{aligned} \therefore I(s) &= \frac{V(s) + 4i(0^-)}{4s} = \frac{V(s)}{4s} + \frac{i(0^-)}{s} \\ &= \frac{10 - 15e^{-1.5s} + 5e^{-3.5s}}{4s^2} + \frac{1}{s} \end{aligned}$$

$$\therefore i(t) = 2.5t u(t) - 3.75(t-1.5)u(t-1.5) + 1.25(t-3.5)u(t-3.5) + u(t)$$



(Q1) (a) $t \cos(t) u(t)$

$$\mathcal{L}\{\cos(t) u(t)\} = \frac{s}{s^2 + 1}$$

$$\therefore \mathcal{L}\{t \cos(t) u(t)\} = \frac{d}{ds} \left(\frac{s}{s^2 + 1} \right) \quad \left[\because \mathcal{L}\{t x(t)\} = \frac{d}{ds} X(s) \right]$$

$$= \frac{1(s^2 + 1) - 2s \times s}{(s^2 + 1)^2} = \frac{1 - s^2}{(s^2 + 1)^2}$$

(b) $t \sin(t) u(t)$

$$\mathcal{L}\{\sin(t) u(t)\} = \frac{1}{s^2 + 1}$$

$$\therefore \mathcal{L}\{t \sin(t) u(t)\} = \frac{d}{ds} \left(\frac{1}{s^2 + 1} \right) \quad \left[\because \mathcal{L}\{t x(t)\} = \frac{d}{ds} X(s) \right]$$


$$= \frac{-2s}{(s^2 + 1)^2}$$

(c) $\mathcal{L}\{e^{-t} t \cos(t) u(t)\} = \frac{1 - (s+1)^2}{((s+1)^2 + 1)^2} \quad \left[\because \mathcal{L}\{e^{-at} x(t)\} = X(s+a) \right]$

$$= \frac{-s^2 - 2s}{(s^2 + 2s + 2)^2}$$


(d) $\mathcal{L}\{e^t t \sin(t) u(t)\} = \frac{-2(s+1)}{((s+1)^2 + 1)^2} \quad \left[\because \mathcal{L}\{e^{at} x(t)\} = X(s-a) \right]$

$$= \frac{-2s - 2}{(s^2 + 2s + 2)^2}$$

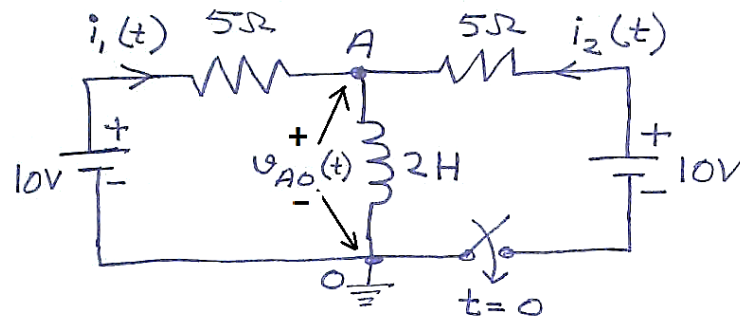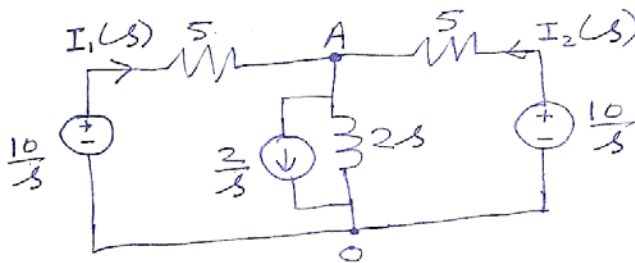QUESTION 8:

The switch was closed at $t = 0$. Before that the circuit was already in a steady state. Using circuit analysis in Laplace domain, find the expression for the voltage $v_{AO}(t)$ and current $i_2(t)$ for $t \geq 0$.

Initial current through inductor (before closing switch) $= \frac{10V}{5\Omega} = 2A$ (top to bottom)



KCL at A:

$$V_{AO}(s) \left(\frac{1}{5} + \frac{1}{5} + \frac{1}{2s} \right) = -\frac{2}{s} + \frac{10}{s} + \frac{10}{s}$$

$$\Rightarrow V_{AO}(s) \left(\frac{4s+5}{10s} \right) = -\frac{2}{s} + \frac{2}{s} + \frac{2}{s} = \frac{2}{s}$$


$$\Rightarrow V_{AO}(s) = \frac{2}{s} \times \frac{10s}{4s+5} = \frac{20}{4s+5} = \frac{5}{s + \frac{5}{4}}$$

$$\therefore V_{AO}(t) = 5e^{-\frac{5t}{4}} u(t)$$

$$I_2(s) = \frac{\frac{10}{s} - V_{AO}(s)}{5} = \frac{\frac{10}{s} - \frac{5}{s + \frac{5}{4}}}{5} = \frac{2}{s} - \frac{1}{s + \frac{5}{4}}$$

$$\therefore i_2(t) = 2u(t) - e^{-\frac{5t}{4}} u(t)$$

QUESTION 9:

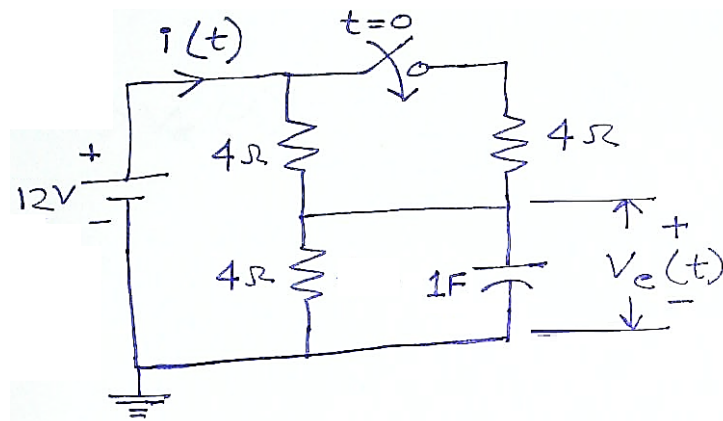


The switch was closed at $t = 0$. Before that the circuit was already in a steady state. Using circuit analysis in Laplace domain, find the expression for the capacitor voltage $v_c(t)$ and current $i(t)$ for $t \geq 0$.

Initial capacitor voltage

$$v_c(0) = 12V \times \frac{4\Omega}{4\Omega + 4\Omega} = 6V \text{ (upper side positive)}$$

(using potential divider rule)

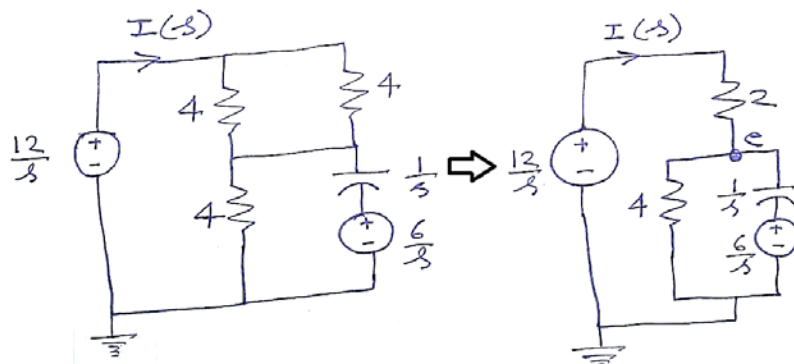

KCL at node e:

$$V_e(s) \left(\frac{1}{2} + \frac{1}{4} + s \right) = \frac{12}{s} + \frac{6}{\frac{1}{s}}$$

$$\Rightarrow V_e(s) \left(\frac{3+4s}{4} \right) = \frac{6}{s} + 6 = \frac{6+6s}{s}$$

$$\begin{aligned}\Rightarrow V_e(s) &= \frac{6+6s}{s} \times \frac{4}{3+4s} \\&= 24 \frac{(1+s)}{s(3+4s)} \\&= \frac{6(3+4s+1)}{s(3+4s)} \\&= 6 \left(\frac{1}{s} + \frac{1}{s(3+4s)} \right) \\&= 6 \left(\frac{1}{s} \right) + 2 \left(\frac{1}{s} - \frac{4}{3+4s} \right) \\&= \frac{8}{s} - \frac{8}{3+4s}\end{aligned}$$

$$\begin{aligned}\therefore v_e(t) &= 8u(t) - \frac{8}{4} e^{-\frac{3}{4}t} u(t) \\&= (8 - 2e^{-\frac{3}{4}t})u(t)\end{aligned}$$


$$I(s) = \frac{\frac{12}{s} - V_e(s)}{2} = \frac{\frac{12}{s} - \frac{8}{s} + \frac{8}{3+4s}}{2}$$

$$= \frac{2}{s} + \frac{4}{3+4s}$$

$$= \frac{2}{s} + \frac{1}{s + \frac{3}{4}}$$

$$\begin{aligned}\therefore i(t) &= 2u(t) + e^{-\frac{3}{4}t} u(t) \\&= (2 + e^{-\frac{3}{4}t})u(t)\end{aligned}$$


QUESTION 10:

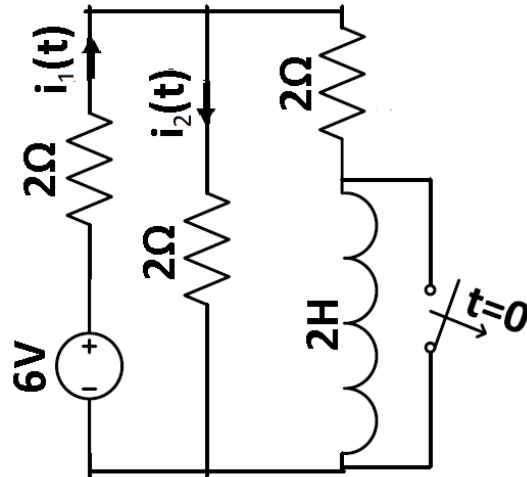

The switch was **opened** at $t = 0$. Before that the circuit was already in a steady state. (Assume the inductor has a very low amount of resistance but the switch has much lower resistance)

Using circuit analysis in Laplace domain, find the expression for the current $i_1(t)$ and $i_2(t)$ for $t \geq 0$.

Initial current through the inductor = 0

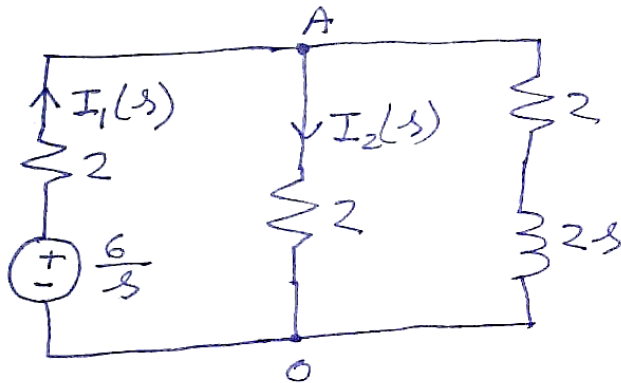

KCL at A

$$V_{AO}(s) \left(\frac{1}{2} + \frac{1}{2} + \frac{1}{2+2s} \right) = \frac{6}{s}$$

$$\Rightarrow V_{AO}(s) \left(\frac{3+2s}{2+2s} \right) = \frac{3}{s}$$

$$\Rightarrow V_{AO}(s) = \frac{6(1+s)}{s(2s+3)} = \frac{3(s+1)}{s(s+\frac{3}{2})}$$

$$= 3 \left(\frac{1}{s+\frac{3}{2}} + \frac{1}{\frac{s}{2}} \right) \times \frac{1}{3}$$

$$= \frac{1}{s+\frac{3}{2}} + \frac{2}{s}$$

$$I_1(s) = \frac{\frac{6}{s} - V_{AO}(s)}{2} = \frac{\frac{6}{s} - \frac{1}{s+\frac{3}{2}} - \frac{2}{s}}{2}$$


$$= \left(\frac{4}{s} - \frac{1}{s+\frac{3}{2}} \right) \times \frac{1}{2}$$

$$\therefore i_1(t) = 2u(t) - \frac{1}{2} e^{-\frac{3}{2}t} u(t)$$

$$I_2(s) = \frac{V_{AO}(s)}{2} = \frac{1}{2} \times \frac{1}{s + \frac{3}{2}} + \frac{1}{s}$$


$$\therefore i_2(t) = \frac{1}{2} e^{-\frac{3t}{2}} u(t) + u(t)$$

QUESTION 11:

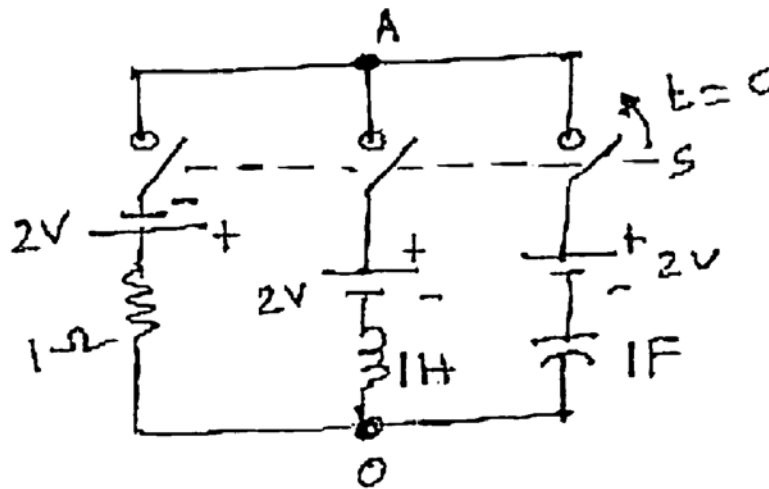

All switches were closed at $t = 0$ together. Before that the capacitor was uncharged.

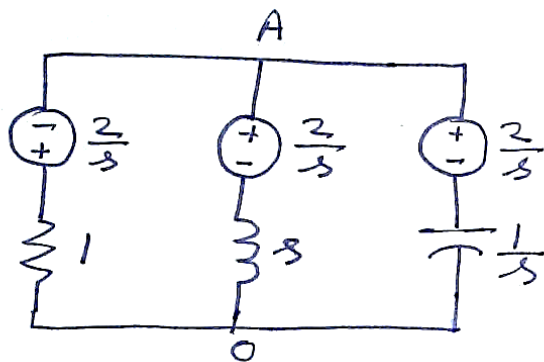Using circuit analysis in Laplace domain, find the expression for the voltage $v_{AO}(t)$ and capacitor voltage $v_c(t)$ for $t \geq 0$.



KCL at A:

$$V_{Ao}(s) \left(\frac{1}{1} + \frac{1}{s} + s \right) = -\frac{2}{s} + \frac{2}{s^2} + \frac{2}{s} \times s$$

$$\Rightarrow V_{Ao}(s) \left(\frac{s^2 + s + 1}{s} \right) = \frac{2(s^2 - s + 1)}{s^2}$$

$$\Rightarrow V_{Ao}(s) = \frac{2(s^2 - s + 1)}{s(s^2 + s + 1)}$$

$$= \frac{2(s^2 + s + 1 - 2s)}{s(s^2 + s + 1)}$$

$$= \frac{2}{s} - \frac{4}{s^2 + s + 1}$$

$$= \frac{2}{s} - \frac{4}{\left(s + \frac{1}{2}\right)^2 + \left(\frac{\sqrt{3}}{2}\right)^2}$$

$$\therefore V_{Ao}(s) = 2u(t) - 4 \times \frac{2}{\sqrt{3}} \sin\left(\frac{\sqrt{3}}{2}t\right) e^{-\frac{t}{2}} u(t)$$

$$= \left(2 - \frac{8}{\sqrt{3}} e^{-t/2} \sin\left(\frac{\sqrt{3}}{2}t\right) \right) u(t)$$

Voltage across the capacitor

$$= V_{Ao}(s) - \frac{2}{s}$$


$$= \frac{2}{s} - \frac{4}{(s + \frac{1}{2})^2 + (\frac{\sqrt{3}}{2})^2} - \frac{2}{s}$$

\therefore Voltage across the capacitor

$$= \left(-4 \times \frac{2}{\sqrt{3}} e^{-t/2} \sin\left(\frac{\sqrt{3}}{2}t\right) \right) u(t)$$

$$= -\frac{8}{\sqrt{3}} e^{-t/2} \sin\left(\frac{\sqrt{3}}{2}t\right) u(t)$$

QUESTION 12:

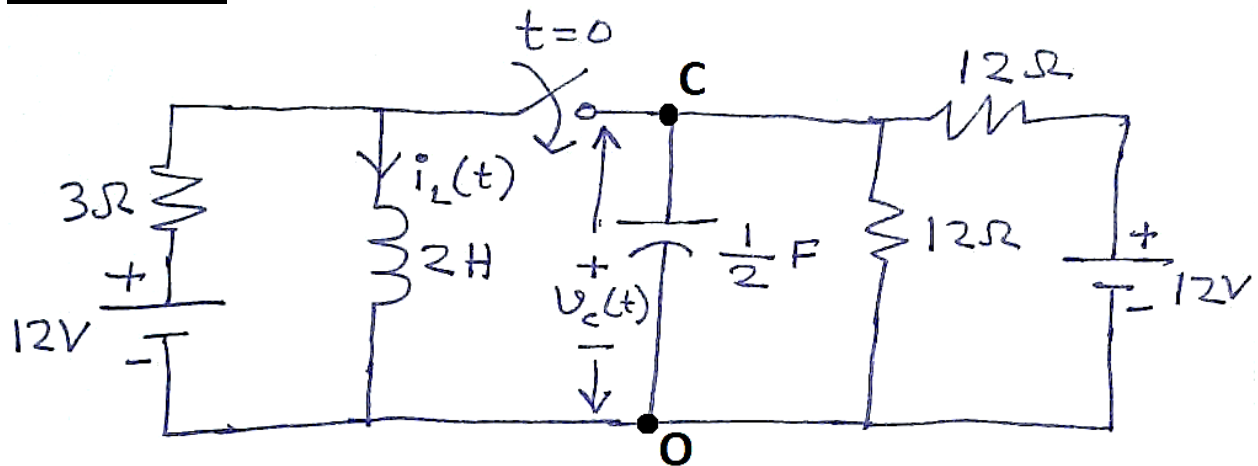

The switch was closed at $t = 0$. Before that the circuit was already in a steady state.


Using circuit analysis in Laplace domain, find the expression for the voltage $v_c(t)$ and current $i_L(t)$ for $t \geq 0$.

(Hint: You may use nodal analysis at node C in Laplace domain for ease of calculation)

Initial inductor current = $\frac{12V}{3\Omega} = 4A$
(top to bottom)

Initial capacitor voltage = $12V \times \frac{12}{12+12} = 6V$
(upside positive)

For $t \geq 0$:

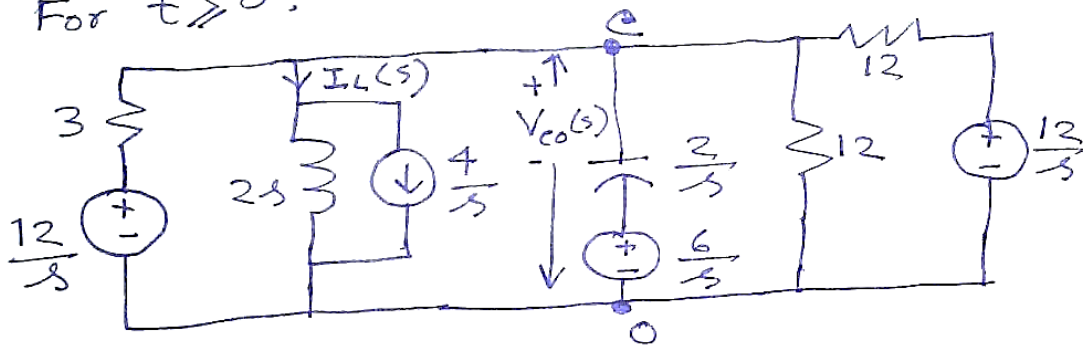

KCL at c:

$$V_{co}(s) \left(\frac{1}{3} + \frac{1}{2s} + \frac{s}{2} + \frac{1}{12} + \frac{1}{12} \right) = \frac{12/s}{3} - \frac{4/s}{s} + \frac{6/s}{2/s} + \frac{12/s}{12}$$

$$\Rightarrow V_{co}(s) \left(\frac{1}{2} + \frac{1}{2s} + \frac{s}{2} \right) = 3 + \frac{1}{s}$$

$$\begin{aligned}
 \Rightarrow V_{co}(s) &= \frac{3s+1}{s} \times \frac{2s}{s^2+s+1} \\
 &= \frac{6s+2}{\left(s+\frac{1}{2}\right)^2 + 1 - \frac{1}{4}} \\
 &= \frac{6s+2}{\left(s+\frac{1}{2}\right)^2 + \left(\frac{\sqrt{3}}{2}\right)^2} \\
 &= \frac{6\left(s+\frac{1}{2}\right) - 1}{\left(s+\frac{1}{2}\right)^2 + \left(\frac{\sqrt{3}}{2}\right)^2}
 \end{aligned}$$

$$\therefore V_{co}(t) = \left(6 e^{-\frac{1}{2}t} \cos\left(\frac{\sqrt{3}}{2}t\right) - \frac{2}{\sqrt{3}} e^{-\frac{1}{2}t} \sin\left(\frac{\sqrt{3}}{2}t\right) \right) u(t)$$

$$= e^{-\frac{1}{2}t} \left(6 \cos\left(\frac{\sqrt{3}}{2}t\right) - \frac{2}{\sqrt{3}} \sin\left(\frac{\sqrt{3}}{2}t\right) \right) u(t)$$

$$\begin{aligned}
 I_L(s) &= \frac{V_{co}(s)}{2s} + \frac{4}{s} \\
 &= \frac{6s+2}{2s(s^2+s+1)} + \frac{4}{s}
 \end{aligned}$$

$$\text{Let } \frac{6s+2}{2s(s^2+s+1)} = \frac{A}{s} + \frac{B+Ds}{s^2+s+1}$$

$$\Rightarrow 3s+1 = A(s^2+s+1) + Bs + Ds^2$$

$$\text{Putting } s=0: A=1$$

$$\text{Putting } s=1: 4=3+B+D \Rightarrow B+D=1$$

$$\text{Putting } s=-1: -2=1-B+D \Rightarrow B-D=3$$

$$\therefore B=2 \text{ and } D=-1$$

$$\begin{aligned}
 \therefore I_L(s) &= \frac{1}{s} + \frac{2-s}{s^2+s+1} + \frac{4}{s} \\
 &= \frac{5}{s} - \frac{s-2}{\left(s+\frac{1}{2}\right)^2 + \left(\frac{\sqrt{3}}{2}\right)^2} \\
 &= \frac{5}{s} - \frac{\left(s+\frac{1}{2}\right) - \frac{5}{2}}{\left(s+\frac{1}{2}\right)^2 + \left(\frac{\sqrt{3}}{2}\right)^2}
 \end{aligned}$$

$$\begin{aligned}
 \therefore i_L(t) &= 5u(t) - \left(e^{-\frac{1}{2}t} \cos\left(\frac{\sqrt{3}}{2}t\right) u(t) - \frac{5}{\sqrt{3}} e^{-\frac{1}{2}t} \sin\left(\frac{\sqrt{3}}{2}t\right) u(t) \right) \\
 &= \left(5 - e^{-\frac{1}{2}t} \cos\left(\frac{\sqrt{3}}{2}t\right) + \frac{5}{\sqrt{3}} e^{-\frac{1}{2}t} \sin\left(\frac{\sqrt{3}}{2}t\right) \right) u(t)
 \end{aligned}$$
