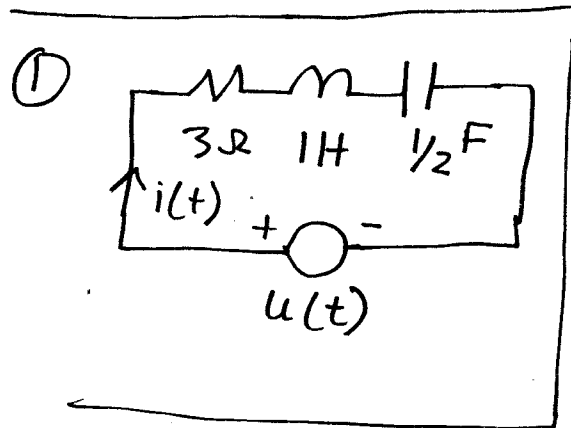


ON DIFFERENTIAL EQUATIONS



$$iR + L \frac{di}{dt} + \int_{-\infty}^t \frac{i(\tau) d\tau}{C} = u(t)$$

$$\Rightarrow R \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{i}{C} = \delta(t)$$

$$\Rightarrow \frac{d^2 i}{dt^2} + 3 \frac{di}{dt} + 2i = \delta(t)$$

$$\Rightarrow \int_{0^-}^{0^+} \frac{d^2 i}{dt^2} dt + 3 \int_{0^-}^{0^+} \frac{di}{dt} dt + 2 \int_{0^-}^{0^+} i dt = 1$$

$$\Rightarrow \frac{di}{dt}(0^+) - \frac{di}{dt}(0^-) + 3 \times 0 + 2 \times 0 = 1$$

$$\Rightarrow \frac{di}{dt}(0^+) = 1 \quad \left[\because \frac{di}{dt}(0^-) = 0 \right]$$

\therefore For $t > 0$

$$\frac{d^2 i}{dt^2} + 3 \frac{di}{dt} + 2i = 0$$

$$\left[\text{with } \frac{di}{dt}(0^+) = 1 \right]$$

and $i(0^+) = i(0^-) = 0$, since

i can not have a step jump at

$t=0$, else $\frac{d^2 i}{dt^2}$ will have a

$\frac{d}{dt} \cdot \delta(t)$ term]

Characteristic equation

$$m^2 + 3m + 2 = 0 \Rightarrow (m+2)(m+1) = 0$$

$$\Rightarrow m = -2, -1$$

$$\therefore i(t) = A e^{-2t} + B e^{-t} \quad \text{for } t > 0$$

$$i(0^+) = 0 = A + B$$

$$\frac{di}{dt}(0^+) = 1 = -2A - B$$

$$\therefore A = -1, \quad B = 1$$

$$\therefore i(t) = (e^{-t} - e^{-2t}) u(t)$$

$$v(t) = \int_{-\infty}^t \frac{1}{s} i(\tau) d\tau = \int_{-\infty}^t 2 (e^{-\tau} - e^{-2\tau}) u(\tau) d\tau$$


$$= 2 \int_0^t (e^{-\tau} - e^{-2\tau}) d\tau$$

$$= 2 \left(\left[e^{-\tau} \right]_t^0 + \frac{1}{2} \left[e^{-2\tau} \right]_0^t \right)$$

$$= 2 - 2e^{-t} + e^{-2t} - 1$$

$$= 1 - 2e^{-t} + e^{-2t}$$

②

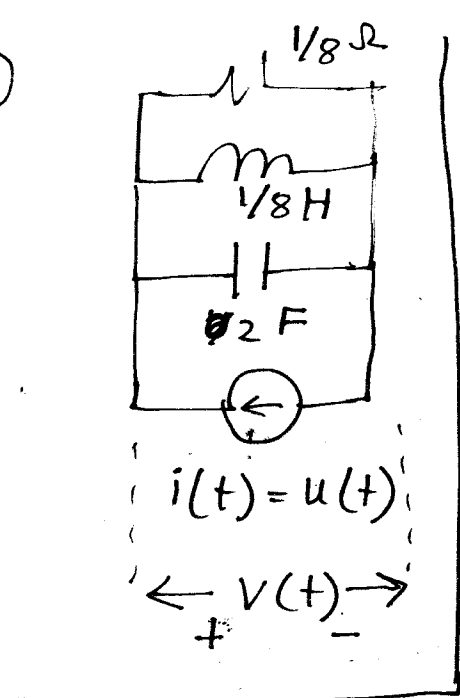

$$\frac{V(t)}{R} + \int_{-\infty}^t \frac{1}{L} V(\tau) d\tau + C \frac{dV}{dt} = u(t)$$

$$\Rightarrow \frac{1}{R} \frac{dV}{dt} + \frac{1}{L} V(t) + C \frac{d^2 V}{dt^2} = \delta(t)$$

$$\Rightarrow 8 \frac{dV}{dt} + 8V + 2 \frac{d^2 V}{dt^2} = \delta(t)$$

$$\Rightarrow \int_{0^-}^{0^+} (2 \frac{d^2 V}{dt^2} + 8 \frac{dV}{dt} + 8V) dt = 1$$

$$\Rightarrow 2 \left(\frac{dV}{dt}(0^+) - \frac{dV}{dt}(0^-) \right) = 1$$

$$\Rightarrow \frac{dV}{dt}(0^+) = \frac{1}{2} \quad [\because \frac{dV}{dt}(0^-) = 0]$$

$$\text{Also } V(0^+) = V(0^-) = 0$$

For $t > 0$

Characteristic equation

$$2m^2 + 8m + 8 = 0$$

$$\Rightarrow m^2 + 2 \times 2m + 2^2 = 0$$

$$\Rightarrow (m+2)^2 = 0$$

$$\Rightarrow m = -2$$

$$\therefore V(t) = (A + Bt)e^{-2t} \quad \text{for } t > 0$$

$$V(0^+) = 0 = A$$

$$\frac{dV}{dt}(0^+) = \frac{1}{2} = -2A + B(1) = B$$

$$\therefore A = 0, B = \frac{1}{2}$$

$$\therefore V(t) = \frac{1}{2} t e^{-2t} u(t)$$

8 Current through inductor

$$\begin{aligned} &= \int_{-\infty}^t \frac{1}{L} V(\tau) d\tau = \int_0^t 8 \times \frac{1}{2} \tau e^{-2\tau} d\tau \\ &= 4 \left[\left[\frac{\tau e^{-2\tau}}{-2} \right]_0^t + \frac{1}{2} \int_0^t e^{-2\tau} d\tau \right] \\ &= 4 \left[\frac{t e^{-2t}}{-2} + \frac{1}{2} \left(-\frac{1}{2} \right) \left[e^{-2\tau} \right]_0^t \right] \\ &= -2 t e^{-2t} - (e^{-2t} - 1) \\ &= 1 - e^{-2t} - 2 t e^{-2t} \end{aligned}$$

$$\textcircled{3} \text{ i) } \int_{0^-}^{0^+} \left(\frac{d^2 y}{dt^2} + 4y \right) dt = \int_{0^-}^{0^+} \delta(t) dt = 1$$

$$\Rightarrow \int_{0^-}^{0^+} \frac{d^2 y}{dt^2} dt + \int_{0^-}^{0^+} 4y dt = 1$$

$$\Rightarrow \frac{dy}{dt}(0^+) - \frac{dy}{dt}(0^-) + 0 = 1$$

$$\Rightarrow \frac{dy}{dt}(0^+) = 1 + \frac{dy}{dt}(0^-) = 2$$

$$y(0^+) = y(0^-) = 2$$

because otherwise if $y(0^+) \neq y(0^-)$ then there will be a step jump in y & a $\delta(t)$ term in $\frac{d^2 y}{dt^2}$, so LHS will have $\delta(t)$, but there is no $\delta(t)$ on RHS.

ii) For $t > 0$

$$\frac{d^2 y}{dt^2} + 4y = 0$$

characteristic equation

$$m^2 + 4 = 0 \Rightarrow m = \pm 2j$$

$$\therefore y(t) = A e^{2jt} + B e^{-2jt} \quad \text{for } t > 0$$

$$\Rightarrow y(0^+) = A + B = 2$$

$$\text{and } \frac{dy}{dt}(0^+) = 2jA - 2jB = 2$$

$$\Rightarrow A - B = -j$$

$$\therefore A = \frac{2-j}{2} \quad \text{and} \quad B = \frac{2+j}{2}$$

$$\therefore y(t) = \frac{(2-j)e^{2jt} + (2+j)e^{-2jt}}{2}$$

$$= 2 \cos(2t) + \sin(2t)$$

$$= \sqrt{5} \left(\frac{2}{\sqrt{5}} \cos(2t) + \frac{1}{\sqrt{5}} \sin(2t) \right)$$

$$= \sqrt{5} \sin(2t + \theta)$$

$$\text{where } \theta = \tan^{-1}(2)$$

$$\therefore \text{For } t > 0 \quad y(t) = \sqrt{5} \sin(2t + \theta)$$

$$(iii) \text{ For } t < 0 \quad \frac{d^2 y}{dt^2} + 4y = 0$$

$$\text{Characteristic equation } m^2 + 4 = 0$$

$$\therefore y(t) = A e^{2jt} + B e^{-2jt}$$

$$y(0^-) = A + B = 2$$

$$\frac{dy}{dt}(0^-) = 2jA - 2jB = 1$$

$$\Rightarrow A - B = -\frac{j}{2}$$


$$\therefore A = \frac{4-j}{4} \quad \text{and} \quad B = \frac{4+j}{4}$$

$$\therefore y(t) = e^{2jt} \left(\frac{4-j}{4} \right) + e^{-2jt} \left(\frac{4+j}{4} \right)$$

$$= 2 \cos 2t - \frac{1}{2} \sin(2t)$$

$$= \frac{\sqrt{17}}{2} \left(\sin(2t + \phi) \right)$$

$$\text{where } \phi = \tan^{-1}(4)$$

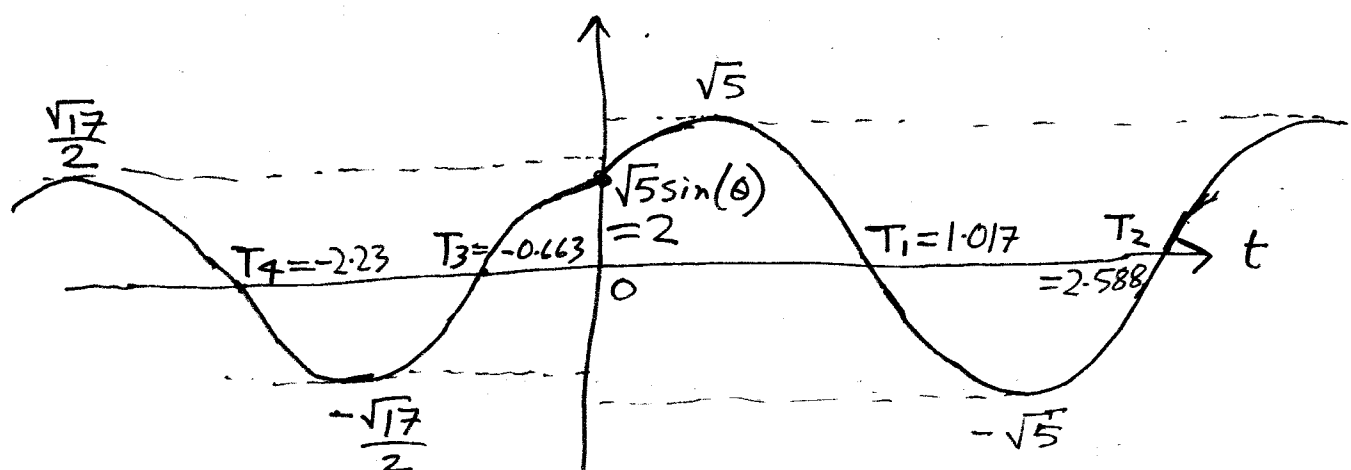

Important time and amplitudes

$$\sqrt{5} \sin \theta = \sqrt{5} \sin(\tan^{-1}(2)) = 2$$

$$\text{Period} = \frac{2\pi}{2} = \pi$$

$$\sin(\tan^{-1}(2) + 2T_1) = 0$$

$$\Rightarrow T_1 = \frac{\pi - \tan^{-1}(2)}{2} = 1.017$$

$$T_2 = 1.017 + \frac{\pi}{2} = ~~4.589~~ 2.588$$

$$\sin(2T_3 + \tan^{-1}(4)) = 0$$

$$\Rightarrow 2T_3 + \tan^{-1}(4) = ~~0~~ 0$$

$$\Rightarrow T_3 = -0.663$$

$$T_4 = -0.663 - \frac{\pi}{2} = -2.23$$

QUESTION 4:

A system is described by the following differential equation $\frac{dy}{dt} + 4y = t$ with boundary condition $y(0) = 2$. Find the solution to this differential equation.

Solution:

Characteristic equation: $m + 4 = 0$

root : $m = -4$

\therefore Natural response : $A e^{-4t}$

$$\begin{aligned}\text{Forced response} &= k_1 t + k_2 \frac{d}{dt}(t) \\ &= k_1 t + k_2\end{aligned}$$

The forced response must satisfy the given differential equation

$$\therefore \frac{d}{dt}(k_1 t + k_2) + 4(k_1 t + k_2) = t$$

$$\Rightarrow k_1 + 4k_1 t + 4k_2 = t$$

$$\Rightarrow 4k_1 = 1 \quad \text{or} \quad k_1 = \frac{1}{4}$$

$$\text{and} \quad k_1 + 4k_2 = 0$$

$$\Rightarrow k_2 = -\frac{k_1}{4} = -\frac{1}{16}$$

$$\therefore y(t) = \text{Forced response} + \text{Natural response}$$

$$= k_1 t + k_2 + A e^{-4t}$$

$$= \frac{1}{4}t - \frac{1}{16} + A e^{-4t}$$

$$\therefore y(0) = 2$$

$$\Rightarrow \frac{1}{4} \times 0 - \frac{1}{16} + A e^0 = 2$$

$$\Rightarrow A = 2 + \frac{1}{16} = \frac{33}{16}$$

$$\therefore y(t) = \frac{1}{4}t - \frac{1}{16} + \frac{33}{16} e^{-4t}$$

QUESTION 5:

A system is described by the following differential equation $\frac{d^2y}{dt^2} + 5\frac{dy}{dt} + 6y = 1 + 2t + 3t^2$ with boundary condition $y(0) = 1$ and $\frac{dy}{dt}(0) = 2$. Find the solution to this differential equation.

Solution:

$$\text{Characteristic equation: } m^2 + 5m + 6 = 0$$

$$\Rightarrow (m+2)(m+3) = 0$$

$$\text{Roots: } m = -2 \text{ and } -3$$

$$\text{Natural response } y_n(t) = A_1 e^{-2t} + A_2 e^{-3t}$$

$$x(t) = 1 + 2t + 3t^2$$

$$\frac{dx}{dt} = 2 + 6t$$

$$\frac{d^2x}{dt^2} = 6$$

$$\frac{d^3x}{dt^3} = 0$$

\therefore Forced response will be of the form

$$k_1 + k_2 t + k_3 t^2$$

$$\text{Now } \frac{d^2 y_f}{dt^2} + 5 \frac{dy_f}{dt} + 6 y_f = 1 + 2t + 3t^2$$

$$\Rightarrow 2k_3 + 5(k_2 + 2k_3 t) + 6(k_1 + k_2 t + k_3 t^2) = 1 + 2t + 3t^2$$

$$\Rightarrow 6k_3 = 3 \Rightarrow k_3 = \frac{1}{2}$$

$$6k_2 + 10k_3 = 2 \Rightarrow k_2 = \frac{2 - \frac{10}{2}}{6} = -\frac{1}{2}$$

$$\text{And } 2k_3 + 5k_2 + 6k_1 = 1$$

$$\Rightarrow k_1 = \frac{1 - 5(-\frac{1}{2}) - 2(\frac{1}{2})}{6} = \frac{5}{12}$$

$$\therefore y_f(t) = \frac{5}{12} - \frac{1}{2}t + \frac{1}{2}t^2$$

$$y(t) = y_f(t) + y_n(t)$$

$$= \frac{5}{12} - \frac{1}{2}t + \frac{1}{2}t^2 + A_1 e^{-2t} + A_2 e^{-3t}$$

$$y(0) = \frac{5}{12} + A_1 + A_2 = 1 \Rightarrow A_1 + A_2 = \frac{7}{12} \dots \textcircled{1}$$

$$\frac{dy}{dt} = -\frac{1}{2} + t - 2A_1 e^{-2t} - 3A_2 e^{-3t}$$

$$\frac{dy}{dt}(0) = -\frac{1}{2} - 2A_1 - 3A_2 = 2$$

$$\Rightarrow 2A_1 + 3A_2 = -\frac{5}{2} \dots \textcircled{2}$$

From $2 \times \textcircled{1} - \textcircled{2}$ we get

$$2A_2 - 3A_2 = \frac{14}{12} + \frac{5}{2} = \frac{44}{12}$$

$$\Rightarrow A_2 = -\frac{44}{12} = -\frac{11}{3}$$

$$\therefore A_1 = \frac{7}{12} - A_2 = \frac{7}{12} + \frac{11}{3} = \frac{51}{12} = \frac{17}{4}$$

$$\therefore y(t) = \frac{17}{4} e^{-2t} - \frac{11}{3} e^{-3t} + \frac{5}{12} - \frac{1}{2}t + \frac{1}{2}t^2$$

QUESTION 6:

A system is described by the following differential equation $\frac{d^2y}{dt^2} + 5\frac{dy}{dt} + 6y = 2e^{-5t}$ with boundary condition $y(0) = 1$ and $\frac{dy}{dt}(0) = 2$. Find the solution to this differential equation.

Solution:

$$\text{Characteristic equation: } m^2 + 5m + 6 = 0$$

$$\Rightarrow (m+2)(m+3) = 0$$

$$\Rightarrow m = -2, -3$$

$$\therefore \text{Natural response: } y_n(t) = A_1 e^{-2t} + A_2 e^{-3t}$$

Forced response:

$$y_f(t) = \frac{2e^{-5t}}{(m^2 + 5m + 6)|_{m=-5}}$$

$$= \frac{2e^{-5t}}{6} = \frac{e^{-5t}}{3}$$

$$\therefore y(t) = y_n(t) + y_f(t)$$

$$= A_1 e^{-2t} + A_2 e^{-3t} + \frac{e^{-5t}}{3}$$

$$y(0) = A_1 + A_2 + \frac{1}{3} = 1$$

$$\Rightarrow A_1 + A_2 = \frac{2}{3} \quad \dots \dots \dots (1)$$

$$\frac{dy}{dt} = -2A_1 e^{-2t} - 3A_2 e^{-3t} - \frac{5}{3} e^{-5t}$$

$$\frac{dy}{dt}(0) = -2A_1 - 3A_2 - \frac{5}{3} = 2$$

$$\Rightarrow 2A_1 + 3A_2 = -\frac{11}{3} \quad \dots \dots \dots (2)$$

From (2) - 2 × (1)

$$A_2 = \frac{-11}{3} - \frac{4}{3} = -5$$

$$\therefore A_1 = 5 + \frac{2}{3} = \frac{17}{3}$$

$$\therefore y(t) = \frac{17}{3} e^{-2t} - 5e^{-3t} + \frac{e^{-5t}}{3}$$

QUESTION 7:

A system is described by the following differential equation $\frac{dy}{dt} + 5y = 2e^{-5t}$ with boundary condition $y(0) =$

1. Find the solution to this differential equation.

Solution:

Here the root of the characteristic equation $= -5 =$ the exponent of the excitation function.

$$\frac{dy}{dt} + 5y = 2e^{-5t}$$

$$\Rightarrow e^{5t} \left(\frac{dy}{dt} + 5y \right) = 2$$

$$\Rightarrow e^{5t} \frac{dy}{dt} + 5e^{5t} y = 2$$

$$\Rightarrow \frac{d}{dt} (e^{5t} y) = 2$$


$$\Rightarrow e^{5t} y = 2t + A$$

$$\Rightarrow y = 2te^{-5t} + Ae^{-5t}$$
$$= (2t + A)e^{-5t}$$

$$\therefore y(0) = A = 1$$

$$\therefore y(t) = (2t + 1)e^{-5t}$$

QUESTION 8:

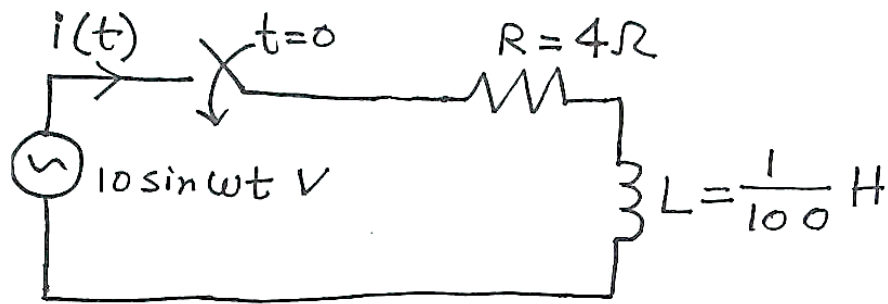

Find the expression of current $i(t)$ for $t > 0$ if the switch is closed at $t = 0$ and $\omega = 300$ radian/sec.

Solution:

$$L \frac{di}{dt} + Ri = 10 \sin \omega t$$

$$\Rightarrow \frac{di}{dt} + \frac{R}{L} i = \frac{10}{L} \sin \omega t$$

$$\Rightarrow \frac{di}{dt} + 400 i = 1000 \sin \omega t$$

Characteristic root: $m = -400$

Natural response: $y_n(t) = A e^{-400t}$

$$x(t) = 1000 \sin \omega t$$

$$\frac{dx}{dt} = 1000 \omega \cos \omega t$$

$$\frac{d^2x}{dt^2} = -1000 \omega^2 \sin \omega t$$

\vdots

\therefore Forced response

$$y_f(t) = k_1 \sin \omega t + k_2 \cos \omega t$$

$$\text{Now } \frac{d y_f}{dt} + 400 y_f = 1000 \sin \omega t$$

$$\Rightarrow (k_1 \omega \cos \omega t - k_2 \omega \sin \omega t) + 400(k_1 \sin \omega t + k_2 \cos \omega t) = 1000 \sin \omega t$$

$$\therefore k_1 \omega + 400 k_2 = 0$$

$$\text{or } 300 k_1 + 400 k_2 = 0 \quad [\because \omega = 300]$$

$$\text{and } -k_2 \omega + 400 k_1 = 1000$$

$$\text{or } 400 k_1 - 300 k_2 = 1000$$

So we have

$$3k_1 + 4k_2 = 0 \quad \text{--- (1)}$$

$$\text{and } 4k_1 - 3k_2 = 10 \quad \text{--- (2)}$$

From $3 \times (1) + 4 \times (2)$ we get

$$25k_1 = 40 \Rightarrow k_1 = \frac{8}{5}$$

$$\therefore k_2 = -\frac{3k_1}{4} = -\frac{6}{5}$$

$$\begin{aligned} \therefore i(t) &= y_n(t) + y_f(t) \\ &= A e^{-400t} + \frac{8}{5} \sin \omega t \\ &\quad - \frac{6}{5} \cos \omega t \end{aligned}$$

$$\therefore i(0) = A - \frac{6}{5} = 0 \Rightarrow A = \frac{6}{5}$$

$$\therefore i(t) = \frac{6}{5} e^{-400t} + \frac{8}{5} \sin \omega t - \frac{6}{5} \cos \omega t$$

$$= \frac{6}{5} e^{-400t} + \frac{10}{5} \left(\frac{8}{10} \sin \omega t - \frac{6}{10} \cos \omega t \right)$$


$$= \frac{6}{5} e^{-400t} + 2 \sin(\omega t - \phi)$$

$$\text{with } \phi = \tan^{-1} \frac{6}{8}$$

$$= \tan^{-1} \frac{3}{4}$$

$$\therefore i(t) = \frac{6}{5} e^{-400t} + 2 \sin\left(\omega t - \tan^{-1} \frac{3}{4}\right)$$

$$= \frac{6}{5} e^{-400t} + 2 \sin\left(300t - \tan^{-1} \frac{3}{4}\right)$$

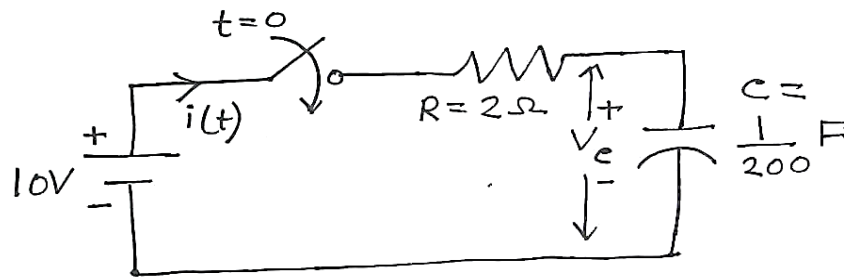QUESTION 9:

Find the expression of current $i(t)$ for $t > 0$ if the switch is closed at $t = 0$. The capacitor was initially uncharged.

Solution:

$$V_c(t) + Ri(t) = 10$$

$$\Rightarrow V_c(t) + R \left(C \frac{dV_c}{dt} \right) = 10$$

$$\Rightarrow \frac{dV_c}{dt} + \frac{1}{RC} V_c = \frac{10}{RC}$$

$$\Rightarrow \frac{dV_c}{dt} + 100 V_c = 1000$$

Forced response : $y_f(t) = k$

Now $\frac{dy_f(t)}{dt} + 100 y_f(t) = 1000$

$$\Rightarrow 0 + 100k = 1000$$

$$\Rightarrow k = 10$$

characteristic root : $m = -100$

\therefore Natural response : $y_n(t) = Ae^{-100t}$


$$\begin{aligned} \therefore V_c(t) &= y_n(t) + y_f(t) \\ &= Ae^{-100t} + k \\ &= Ae^{-100t} + 10 \end{aligned}$$

$$V_c(0) = A + 10 = 0 \Rightarrow A = -10$$

$$\therefore V_c(t) = 10 - 10e^{-100t} = 10(1 - e^{-100t})$$

$$\therefore i(t) = C \frac{dV_c}{dt} = \frac{1}{200} \frac{d}{dt} (10(1 - e^{-100t}))$$

$$= \frac{10}{200} \times 100 e^{-100t} = 5e^{-100t}$$

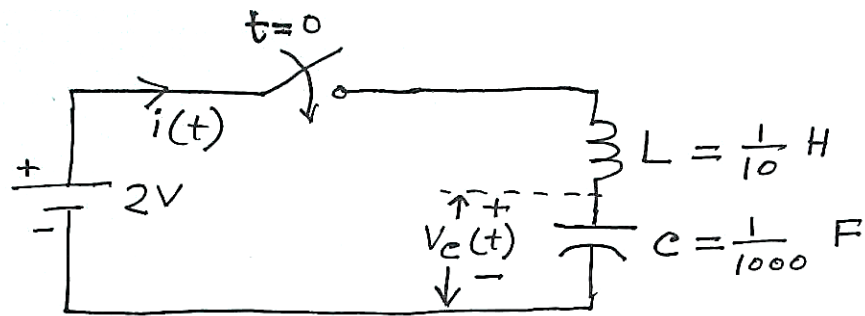QUESTION 10:

Find the expression of capacitor voltage $v_c(t)$ for $t > 0$ if the switch is closed at $t = 0$. The capacitor was initially uncharged.

Solution:

$$v_c(t) + L \frac{di}{dt} = 2$$

$$\Rightarrow v_c(t) + L \frac{d}{dt} \left(C \frac{dv_c}{dt} \right) = 2$$

$$\Rightarrow LC \frac{d^2 v_c}{dt^2} + v_c(t) = 2$$

$$\Rightarrow \frac{1}{10000} \frac{d^2 v_c}{dt^2} + v_c(t) = 2$$

$$\Rightarrow \frac{d^2 v_c}{dt^2} + 10000 v_c(t) = 20000$$

Characteristic equation:

$$m^2 + 10000 = 0$$

$$\Rightarrow m = \pm 100 j$$

$$[j = \sqrt{-1}]$$

\therefore Natural response

$$y_n(t) = A_1 e^{j100t} + A_2 e^{-j100t}$$

Forced response

$$y_f(t) = K$$

$$\text{Now } \frac{d^2 y_f(t)}{dt^2} + 10000 y_f = 20000$$

$$\Rightarrow 0 + 10000K = 20000$$

$$\Rightarrow K = 2$$

$$\begin{aligned} \therefore V_c(t) &= y_f(t) + y_n(t) \\ &= 2 + A_1 e^{j100t} + A_2 e^{-j100t} \end{aligned}$$

$$V_c(0) = 2 + A_1 + A_2 = 0$$

$$\Rightarrow A_1 + A_2 = -2$$

$$i(0) = 0 \Rightarrow \frac{dV_c(0)}{dt} = 0$$

$$\Rightarrow 100jA_1 - 100jA_2 = 0$$

$$\Rightarrow A_1 = A_2$$


$$\therefore A_1 = A_2 = -1$$

$$\therefore V_c(t) = 2 - (e^{j100t} + e^{-j100t})$$

$$= 2 - 2\cos 100t$$

$$= 2(1 - \cos 100t)$$

QUESTION 11:

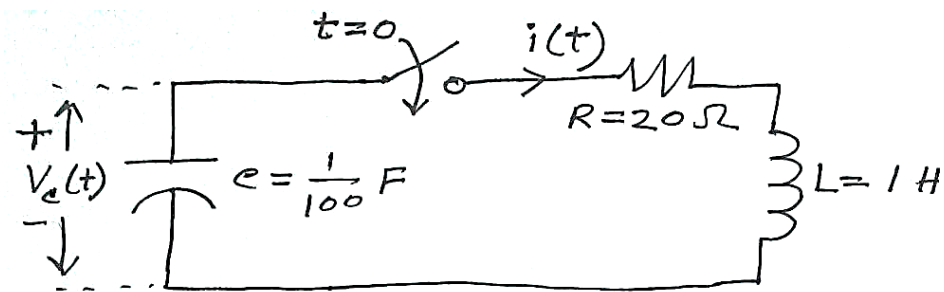

Find the expression of current $i(t)$ for $t > 0$ if the switch is closed at $t = 0$. The initial capacitor voltage $v_c(0) = 1 \text{ V}$.

Solution:

$$\begin{aligned} v_c(t) &= i(t)R + L \frac{di}{dt} \\ &= R \left(-C \frac{dv_c}{dt} \right) + L \frac{d}{dt} \left(-C \frac{dv_c}{dt} \right) \\ &= -RC \frac{dv_c}{dt} - LC \frac{d^2 v_c}{dt^2} \end{aligned}$$

$$\Rightarrow LC \frac{d^2 v_c}{dt^2} + RC \frac{dv_c}{dt} + v_c = 0$$

$$\Rightarrow \frac{d^2 v_c}{dt^2} + \frac{R}{L} \frac{dv_c}{dt} + \frac{1}{LC} v_c = 0$$

$$\Rightarrow \frac{d^2 v_c}{dt^2} + 20 \frac{dv_c}{dt} + \frac{100}{1} = 0$$

Forced response will be zero

Characteristic equation:

$$m^2 + 20m + 100 = 0$$

$$\Rightarrow (m + 10)^2 = 0$$

$$\Rightarrow m = -10 \text{ (repeated roots)}$$

\therefore Natural response $y_n(t)$

$$= (A_1 + A_2 t) e^{-10t}$$

$$\therefore V_c(t) = (A_1 + A_2 t) e^{-10t}$$

$$V_c(0) = A_1 = 1$$

$$i(0) = -C \frac{dV_c(0)}{dt} = 0$$

$$\Rightarrow \frac{-1}{100} \left(A_2 e^{-10t} + (A_1 + A_2 t) \times (-10) e^{-10t} \right) \Big|_{t=0} = 0$$

$$\Rightarrow A_2 + (A_1)(-10) = 0$$

$$\Rightarrow A_2 = 10 A_1 = 10$$

$$\therefore V_c(t) = (1 + 10t) e^{-10t}$$


$$i(t) = -C \frac{dV_c}{dt}$$

$$= \frac{-1}{100} \times \left(10 e^{-10t} + (-10)(1+10t) e^{-10t} \right)$$

$$= \frac{-1}{100} \left(-100t e^{-10t} \right)$$


$$= t e^{-10t}$$

Question 12

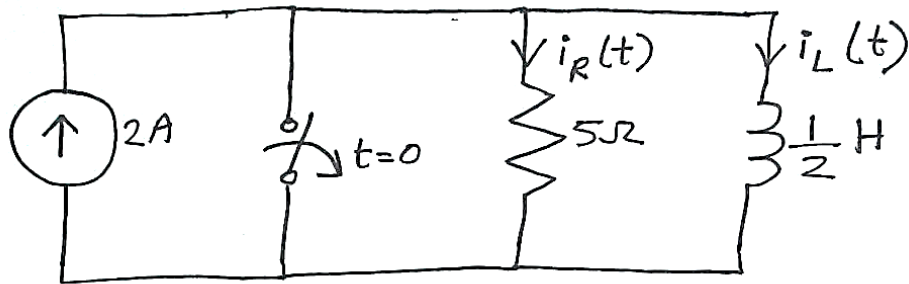

Find the expression of currents $i_R(t)$ and $i_L(t)$ for $t > 0$ if the switch is **opened (disconnected)** at $t = 0$ and the initial current through the inductor was zero.

Solution:

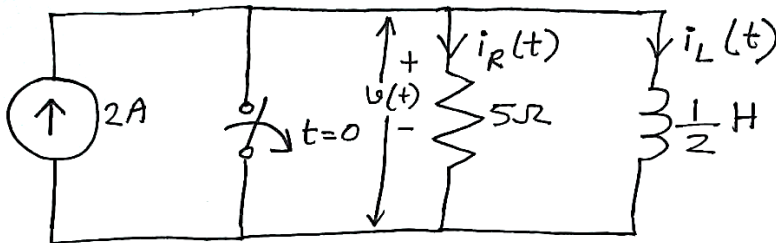

$$i_R(t) + i_L(t) = 2 \quad \text{for } t \geq 0$$

$$\Rightarrow \frac{v(t)}{R} + i_L = 2$$

$$\Rightarrow \frac{L \frac{di_L}{dt}}{R} + i_L = 2$$

$$\Rightarrow \frac{di_L}{dt} + \frac{R}{L} i_L = 2 \frac{R}{L}$$

$$\Rightarrow \frac{di_L}{dt} + 10 i_L = 20$$

$$\text{Forced response } y_f = \frac{20}{10} = 2$$

$$\text{Natural response } y_n = A e^{-10t}$$

$$\therefore i_L = 2 + A e^{-10t}$$

$$i_L(0) = 2 + A = 0 \Rightarrow A = -2$$

$$\therefore i_L(t) = 2 - 2 e^{-10t}$$

$$i_R(t) = 2 - i_L(t) = 2 e^{-10t}$$