

$$(2) \quad R_1 = R_2 = 10 \text{ k}\Omega, \quad C_1 = C_2 = 1 \text{ nF}, \quad Q = 1$$

$$\Rightarrow Q = \frac{1}{3-K} = 1 \Rightarrow K=2 \Rightarrow 1 + \frac{R_b}{R} = 2 \Rightarrow \frac{R_b}{R} = 1$$

Hence, we can choose $R = R_b = 1 \text{ k}\Omega$.

$$\Rightarrow f_0 = \frac{1}{2\pi\sqrt{C_1 R C_2 R_2}} \text{ Hz} = \frac{1}{2\pi \times 10^{-9} \times 10^{-9}} \text{ Hz} = \frac{10^5}{2\pi} \text{ Hz} = 15915 \text{ Hz}$$

Experimentally the peak in gain is obtained around 11.3 kHz. The peak is not very sharp though owing to the low Q-factor. The transition is not very sharp.

(4) $R_1 = R_2 = 10k\Omega$, $C_1 = C_2 = 1\mu F$, $Q = 2.5$

NISARG UPADHYAYA
19CS30031 Nimg.

$$\Rightarrow Q = \frac{1}{3-K} = \frac{5}{2} \Rightarrow K = \frac{13}{5} \Rightarrow 1 + \frac{R_F}{R} = \frac{13}{5} \Rightarrow \frac{R_F}{R} = \frac{8}{5}$$

Hence we can choose $R_F = 2k\Omega$ and $R = 1.25k\Omega$

$$\Rightarrow f_0 = \frac{1}{2\pi\sqrt{R_F R C_2}} \text{ Hz} = \frac{1}{2\pi RC} \text{ Hz} = \frac{10^8}{2\pi} \text{ Hz} = 15915 \text{ KHz}$$

Experimentally the gain starts to drop around 150 KHz and reaches -3dB value near 300 KHz. The huge difference between theoretical and experimental value stems from the fact that the op-amp used (OP-777) has a finite bandwidth. (non ideal) Moreover this bandwidth is much lesser (for the OP-AMP used) than 15915 KHz. Due to this the OP-AMP deviates from its ideal behaviour. It can be observed by using a different OP-AMP such as LT-1226 the roll-off occurs near the expected value.