

## • Instructions

- **Answer all questions (Question no. 1 to 3). Answers must be brief and to the point.**
- **Avoid writing answers of the various parts of a single question at different locations in your answer-script. For every Question No., start your answer from a new page. Symbols/notations used in the Question paper represent their conventional meanings.**
- **The final answers (numerical values with unit) should be underlined or enclosed box within with unit.**
- **Show the necessary steps in your answers with high clarity and supported explanation.**
- **All waveform sketches / diagrams must be neatly drawn and clearly labelled.**
- **For any value related to any device parameter or circuit parameter, which you may find not given with a problem, assume suitable value for such parameter and clearly write your assumptions.**

1. In the bridge-rectifier circuit with filter capacitor as shown in Fig. 1,  $V_f$  of each diode is 0.7 V and the load resistance (R) is 100  $\Omega$ . The transformer secondary is delivering a sinusoidal signal of 60 Hz of magnitude 12 V (RMS). (a) Find the value of capacitance (C) such that the peak-to-peak ripple voltage becomes 1 V. (b) In this case, what is the DC value of  $V_{out}$ ? (c) Estimate the maximum current through 'R'. (d) What is PIV of each diode? (e) For a complete sine wave (one time-period) of input, calculate the time duration (in Sec) when a diode conducts.

[2+2+2+2+2 = 10]

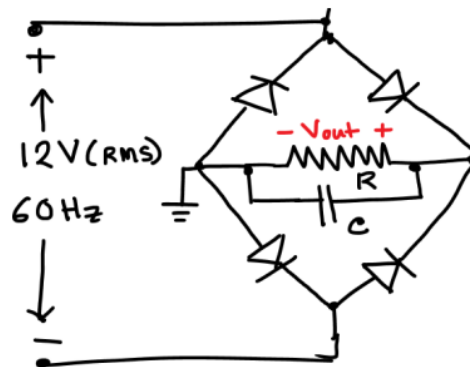


Figure 1

2. Consider the following amplifier circuit (Fig. 2) using a npn BJT. Given that  $\beta = 150$ ,  $V_{BE\_ON} = 0.7$  V and Early voltage is very high for this transistor. Magnitude of other circuit parameters are indicated in the figure. (a) Estimate the value of emitter current ( $I_E$ ) and voltage  $V_C$ . (b) Neatly draw the complete small signal equivalent circuit and find the magnitude  $r_\pi$  and  $g_m$ . (c) Find the small signal voltage gain ( $A_v$ ) of the amplifier. (d) What will happen to the  $A_v$  if you reduce the magnitude of  $C_2$  from 100  $\mu$ F to 10 nF. (your comment + justification) (e) If  $V_s = 10 \sin(\omega t)$  mV, then neatly draw the waveform of output voltage ( $V_{out}$ ) along with the waveform of signal source ( $V_s$ ) in a single plot. Clearly indicate the voltage level in the Y-axis. (f) Find  $V_x$  (total voltage at this node).

[(1+1)+(1+1+1)+2+1+1+1 = 10]

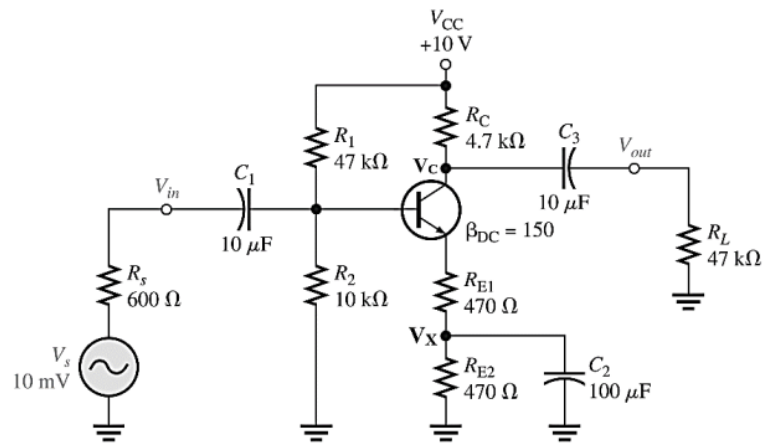


Figure 2

3. In the following circuit (Figure 3) given that  $V_{Thn} = 1\text{ V}$ ,  $V_{GS} = 2\text{ V}$ ,  $k'_n = 2\text{ mA/V}^2$ . (a) Find the value of node voltage  $V_D$  and  $(W/L)$  ratio of the MOSFET. (b) Draw the small signal AC equivalent circuit and calculate the voltage gain. For this part, consider  $\lambda = 0.01\text{ V}^{-1}$ . (c) Estimate the small-signal voltage gain if the capacitor  $C_s$  is removed from the circuit. Consider  $\lambda = 0$  for this part and use suitable approximation for estimating the gain. (d) In the circuit shown in Fig. 3, if the magnitude of  $C_1$  is reduced drastically, then comment on the small-signal voltage gain of the amplifier (compare the gain with that of part (b)). [(2+2)+ (1+2)+ 2+1) = 10]

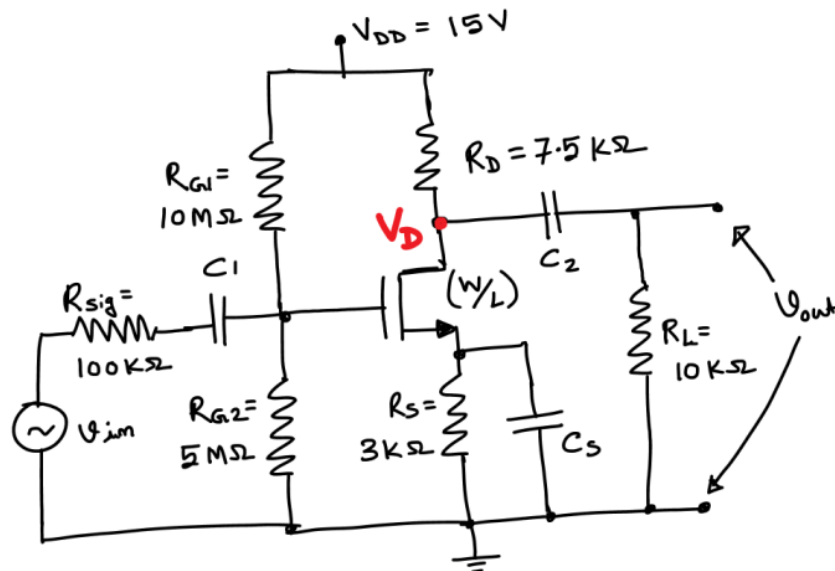


Figure 3

Upload your Soft-copy using the Google Form.

For Back-up, please send the same by email to

[intro2electtheory@gmail.com](mailto:intro2electtheory@gmail.com)