

Report 5 Template (The report must be completely hand written following this template)

Negative impedance convertor

[Draw a circuit diagram of a negative capacitor here]

.....
Observation table

Frequency (vary from 100 Hz to 10k Hz)	Applied voltage magnitude (V)	Current magnitude (A)	Phase of current w.r.t the voltage (degree leading or lagging)	Calculated complex impedance (Ω)

Plot on a graph paper: (a) how the magnitude of the impedance varies with frequency, (b) how the angle of the impedance varies with frequency

Comment whether you can create an inductor using a capacitor (or vice-versa) using this negative impedance convertor

Full Signature with Pen _____

Gyrator

[Draw a gyrator here]

.....

From the two-port network representation of a gyrator, derive how an inductor can be simulated using a capacitor

Observation table

Frequency (vary from 100 Hz to 10k Hz)	Applied voltage magnitude (V)	Current magnitude (A)	Phase of current w.r.t the voltage (degree leading or lagging)	Calculated complex impedance (Ω)

Plot on a graph paper: (a) how the magnitude of the impedance varies with frequency, (b) how the angle of the impedance varies with frequency

Full Signature with Pen _____