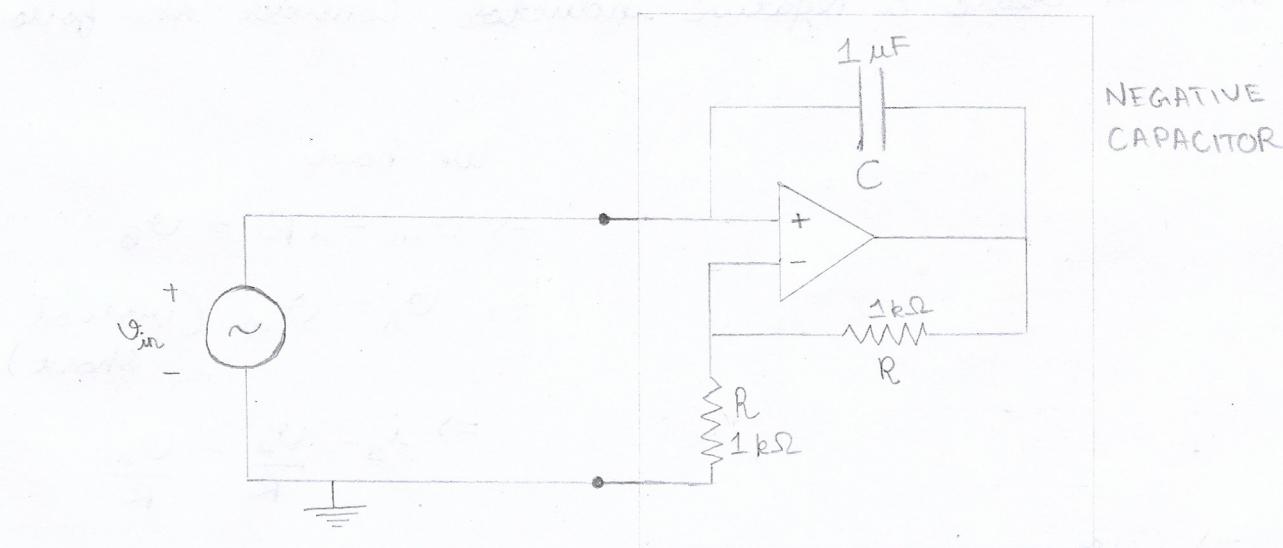


EXPERIMENT 5

## ① NEGATIVE IMPEDANCE CONVERTOR

OBSERVATION TABLE ( $C = 1\mu\text{F}$ )

Frequency (Hz)	Applied voltage (V)	Current magnitude	Phase of current w.r.t the voltage (degrees)	Calculated complex impedance (Ω)
100	5	$3.14 \times 10^3$	-90	$1592.36j$
200	5	$6.28 \times 10^3$	-90	$796.18j$
300	5	$9.42 \times 10^3$	-90	$530.79j$
400	5	$1.26 \times 10^4$	-90	$396.83j$
500	5	$1.57 \times 10^4$	-90	$318.47j$
1000	5	$3.14 \times 10^2$	-90	$159.24j$
2000	5	$6.28 \times 10^2$	-90	$79.62j$
3500	5	$1.10 \times 10^3$	-90	$45.45j$
5000	5	$1.57 \times 10^3$	-90	$31.85j$
6500	5	$2.04 \times 10^3$	-90	$24.51j$
8000	5	$2.51 \times 10^3$	-90	$19.92j$
10000	5	$3.14 \times 10^3$	-90	$15.92j$

(2)



19CS30031

## VARIATION OF CAPACITANCE (INDUCTANCE)

SCALE

DC-current: 1 unit = 0.5 A

Y-axis: 1 unit = 1000  $\mu\text{H}$ INDUCTANCE (MAGNETIC) ( $\mu\text{H}$ )INDUCTANCE ( $\mu\text{H}$ )1700  
1600  
1500  
1400  
1300  
12001100  
1000  
900  
800  
700  
600  
500  
400  
300  
200  
100

0 0.5 1 1.5 2 2.5 3 3.5 4 4.5 5 5.5 6 6.5 7 7.5 8 8.5 9 9.5 10 10.5 11

Ampere

(3)

### VARIATION OF IMPEDANCE (ANGLE)

IMPEDANCE ( $\angle \theta$ )

(LOGM FREQUENCY)

19CS30031

SCALE

X-axis : 1 unit = 0.5 k $\Omega$

Y-axis : 1 unit =  $10^{\circ}$

IMPEDANCE (ANGLE) ( $\text{in degree}$ )

10 20 30 40 50 60 70 80 90 100 110 120 130 140 150 160


$\downarrow$   
Degree.

0 0.5 1 1.5 2 2.5 3 3.5 4 4.5 5 5.5 6 6.5 7 7.5 8 8.5 9 9.5 10 10.5 11 12

FREQUENCY (k Hz)

It is indeed possible to create an inductor using a capacitor using this negative impedance converter with some slight modifications.

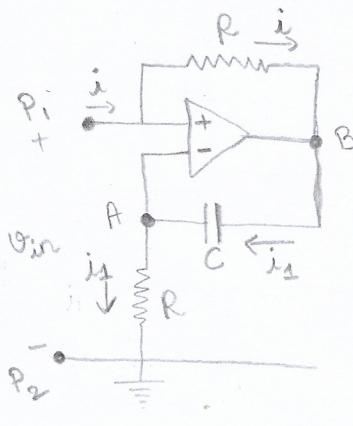First, we will create a negative inductor. Consider the following circuit:



$$\Rightarrow V_A + \frac{i_1}{Cs} = V_B$$

$$\Rightarrow V_{in} + \frac{V_{in}}{Rcs} = V_{in} - iR$$

$$\Rightarrow \frac{V_{in}}{i} = Z_{in} = -\underline{\underline{R^2 Cs}}$$

We have


$$\Rightarrow V_{in} - iR = V_B$$

$$\Rightarrow V_A = V_{in} \text{ (virtual short)}$$


$$\Rightarrow i_1 = \frac{V_A}{R} = \frac{V_{in}}{R}$$

If we take  $R^2 C = L$   
then  $Z_{in} = -Ls$   
which is nothing  
but a negative  
inductor.

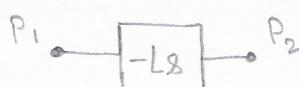We can assume the above to be a two terminal network



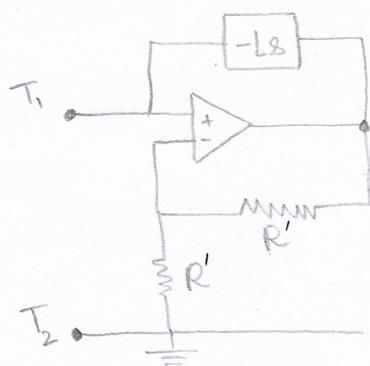
Now using our initial negative impedance converter we can change this to a positive inductor.



Now, the following network between  $T_1$  &  $T_2$  behaves as a positive inductor with inductance


$$\underline{\underline{L = R^2 C}}$$

## ② GYRATOR

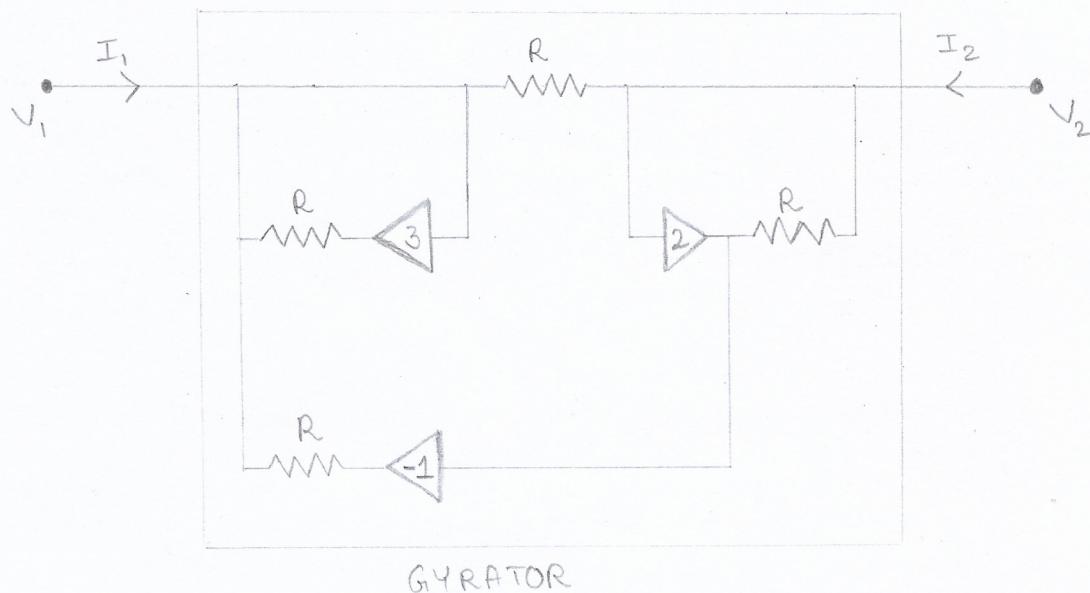

SIMULATING INDUCTOR USING A CAPACITOR

$$\text{GYRATION RESISTANCE} = R$$

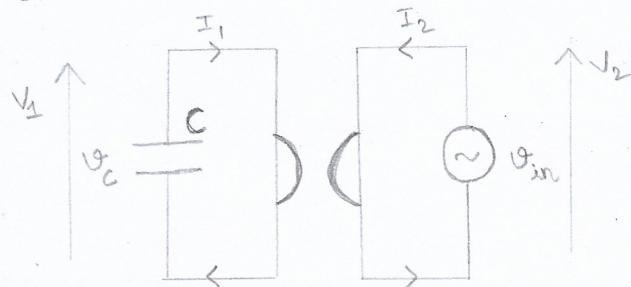

For a gyrator we can write  $v_2 = RI_1$  and  $v_1 = -RI_2$

$$\text{Now } v_2 = v_{in} \text{ and } v_1 = v_C = \frac{-I_1}{Cs}$$

$$\text{Hence } v_1 = -RI_2 = \frac{-I_1}{Cs} \Rightarrow I_1 = Rcs I_2$$

$$\Rightarrow v_2 = v_{in} = RI_1 = R^2 C s I_2$$

$$\Rightarrow Z_{in} = \frac{v_{in}}{I_2} = R^2 C s$$

If we take  $R^2 C = L$  then  $Z_{in}$  can be treated as an inductor, whose inductance  $L = R^2 C$ .

OBSERVATION TABLE ( $C = 1 \mu F$ ,  $R = 1 k\Omega$ )

Frequency (Hz)	Applied voltage magnitude (V)	Current magnitude (A)	Phase of current w.r.t the voltage (degrees)	Calculated complex impedance ( $\Omega$ )
100	5	$7.96 \times 10^{-3}$	-90	$628.14 j$
500	5	$1.59 \times 10^{-3}$	-90	$3144.65 j$
1000	5	$7.96 \times 10^{-4}$	-90	$6281.41 j$
2000	5	$3.98 \times 10^{-4}$	-90	$12562.81 j$
3000	5	$2.65 \times 10^{-4}$	-90	$18867.92 j$
4000	5	$1.99 \times 10^{-4}$	-90	$25125.63 j$
5000	5	$1.59 \times 10^{-4}$	-90	$31446.54 j$
6000	5	$1.33 \times 10^{-4}$	-90	$37593.98 j$
7000	5	$1.14 \times 10^{-4}$	-90	$43859.65 j$
8000	5	$9.95 \times 10^{-5}$	-90	$50251.26 j$
9000	5	$8.84 \times 10^{-5}$	-90	$56561.09 j$
10000	5	$7.96 \times 10^{-5}$	-90	$62814.07 j$

(6)

Wavelength

Frequency (kHz)



26

7

19CS30031

SOURCE

Y-axis: Load: 0.5 kohm

Y-axis: Load: 4 kohm

VARIATION OF IMPEDANCE (MAGNITUDE)

(a) 25.4 FREQUENCY

NISARG  
UPHARNA 68  
64

(8)

## VARIATION OF IMPEDANCE (ANGLE)

NISARG  
UPADHYAYA

(b) X-T-T FREQUENCY

19CCS30031

SCHE

$$\text{X-axis} : I_{\text{max}} = 0.5 \text{ kVA}$$

$$Y-axis : I_{\text{max}} = 1.0$$

IMPEDANCE (ANGLE) (in degree)

60

50

40

30

20

10

0

10

20

30

40

50

60

70

80

90

0 0.5 1 1.5 2 2.5 3 3.5 4 4.5 5 5.5 6 6.5 7 7.5 8 8.5 9 9.5 10 10.5 11

FREQUENCY (kHz)

Wavy.