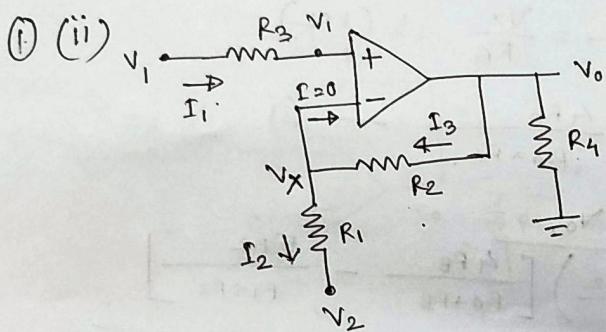


$$\frac{V_A - V_B}{R_1} = \frac{V_B - V_o}{R_2}; \quad (\text{as } I_1 = I_2)$$

$$V_o = \left(1 + \frac{R_2}{R_1} \right) V_B - \frac{R_2}{R_1} V_A$$



as, $I_1 = I_2 = 0.$
 $V_x = V_1$ (virtual short).


$$I_2 = I_3$$

$$\therefore \frac{V_x - V_2}{R_1} = \frac{V_o - V_x}{R_2}$$

$$\therefore V_o = \frac{V_x R_2 - V_2 R_2 + V_x R_1}{R_1}$$

$$\therefore V_o = \left(1 + \frac{R_2}{R_1} \right) V_1 - \frac{R_2}{R_1} V_2$$


(4V) virtual short.

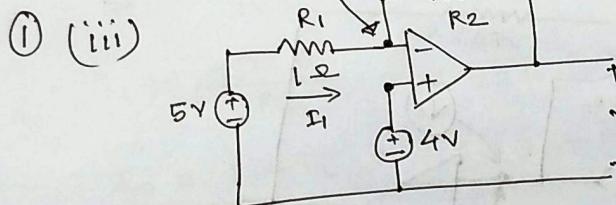

as, $\Rightarrow I_1 = I_2.$

$$\therefore \frac{5-4}{1} = \frac{4-V_o}{4}$$

$$\therefore V_o = 0.$$

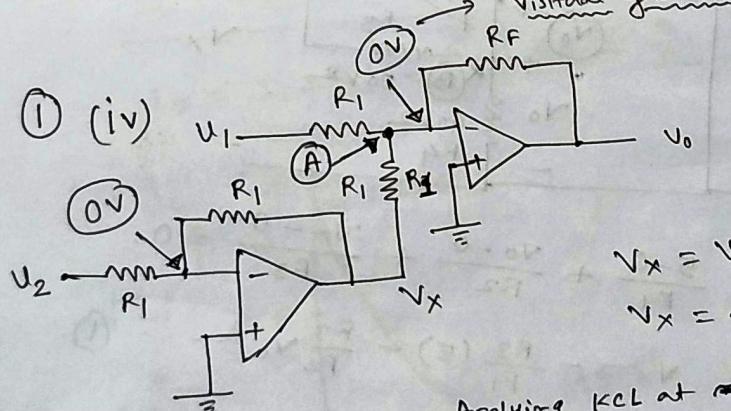

$$V_x = V_2 \times \left(-\frac{R_1}{R_1} \right)$$


$$V_x = -V_2$$

Applying KCL at mode A,

$$\frac{V_1 - 0}{R_1} + \frac{V_x - 0}{R_1} = \frac{0 - V_o}{R_F}$$

$$\therefore V_o = -\frac{R_F}{R_1} (V_1 - V_2)$$

(1) (v)

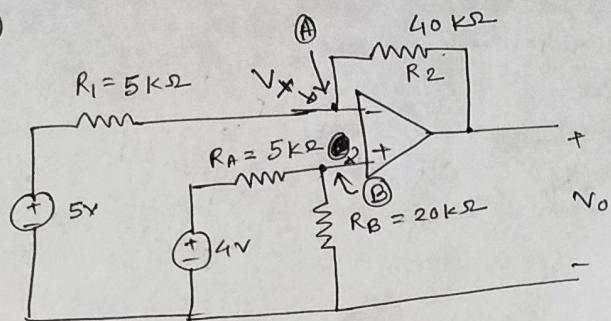

Let potential at mode A
= V_x
So, potential at mode B
= V_x (virtual short).

$$\text{At, mode (A)}, \frac{5 - V_x}{R_1} = \frac{V_x - V_o}{R_2} \quad (\text{kcl})$$

$$\therefore V_x = \left(\frac{R_2}{R_1 + R_2} \right) \cdot 5 + \left(\frac{R_1}{R_1 + R_2} \right) V_o \quad \text{--- (1)}$$

$$\text{At, mode (B)}, \frac{4 - V_x}{R_A} = \frac{V_x}{R_B} \quad ; \quad (\text{kcl})$$


$$\therefore V_x = \frac{4 R_B}{R_A + R_B} \quad \text{--- (2)}$$

From, (1) & (2), Find V_o .

$$V_o = \left(\frac{R_1 + R_2}{R_1} \right) \left[\frac{4 R_B}{R_A + R_B} - \frac{5 R_2}{R_1 + R_2} \right]$$

$$\underline{\underline{V_o = -11.2 \text{ V.}}} \quad (\text{value}).$$

(1) (vi)

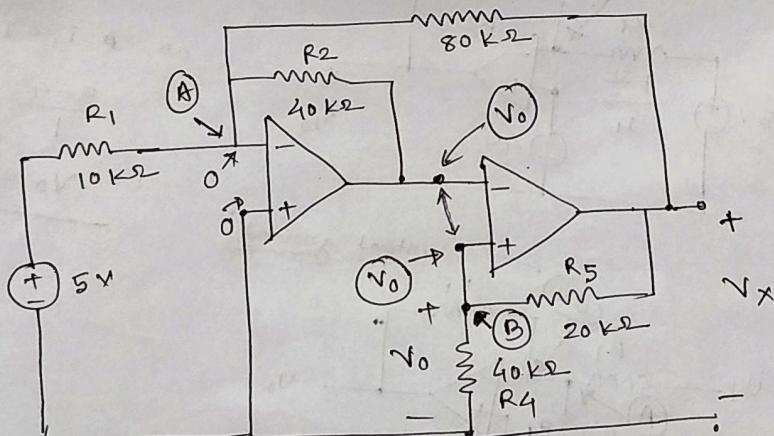

$$\text{At mode (A)}, \frac{5 - 0}{R_1} + \frac{V_o - 0}{R_2} + \frac{V_x - 0}{R_3} = 0.$$

$$\therefore V_x = -\frac{R_3}{R_1} (5) - \frac{R_3}{R_2} V_o \quad \text{--- (1)}$$


$$\text{At mode (B)}, \frac{V_o}{R_4} + \frac{V_o - V_x}{R_5} = 0.$$

$$V_x = V_o \left(1 + \frac{R_5}{R_4} \right) \quad \text{--- (2)}$$

From (1) and (2), find V_o .

$$\underline{\underline{V_o = -11.43 \text{ V.}}}$$

(2)

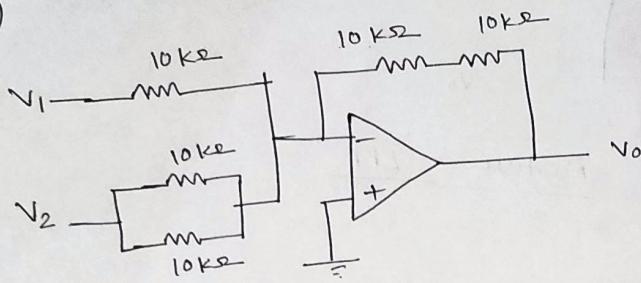


$$V_0 = -20 \left(\frac{V_1}{10} + \frac{V_2}{10} \right)$$

$$V_0 = -2V_1 - 4V_2$$

(Small correction in the question.)

(3)

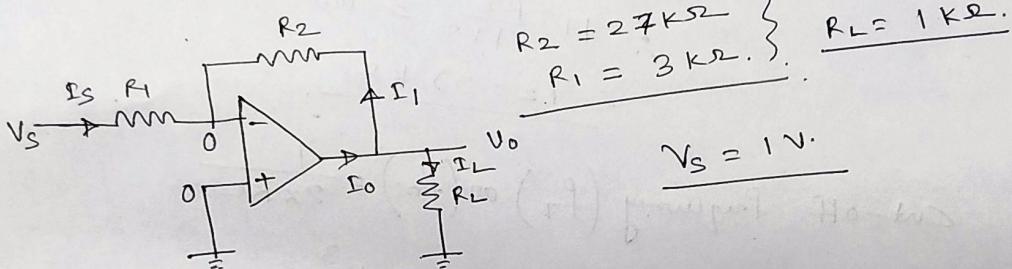

$$\begin{aligned} R_2 &= 27\text{k}\Omega \\ R_1 &= 3\text{k}\Omega \end{aligned} \quad \underline{R_L = 1\text{k}\Omega}$$

$$V_S = 1\text{V}$$

$$V_0 = -\frac{R_2}{R_1} V_S = -\frac{27}{3} \cdot 1 = -9\text{V}$$


$$I_L = -\frac{9\text{V}}{1\text{k}\Omega} = -9\text{mA}$$

$$I_1 = \frac{-9-0}{R_2} = -\frac{9\text{V}}{27\text{k}\Omega} = -0.33\text{mA}$$


$$I_0 = I_1 + I_L = -9.33\text{mA}$$

$$I_S = -I_1 = 0.33\text{mA}$$
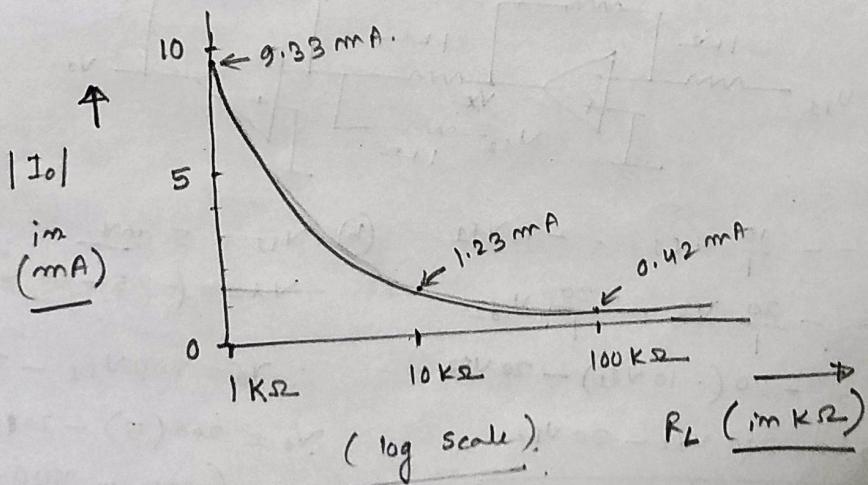
$$I_0 = I_1 + I_L = \left(-0.33 - \frac{9}{R_L} \right) \text{ in mA}$$



(4)

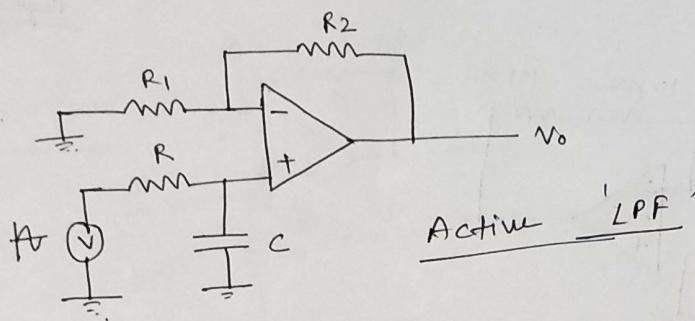

$$R_1 = 1 \text{ k}\Omega, C = 0.2 \text{ mF}$$

pass-band gain = $\frac{100}{1}$ = gain of the non-inverting amplifier.

$$A = \left(1 + \frac{R_2}{R_1}\right) = 100$$

$$\therefore 1 + \frac{R_2}{1 \text{ k}\Omega} = 100$$

$$\therefore R_2 = 99 \text{ k}\Omega.$$

$$\text{Cut-off frequency } (f_T) \text{ or } (f_c) = \frac{1}{2\pi RC}$$

$$\therefore \frac{1}{2\pi RC} = 2 \times 10^3$$

$$\therefore R = 398 \Omega.$$

(5)


$$\text{Differential gain} = 100, 2 \text{ Ad}$$

$$\text{Common mode gain } (Ac) = \frac{V_{out}}{V_{in}} = \frac{0.01}{1} = 10^{-2}$$

$$\therefore \text{CMRR} = \frac{Ad}{Ac} = \frac{100}{10^{-2}} = 10^4$$

$$\therefore (\text{CMRR})_{dB} = 20 \log \left| \frac{Ad}{Ac} \right| = 80 \text{ dB.}$$

(6) (a)

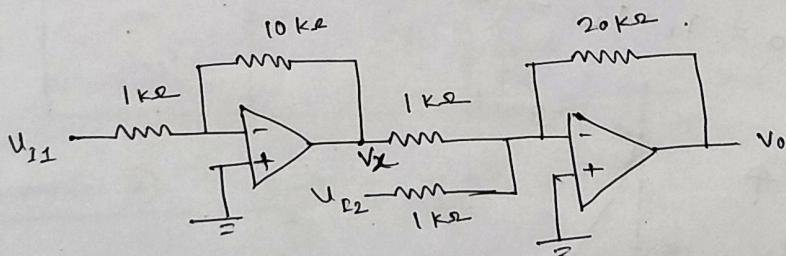

$$V_x = -\frac{10}{1} V_{11} = -10 V_{11}$$

$$(b) V_{11} = 5 \text{ mV.}$$

$$V_o = -\frac{20}{1} V_x - \frac{20}{1} V_{22}$$

$$V_{22} = (-25 - 50 \sin \omega t) \text{ mV}$$

$$= -20(-10 V_{11}) - 20 V_{22}$$

$$\therefore V_o = 200 V_{11} - 20 V_{22}$$


$$\therefore V_o = 200 V_{11} - 20 V_{22}$$

$$V_o = 200(5) - 20(-25 - 50 \sin \omega t)$$

$$= (1000 + 500 + 1000 \sin \omega t) \text{ mV}$$

$$\underline{V_o = (1.5 + \sin \omega t) V.}$$

(7)

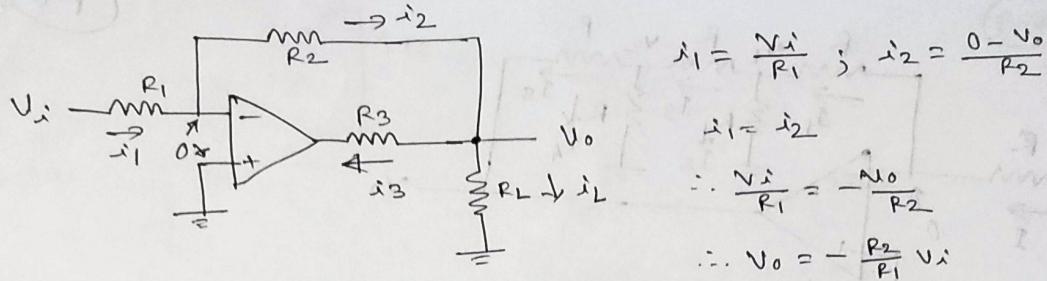

$$i_1 = \frac{V_i}{R_1} ; i_2 = \frac{0 - V_o}{R_2}$$

$$i_1 = i_2$$

$$\therefore \frac{V_i}{R_1} = -\frac{V_o}{R_2}$$

$$\therefore V_o = -\frac{R_2}{R_1} V_i$$

$$i_L = \frac{V_o}{R_L}$$


again, $i_2 = i_3 + i_L$

$$\therefore \frac{V_i}{R_1} = i_3 + \frac{V_o}{R_L}$$

$$\therefore \frac{V_i}{R_1} = i_3 - \frac{R_2}{R_1 R_L} V_i$$

$$\therefore i_3 = \frac{V_i}{R_1} \left(1 + \frac{R_2}{R_L} \right)$$

(8)

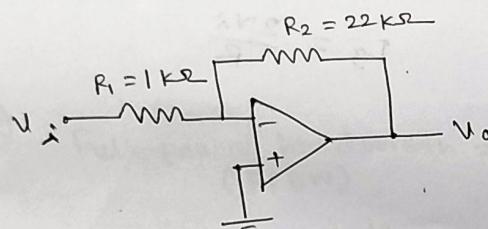

(a) Considering the op-amp as ideal, the gain is $= -\frac{R_2}{R_1}$
 $= -\frac{22}{1} = -22$

(b) Actual gain $= -\frac{R_2}{R_1} \times \frac{1}{\left[1 + \frac{1}{A_{od}} \left(1 + \frac{R_2}{R_1} \right) \right]}$; [we have derived this in the class]

where, A_{od} = open-loop gain.

$$= -22 \times \frac{1}{1 + \frac{1}{5 \times 10^3} (1 + 22)}$$


$$= -21.9$$

(c) Gain $= -22 \pm 0.2\%$ $= -22 \pm 0.044 = \underline{-22.044} \quad \checkmark$

$$\therefore -21.956 = -22 \times \frac{1}{1 + \frac{1}{A_{od}} \times 23}$$

$$\therefore 23/A_{od} = 1.002 - 1$$

$$\therefore A_{od} = 11.4 \times 10^3$$

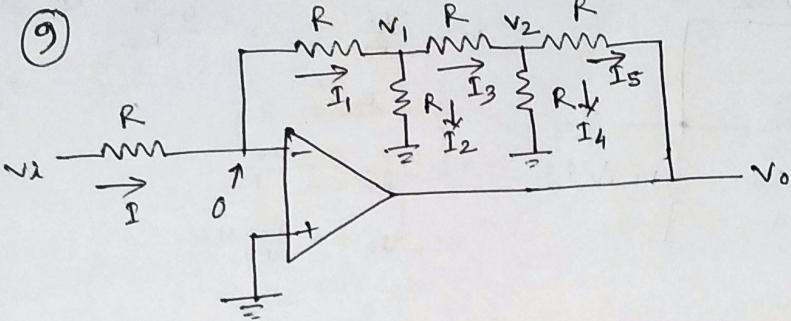

$$I = \frac{V_x - 0}{R} = \frac{V_x}{R} = I_1 \quad \therefore V_1 = 0 - I_1 R \\ V_1 = -\frac{V_x}{R} \times R = -V_x$$

$$\therefore I_2 = \frac{V_1}{R} = -\frac{V_x}{R} ; \text{ again, } I_1 = I_2 + I_3$$

$$\therefore I_3 = I_1 - I_2 \\ = \frac{V_x}{R} - \left(-\frac{V_x}{R} \right)$$

$$I_3 = \frac{2V_x}{R}$$

$$\therefore V_2 = V_1 - I_3 R \\ = -V_x - \frac{2V_x}{R} \times R$$


$$\therefore V_2 = -3V_x$$

$$\text{So, } I_4 = \frac{V_2}{R} = -\frac{3V_x}{R}$$

$$I_5 = I_3 - I_4 = \frac{2V_x}{R} - \left(-\frac{3V_x}{R} \right) = \frac{5V_x}{R}$$

$$V_0 = V_2 - I_5 R = -3V_x - \frac{5V_x}{R} \cdot R = -8V_x$$

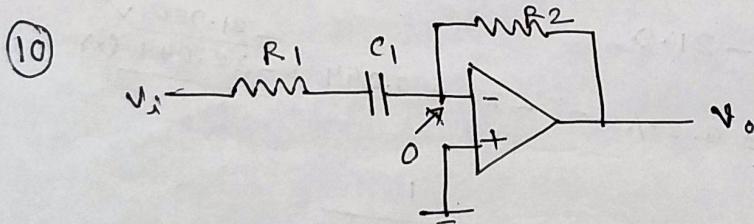
$$\therefore \frac{V_0}{V_x} = -8 = \text{Av}$$



$$\text{Non-inverting amplifier, gain} = \frac{V_0}{V_x} = -\frac{Z_2}{Z_1} \\ = -\frac{R_2}{R_1 + \frac{1}{j\omega C_1}}$$

$$\text{Gain.} = -\frac{R_2 (j\omega C_1)}{R_1 j\omega C_1 + 1}$$

(11)

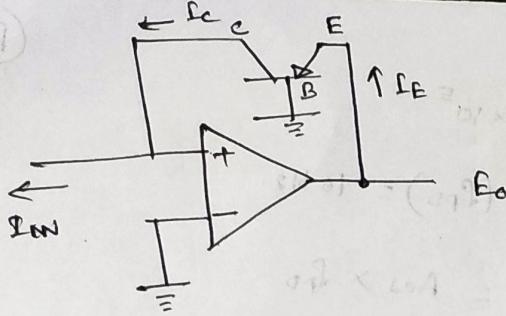

(P-7)

$$V_{EB} = E_0.$$

$$I_E = I_{ES} \exp\left(\frac{V_{EB}}{V_T}\right)$$

$$I_E \approx I_c \quad (\beta \text{ very high})$$

$$\therefore I_c = I_{IN}$$

$$\therefore I_{IN} = I_{ES} \exp\left(\frac{V_{EB}}{V_T}\right)$$

$$\frac{I_{IN}}{I_{ES}} = \exp\left(\frac{E_0}{V_T}\right)$$

$$\therefore E_0 = \frac{kT}{q} \ln\left(\frac{I_{IN}}{I_{ES}}\right); [V_T = \frac{kT}{q}]$$

(12)

Full power bandwidth (FPBW) = $\frac{SR}{2\pi V_{max}}$

 $SR = \text{slew rate}$ $V_{max} = \text{peak output voltage}$

$$(a) \text{ FPBW} = \frac{5 \text{ V/μs}}{2\pi (5)} = \frac{5 \times 10^6 \text{ V/s}}{2\pi \times 5} = 159.2 \text{ kHz.}$$

$$(b) \text{ FPBW} = 530.78 \text{ kHz.}$$

$$(c) \text{ FPBW} = 1.99 \text{ MHz.}$$

$$(13) \text{ Output peak} = 10 \text{ V.} \quad \text{max. frequency} = 12 \text{ kHz.}$$

$$\therefore \text{FPBW} = 12 \text{ kHz.}$$

If the max. operating freq. is limited by the slew rate, then

$$\text{FPBW} = \frac{SR}{2\pi V_{max}}$$

$$\therefore SR = \text{FPBW} \times 2\pi V_{max}$$

$$= 12 \times 10^3 \times 2\pi \times 10$$

$$\therefore SR = 0.75 \text{ V/μs.}$$

(14)

$$\text{open-loop gain } (A_{od}) = 2 \times 10^5$$

$$\text{Dominant pole frequency } (f_{pd}) = 10 \text{ Hz.}$$

$$\therefore \text{unity-gain bandwidth} = A_{od} \times f_{pd}$$



$$= 2 \times 10^6$$

$$\text{closed loop gain } (A_{cd}) = 100$$

$$\therefore \text{so, closed loop frequency} = \frac{2 \times 10^6}{100} = 2 \times 10^4$$

$\approx 20 \text{ kHz.}$


(15)

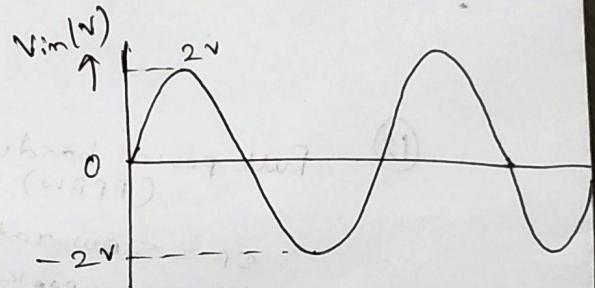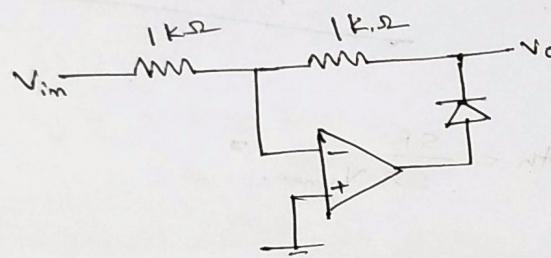

This is an inverting amplifier with gain = -1

When V_{in} is negative, V_o is positive, diode is forward biased.

Precision rectifier (inverting).

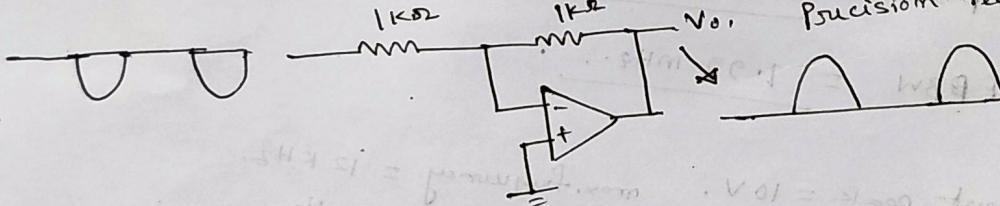

When V_{in} is positive, diode is OFF.

