

# Introduction to Electronics (Practice Paper – 7A)

## Topic: Digital Electronics

1. Convert the following hexadecimal numbers to their decimal and binary equivalents:

- (a)  $(13AF)_{16}$     (b)  $(25E6)_{16}$     (c)  $(B4.C9)_{16}$     (d)  $(45)_{16}$

2. Convert the following octal number to their decimal and binary equivalents:

- (a)  $(56.2)_8$                       (b)  $(16.2)_8$                       (c)  $(20.45)_8$

3. Draw a combinational logic circuit that uses only one AND gate and one OR gate to realize each of the following functions:

- (a)  $(A + B + C + D)(A + B + C + E)(A + B + C + F)$

- (b)  $WXYZ + VXYZ + UXYZ$

4. Factor each of the following expressions to obtain a product of sums:

- (a)  $AB + C'D'$                       (b)  $WX + WY'X + ZYX$

- (c)  $A'BC + EF + DEF'$               (d)  $XYZ + W'Z + XQ'Z$

5. Simplify each of the following expressions by applying one of the theorems.

- (a)  $(X + Y'Z) + (X + Y'Z)'$

- (b)  $[W + X'(Y + Z)][W' + X'(Y + Z)]$

- (c)  $(V'W + UX)'(UX + Y + Z + V'W)$

6. Express the following function in POS (Product of Sums) and SOP (Sum of Products) forms:

$$F = xy + z'$$

7. Draw a circuit that uses two OR gates and two AND gates to realize the following function:


$$F = (V + W + X)(V + X + Y)(V + Z)$$

8. Simplify the following expressions:

- (a)  $AB'CD' + A'BCD + CD'$                       (b)  $AB'C' + CD' + BC'D'$

- (c)  $(A+B')(A'+B'+D)(B'+C+D')$               (d)  $(A'+B+C'+D)(A'+C'+D+E)(A'+C'+D+E')$


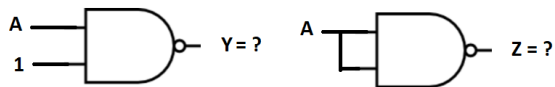
9. Find Y and Z. Identify the logic operation.



10. Implement NOR operation using only NAND gates.

Implement NAND operation using only NOR gates.

11. Draw the output waveform Y.

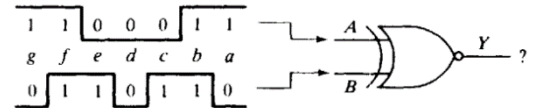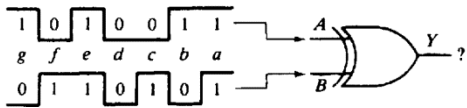

12. Express F in product of sum (POS) form or max. term form.

$$F = a'(b' + d) + cd'(a+b')$$

$$F = AB + A'BC'$$