

$$\beta_F = 65 \text{ V}.$$

$$V_A = 50 \text{ V}.$$

$$V_{BE(on)} = 0.7 \text{ V}.$$

DC analysis

KVL base loop:

$$100 \times 10^3 \times I_B + 0.7 + (1+\beta) \times 16 \times 10^3 I_E = 5$$

$$\therefore [I_F = (1+\beta) I_B].$$

$$\therefore I_B = 3.71 \text{ mA}.$$

$$\therefore I_C = 65 \times 3.71 \text{ mA} = 241.65 \text{ mA}.$$

$$I_E = 244.86 \text{ mA}.$$

KVL in outer loop:

$$5 - 10 \times 10^3 I_C - V_{CE} - 16 \times 10^3 I_E - (-5) = 0.$$

$$V_{CE} = 3.67 \text{ V}.$$


AC analysis:

$$g_m = \frac{I_C}{V_T} = 9.27 \times 10^{-3} \text{ S}.$$

$$r_x = \frac{\beta}{g_m} = 7.03 \times 10^3 \Omega.$$

$$r_o = \frac{V_A + V_{CE}}{I_C} = 222.69 \text{ k}\Omega.$$

with Early effect
No Early effect

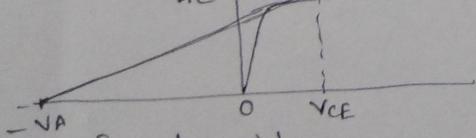


Input resistance


$$R_{in} = R_B \parallel r_x = 6.54 \text{ k}\Omega.$$

Output resistance
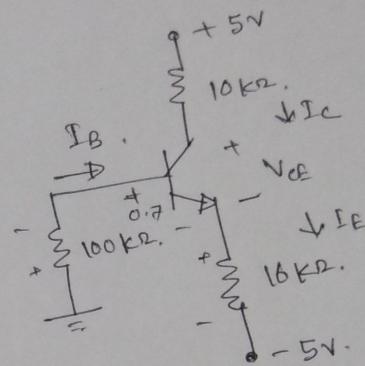
$$R_{out} = R_C \parallel r_o = 9.57 \text{ k}\Omega.$$



B-point:


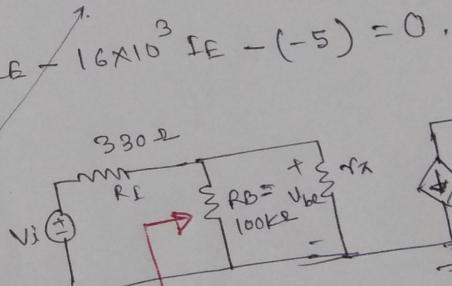


$$V_o = -g_m V_{be} \cdot (\text{roll } R_C \parallel R_B).$$

$$\therefore V_o = -g_m \left(\frac{R_B \parallel r_x}{R_B \parallel r_x + R_C} \right) \cdot V_i \cdot (\text{roll } R_C \parallel R_B)$$



$$\therefore \frac{V_o}{V_i} = -g_m \left(\frac{R_B \parallel r_x}{R_B \parallel r_x + R_C} \right) (\text{roll } R_C \parallel R_B).$$

$$\text{Gain} = -81.26.$$

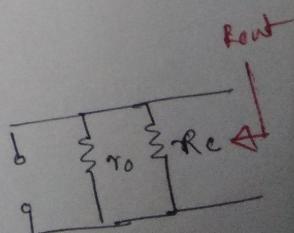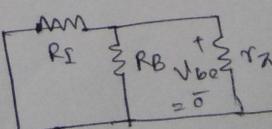

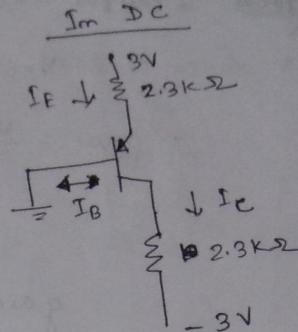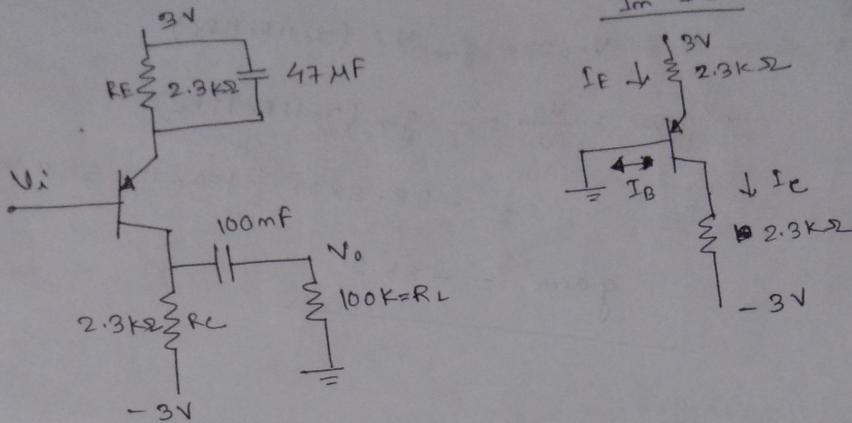(2)

$\beta = 200$ and $V_A = 150 \text{ V}$. (Early voltage)



p-n-p common emitter amplifier

(a) Assuming the BJT is in active mode:

$$V_{EB} = 0.7 \text{ V}, I_c > 0 \text{ and } V_{EC} > 0.7 \text{ V.}$$

Apply KVL in B-E loop, $3 = 2.3 \times 10^3 \times I_E + V_{EB}$

$$\therefore I_E = 1 \text{ mA} \approx I_c$$

[as $\beta = 200$]

$$\therefore I_B = \frac{I_c}{\beta} = 5 \text{ mA.}$$

Apply KVL in C-E loop, $3 = 2.3 \times 10^3 I_E + V_{EC} + 2.3 \times 10^3 I_C - 3$



$$\therefore V_{EC} = 1.4 \text{ V} (> 0.7)$$

so, in active region
is assumed.


$$(b) g_m = \frac{I_c}{V_T} = \frac{10^{-3}}{26 \times 10^3} = 38.5 \text{ mS.}$$

$$r_o = \frac{V_A}{I_c} = \frac{150}{1 \text{ mA}} = 150 \text{ k}\Omega ; V_A \gg V_{EC}$$
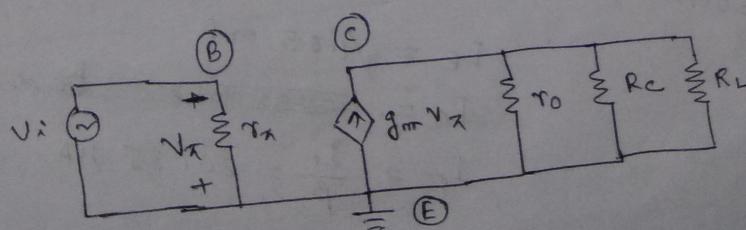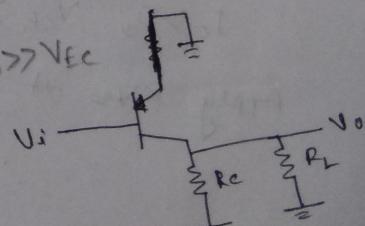
$$r_x = \frac{\beta V_T}{I_c} = 5.2 \text{ k}\Omega$$



(5)

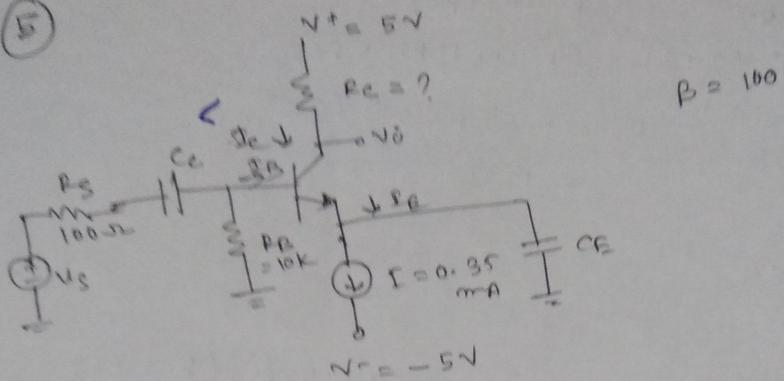

(5)

(6)

$$\text{So, } I_E = 0.35 \text{ mA.}$$

$$\therefore I_B = \frac{0.35}{101} = 0.00347 \text{ mA.} = 3.47 \text{ mA}$$

$$\therefore V_B = -I_B R_B = -(3.47 \text{ mA}) \times 10 \text{ k.}$$

$$V_B = -0.0347 \text{ V.}$$

$$V_{BE(\text{ON})} = 0.7.$$

$$\therefore V_B - V_E = 0.7.$$

$$\therefore V_E = -0.7 + V_B = -0.7347 \text{ V.}$$

~~(b) V_E < V_C so CE is cut off.~~

(b)

$$\frac{5 - V_O}{R_C} = I_C = \frac{\beta}{1+\beta} I_E$$

$$\frac{5 - 2.77}{R_C} = 0.347.$$

$$\therefore R_C = 6.43 \text{ k}\Omega.$$

$$V_{CE(s)} = 3.5 \text{ V.}$$

$$\therefore V_O = V_{CE(s)} + V_E$$

$$= 3.5 - 0.7347$$

$$\approx 2.77 \text{ V.}$$

$$(c) \underline{V_A = 100 \text{ V.}}$$

$$r_o = \frac{V_A}{I_C} = 288 \text{ k}\Omega$$

$$g_m = \frac{I_C}{V_T} = 13.3 \text{ mA/V.}$$

$$r_x = \frac{100 \times V_T}{I_C} = 7.49 \text{ k}\Omega$$

$$\text{gain}(A_v) = \frac{V_o}{V_s} = -g_m \cdot \left(\frac{R_B || r_x}{R_S + R_B || r_x} \right) (R_C || r_o)$$



$$= -81.7.$$

(d) if, $R_S = 500 \Omega$

$$A_v = -g_m \times \frac{R_B || r_A}{R_B || r_A + R_S} \times (R_C || r_o)$$

$$= -74.9 \quad (\text{Comment: gain reduces when } R_S \text{ increases})$$

(e)

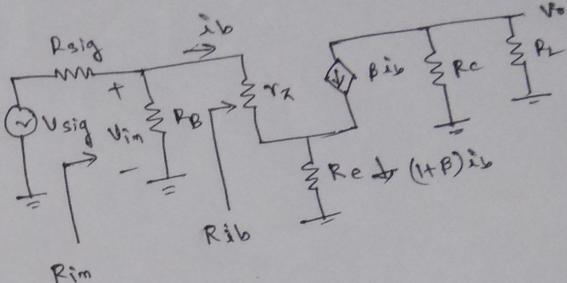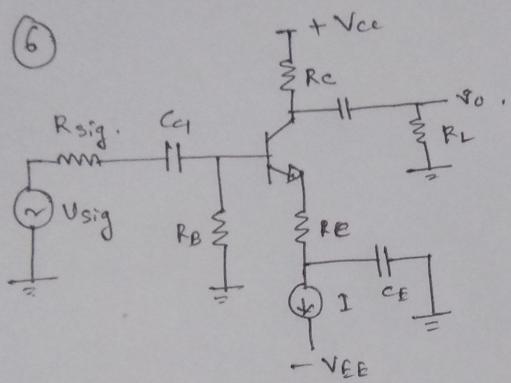

$$V_{in} = i_b r_A + (1+\beta) i_b R_E \quad \therefore R_{in} = \frac{V_{in}}{i_b} = r_A + (1+\beta) R_E$$

$$R_{in} = R_B || R_{bb}$$

$$\therefore V_{in} = \frac{R_{in}}{R_{in} + R_{sig}} U_{sig}$$

$$V_o = -\beta i_b (R_C || R_L)$$

$$V_o = -\beta \cdot \frac{V_{in}}{R_{bb}} (R_C || R_L)$$

$$V_o = -\frac{\beta (R_C || R_L)}{r_A + (1+\beta) R_E} \cdot V_{in}$$

$$\therefore \frac{V_o}{V_{in}} = -\frac{\beta (R_C || R_L)}{r_A + (1+\beta) R_E}$$

$$\therefore \frac{V_o}{U_{sig}} = -\frac{\beta R_{in} (R_C || R_L)}{(R_{in} + R_{sig}) [r_A + (1+\beta) R_E]} = A_v \quad (\text{small-signal voltage gain}).$$