


EXPERIMENT 3 (1)

NISARG UPADHYAYA
19CS30031 Nirav.

OBJECTIVE

To study the frequency response of series R-L-C circuit.

CIRCUIT DIAGRAM

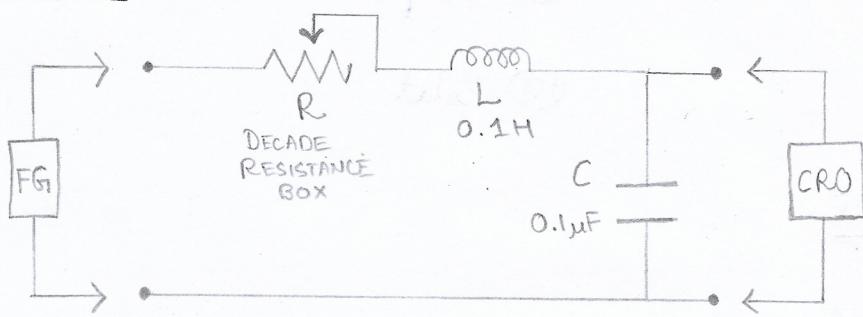

THEORY

The standard Laplace - domain transfer function is

$$H(s) = \frac{1}{\left(\frac{1}{\omega_n^2}s^2 + 2\xi s + 1\right)} \quad \text{--- (1)}$$

The transfer function for the given circuit is


$$H(s) = \frac{1}{LCs^2 + RCs + 1} \quad \text{--- (II)}$$

Comparing (1) & (II) we get

$$\omega_n = \frac{1}{\sqrt{LC}} \quad \text{and} \quad 2\xi\omega_n = \frac{R}{L}$$

Knowing L, C and ξ we can find R.

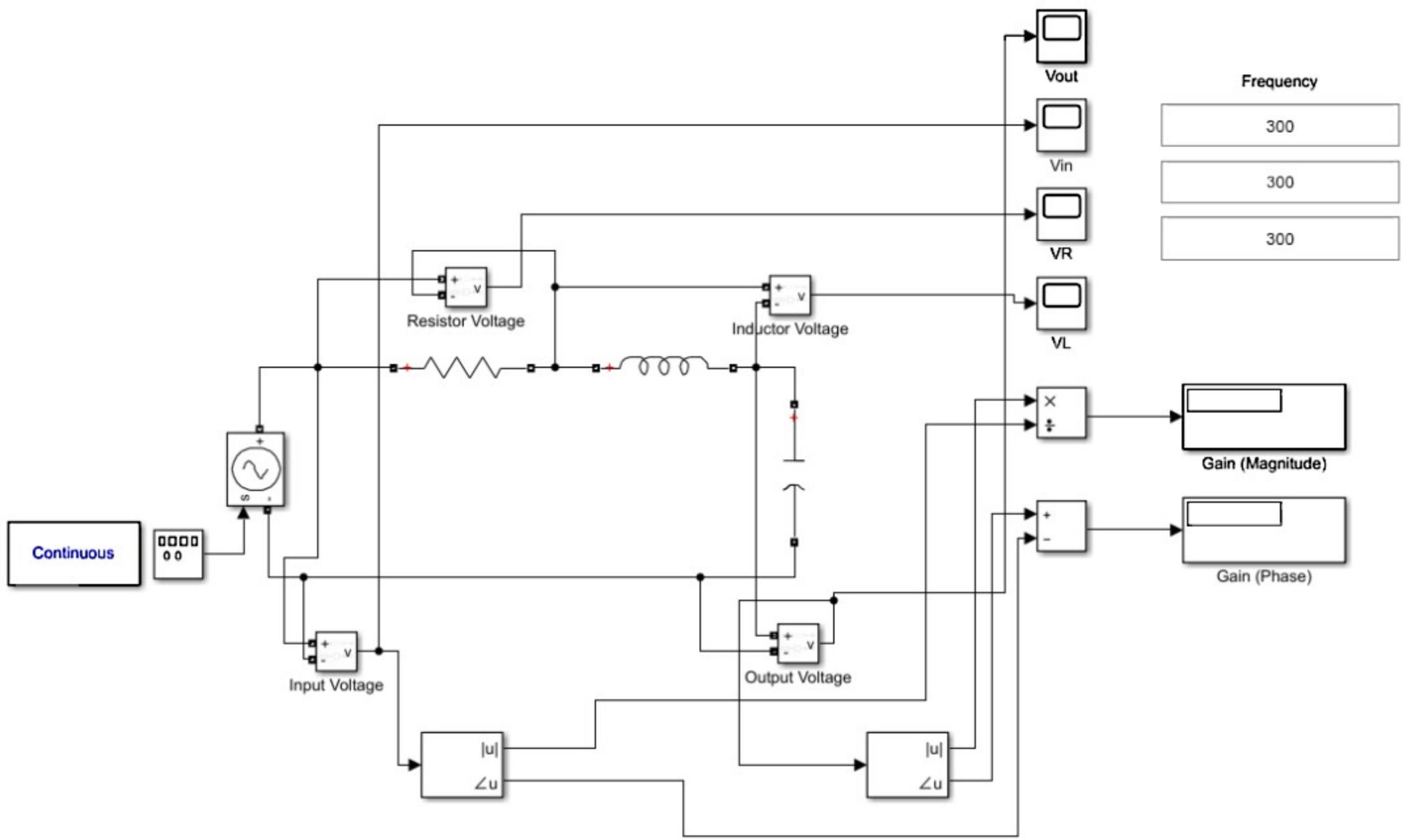The maximum magnitude of gain is $\frac{1}{2\xi\sqrt{1-\xi^2}}$ and it occurs at $\omega = \omega_n\sqrt{1-2\xi^2}$



SIMULINK BLOCKS USED

NISARG UPADHYAYA
19CS30031 Jyoti.

- ① Signal Generator
- ② Controlled Voltage Source
- ③ Series RLC branch
- ④ Voltage Measurement
- ⑤ Fourier
- ⑥ Divide
- ⑦ Add
- ⑧ Display
- ⑨ Scope
- ⑩ Edit
- ⑪ powergui

SIMULINK PROCEDURE

- ① Set the simulation type to continuous using powergui block.
- ② Set the solver to ode23t in model configuration parameters.
- ③ Set the wave form to sine and amplitude to 5V in signal generator.
- ④ Set $R = 400\Omega$ ($\xi = 0.2$)
- ⑤ Using the edit blocks set the frequency of the signal generator and the Fourier blocks. Make sure that frequency of Fourier blocks is same as that of signal generator.
- ⑥ Run the simulation. The gain (magnitude and phase) can be seen on the display blocks. Measure V_R , V_L and V_C by opening their respective scopes and turning on signal statistics.
- ⑦ Repeat step 6 for different values of frequency in (00-10K) Hz range (equally/uniformly distributed).
- ⑧ Repeat steps 4-7 for $\xi = 0.7, 0.95$ and 1.5 .
- ⑨ Plot Gain (magnitude and phase) vs Frequency (Hz) on a semilog graph plot using MATLAB.

OBSERVATION TABLES

NISARGI UPADHYAYA

19CS30031

Silvay.


$$\textcircled{1} \quad \xi = 0.2 \quad (R = 400 \Omega)$$

$$V_{in} = 5V$$


| Frequency (Hz) | V_c (V) | V_L (V) | V_R (V) | Gain (magnitude) (V_c/V_{in}) | Gain (phase) (degrees) |
|-------------------|--------------|--------------|--------------|--------------------------------------|---------------------------|
| 150 | 5.041 | 0.050 | 0.202 | 1.010 | -2.224 |
| 250 | 5.116 | 0.127 | 0.322 | 1.024 | -3.588 |
| 300 | 5.168 | 0.184 | 0.390 | 1.034 | -4.375 |
| 400 | 5.305 | 0.335 | 0.533 | 1.062 | -6.046 |
| 1000 | 7.643 | 3.029 | 1.924 | 1.529 | -22.500 |
| 1420 | 12.190 | 9.739 | 4.358 | 2.441 | -60.410 |
| 1441 | 12.380 | 10.190 | 4.493 | 2.480 | -63.720 |
| 1460 | 12.530 | 10.580 | 4.606 | 2.509 | -66.850 |
| 1500 | 12.720 | 11.350 | 4.807 | 2.549 | -73.720 |
| 2000 | 6.463 | 10.260 | 3.257 | 1.294 | -139.000 |
| 5000 | 0.554 | 5.505 | 0.698 | 0.111 | -171.500 |
| 7500 | 0.233 | 3.213 | 0.441 | 0.047 | -174.300 |
| 10000 | 0.128 | 1.118 | 0.324 | 0.026 | -175.500 |
| 12000 | 0.088 | 0.072 | 0.268 | 0.018 | -176.400 |

* EXPERIMENTAL AND THEORETICAL FREQUENCY
RESPONSE PLOTS ATTACHED BELOW

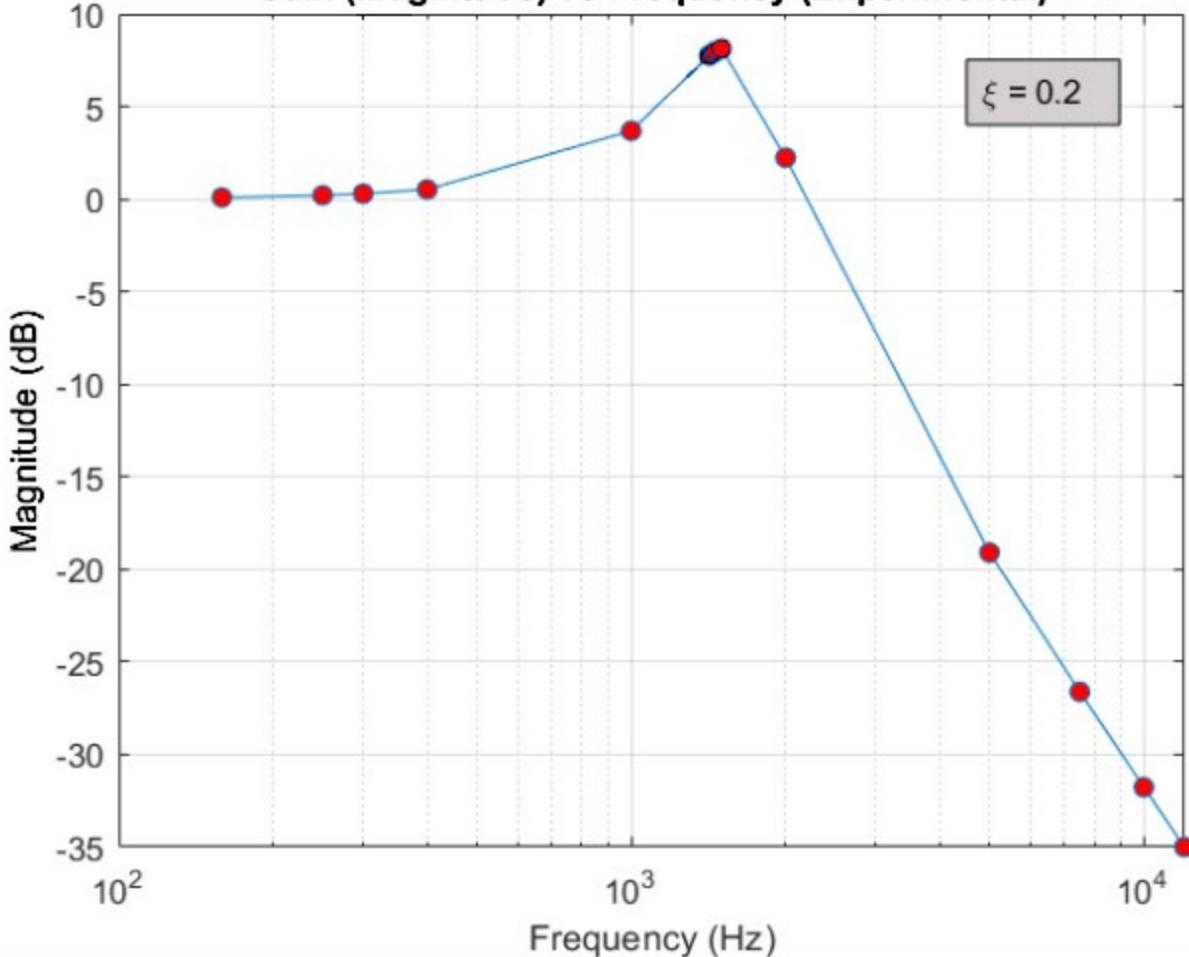
Gain (Magnitude) vs Frequency (Experimental)



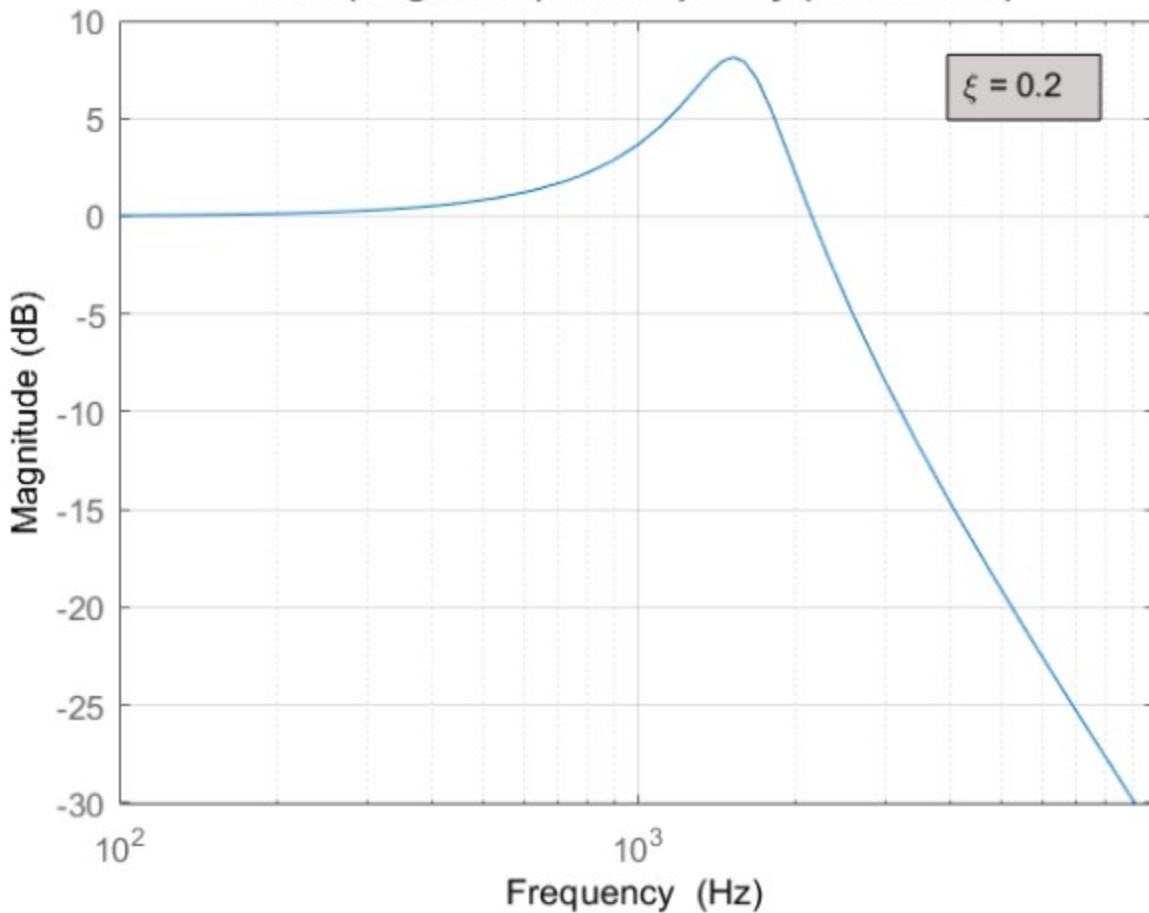
Gain (Magnitude) vs Frequency (Theoretical)



Gain (Phase) vs Frequency (Experimental)

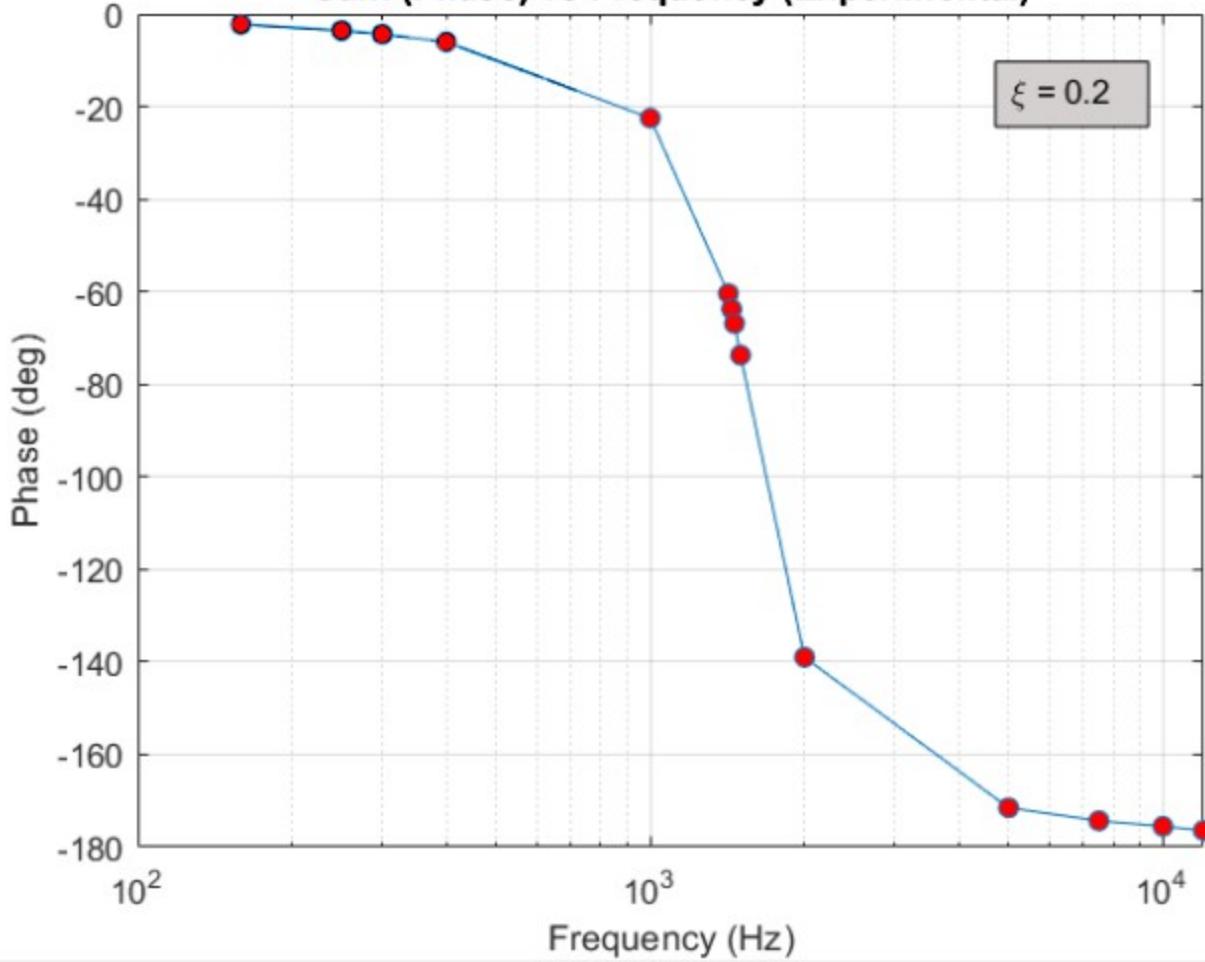

Gain (Phase) vs Frequency (Theoretical)

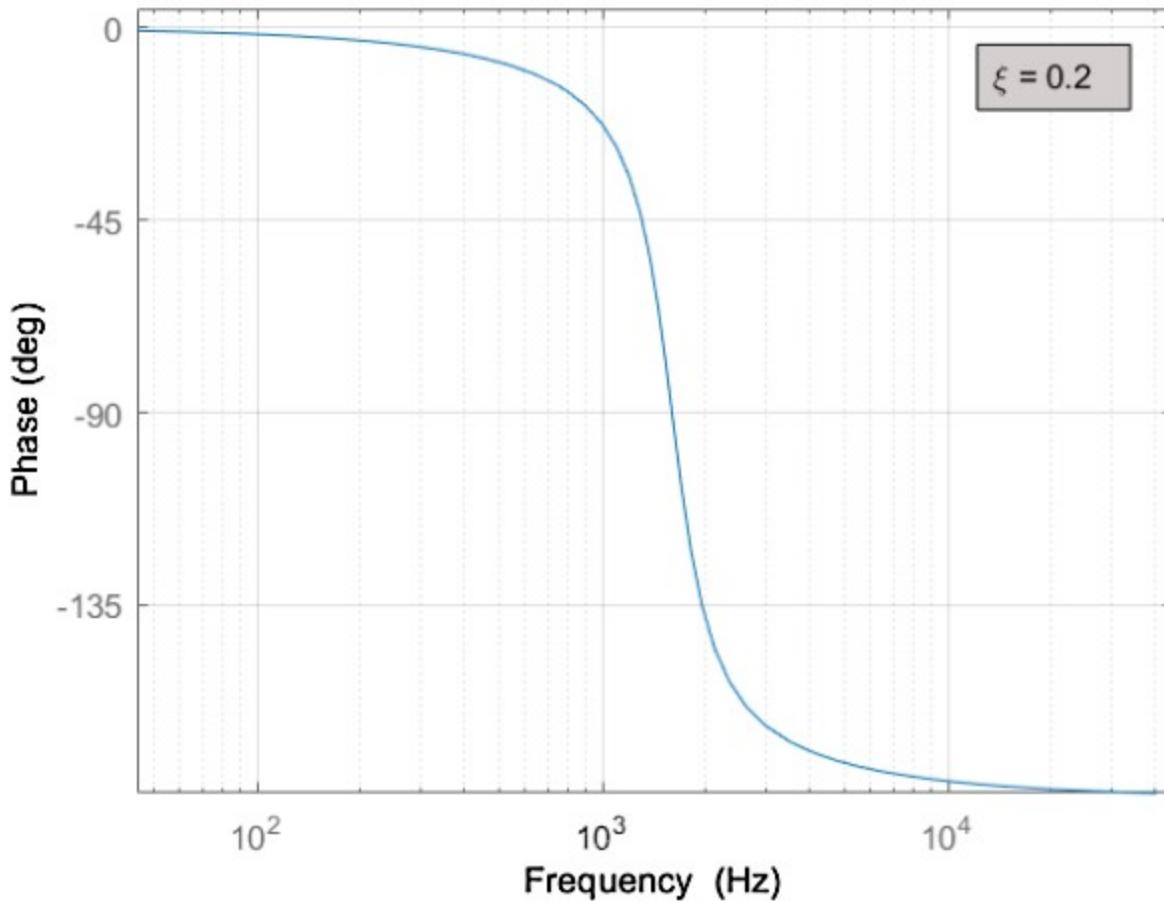


$$\textcircled{2} \quad g = 0.7 \quad (R = 1400 \Omega)$$

$$V_{in} = 5V$$


| Frequency (Hz) | V_c (V) | V_L (V) | V_R (V) | Gain(magnitude) (V_c/V_{in}) | Gain (phase) (degree) |
|-------------------|--------------|--------------|--------------|-------------------------------------|--------------------------|
| 150 | 4.991 | 0.080 | 0.699 | 0.998 | -7.951 |
| 250 | 5.000 | 0.124 | 1.101 | 1.000 | -12.640 |
| 300 | 4.986 | 0.178 | 1.322 | 0.998 | -15.220 |
| 400 | 4.984 | 0.316 | 1.757 | 0.997 | -20.510 |
| 1000 | 4.681 | 1.854 | 4.124 | 0.938 | -55.410 |
| 1420 | 3.945 | 3.152 | 4.937 | 0.790 | -80.630 |
| 1441 | 3.899 | 3.209 | 4.952 | 0.781 | -81.840 |
| 1460 | 3.858 | 3.259 | 4.964 | 0.772 | -82.840 |
| 1500 | 3.769 | 3.362 | 4.983 | 0.755 | -85.010 |
| 2000 | 2.690 | 4.269 | 4.744 | 0.538 | -108.000 |
| 5000 | 0.501 | 4.985 | 2.213 | 0.101 | -183.200 |
| 7500 | 0.223 | 4.999 | 1.480 | 0.045 | -162.200 |
| 10000 | 0.126 | 5.001 | 1.110 | 0.025 | -166.600 |
| 12000 | 0.087 | 5.001 | 0.925 | 0.018 | -168.700 |

* EXPERIMENTAL AND THEORETICAL FREQUENCY
RESPONSE PLOTS ATTACHED BELOW

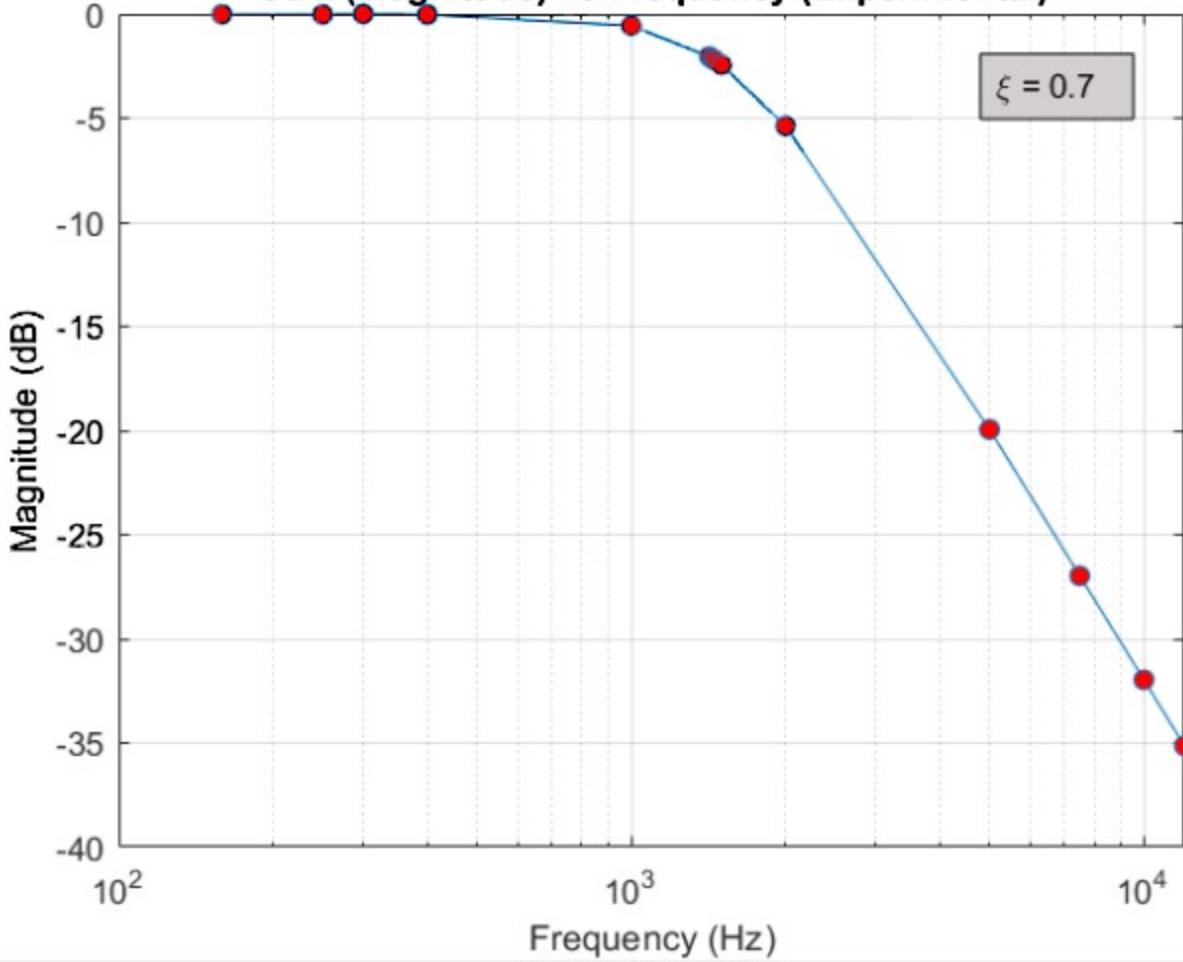
Gain (Magnitude) vs Frequency (Experimental)



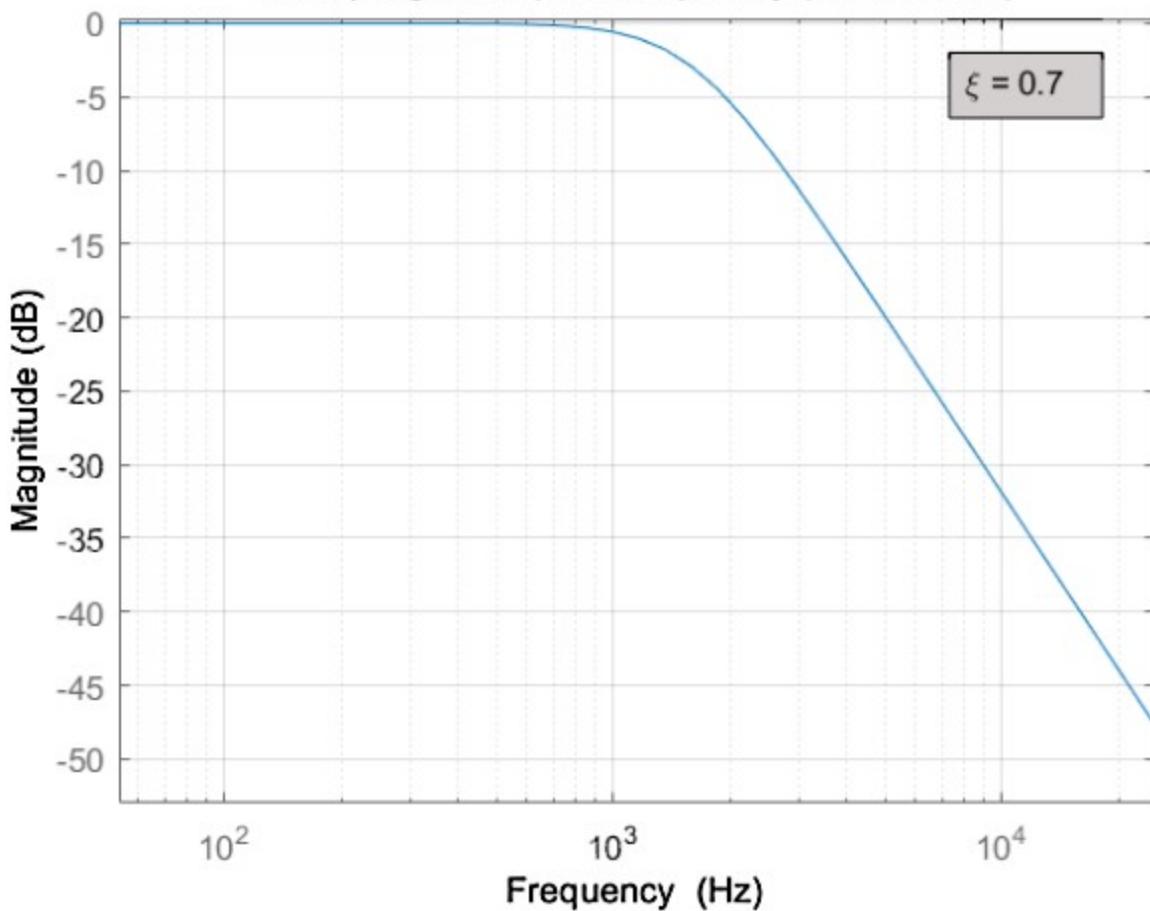
Gain (Magnitude) vs Frequency (Theoretical)



Gain (Phase) vs Frequency (Experimental)

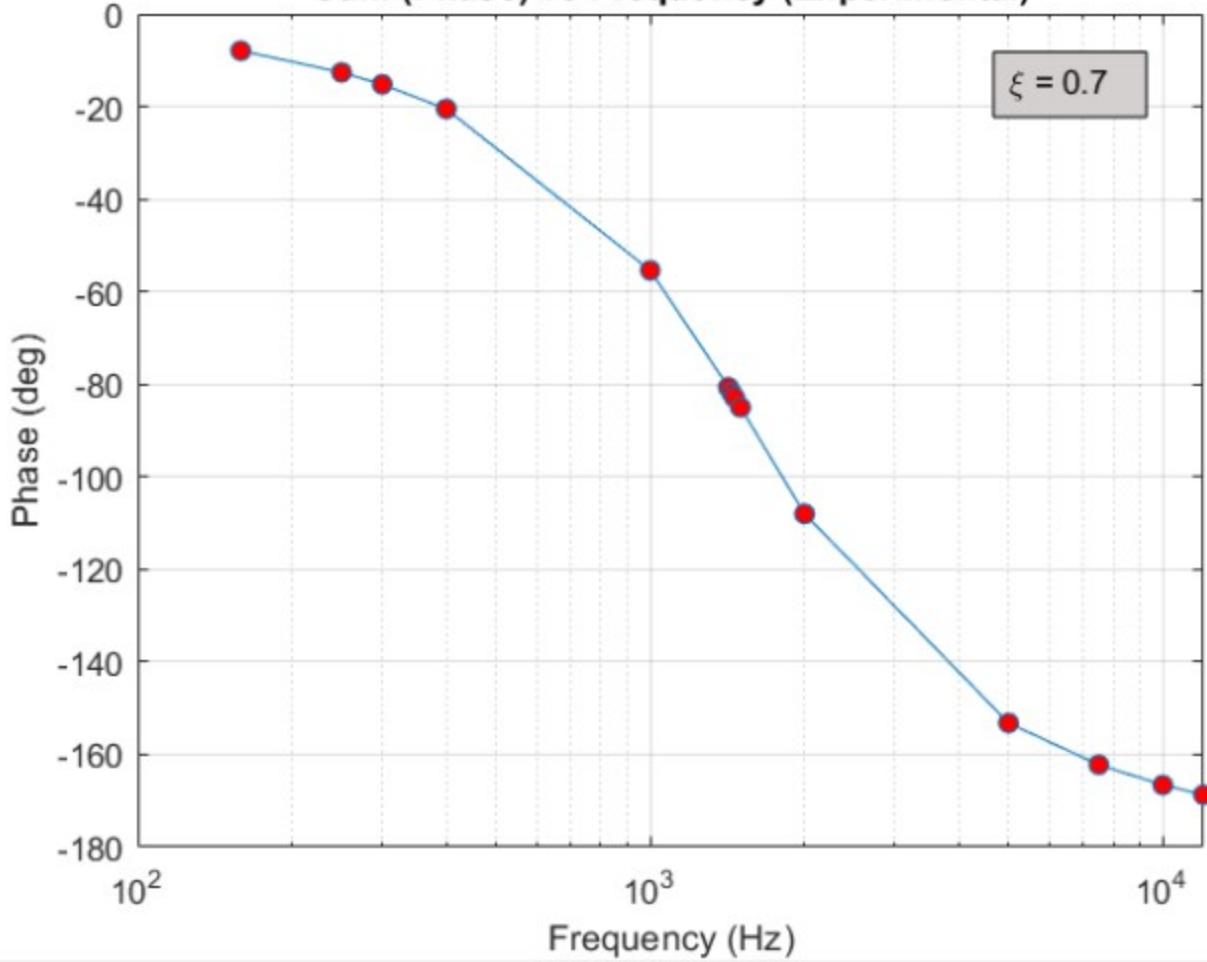

Gain (Phase) vs Frequency (Theoretical)

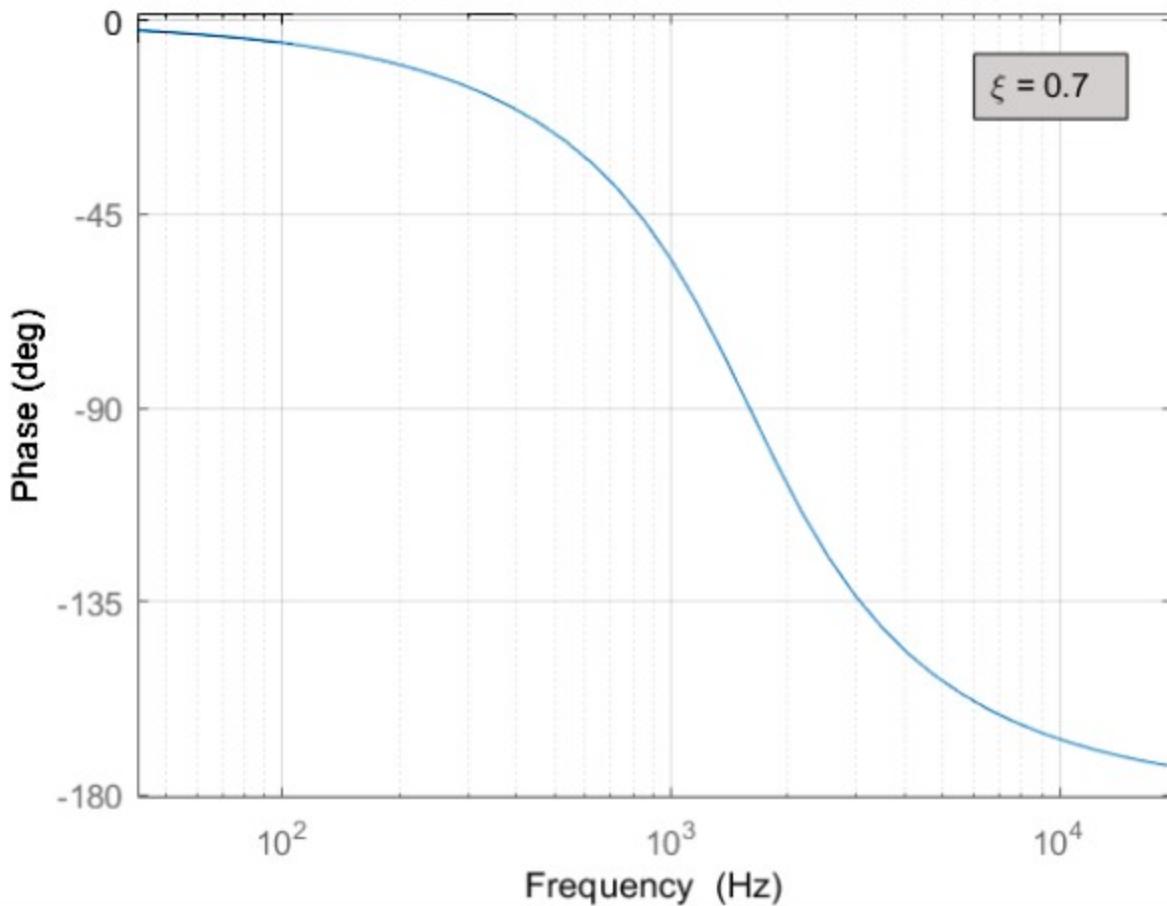


$$\textcircled{3} \quad \xi = 0.45 \quad (R = 1900 \Omega)$$

$$V_{in} = 5V$$


| Frequency (Hz) | V_C (V) | V_L (V) | V_R (V) | Gain(magnitude) (V_C/V_{in}) | Gain(phase) (degree) |
|-------------------|--------------|--------------|--------------|-------------------------------------|-------------------------|
| 150 | 4.950 | 0.050 | 0.942 | 0.993 | -10.770 |
| 250 | 4.894 | 0.121 | 1.462 | 0.981 | -16.930 |
| 300 | 4.885 | 0.173 | 1.743 | 0.973 | -20.280 |
| 400 | 4.753 | 0.301 | 2.273 | 0.951 | -26.960 |
| 1000 | 3.732 | 1.478 | 4.460 | 0.747 | -63.050 |
| 1400 | 2.923 | 2.336 | 4.965 | 0.585 | -83.030 |
| 1441 | 2.886 | 2.375 | 4.974 | 0.578 | -83.850 |
| 1460 | 2.852 | 2.409 | 4.980 | 0.571 | -84.630 |
| 1500 | 2.782 | 2.481 | 4.991 | 0.557 | -86.280 |
| 2000 | 2.030 | 3.219 | 4.857 | 0.406 | -103.500 |
| 5000 | 0.465 | 4.618 | 2.783 | 0.393 | -145.600 |
| 7500 | 0.216 | 4.825 | 1.938 | 0.043 | -156.700 |
| 10000 | 0.123 | 4.900 | 1.476 | 0.025 | -162.300 |
| 12000 | 0.086 | 4.931 | 1.237 | 0.017 | -165.000 |

* EXPERIMENTAL AND THEORETICAL FREQUENCY
RESPONSE PLOTS ATTACHED BELOW

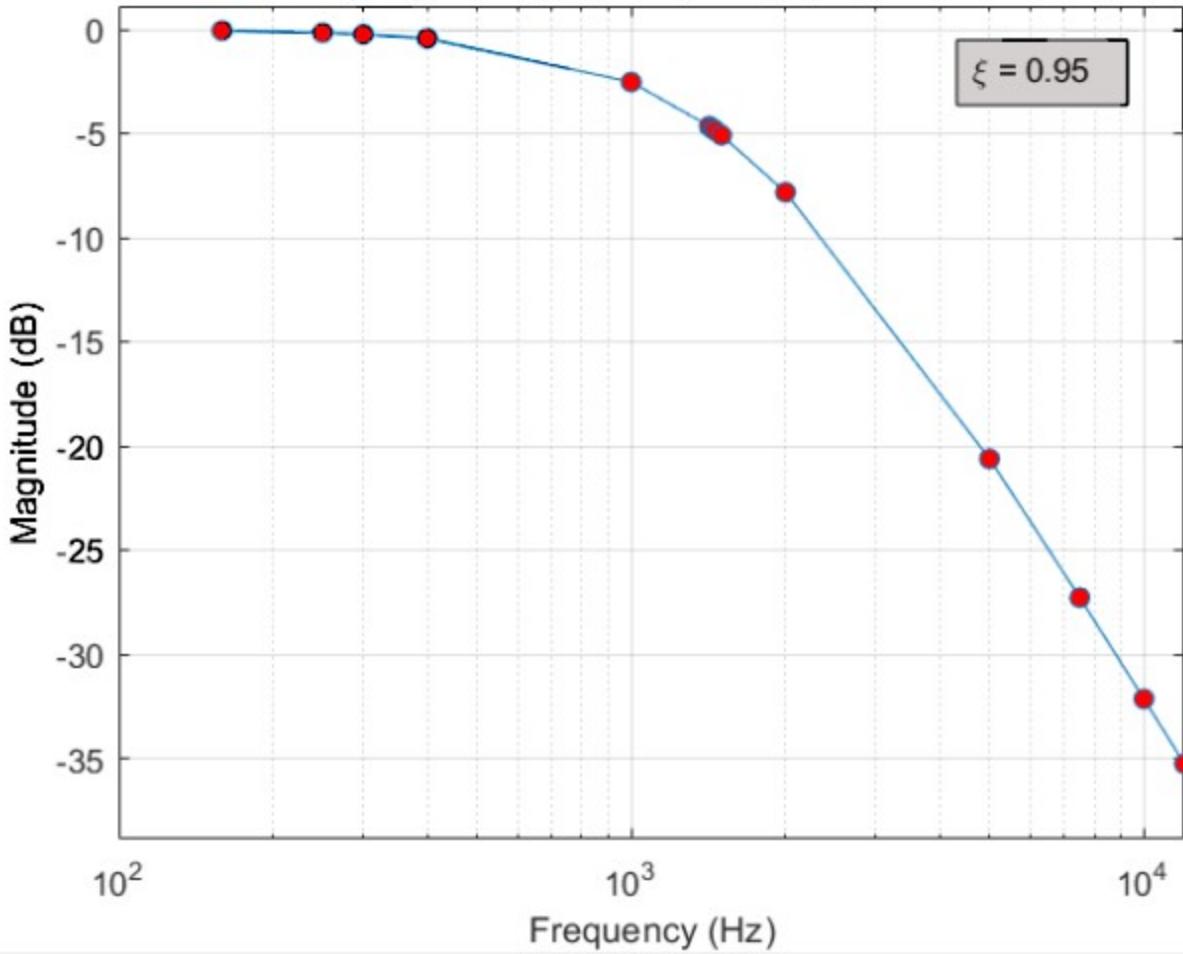
Gain (Magnitude) vs Frequency (Experimental)



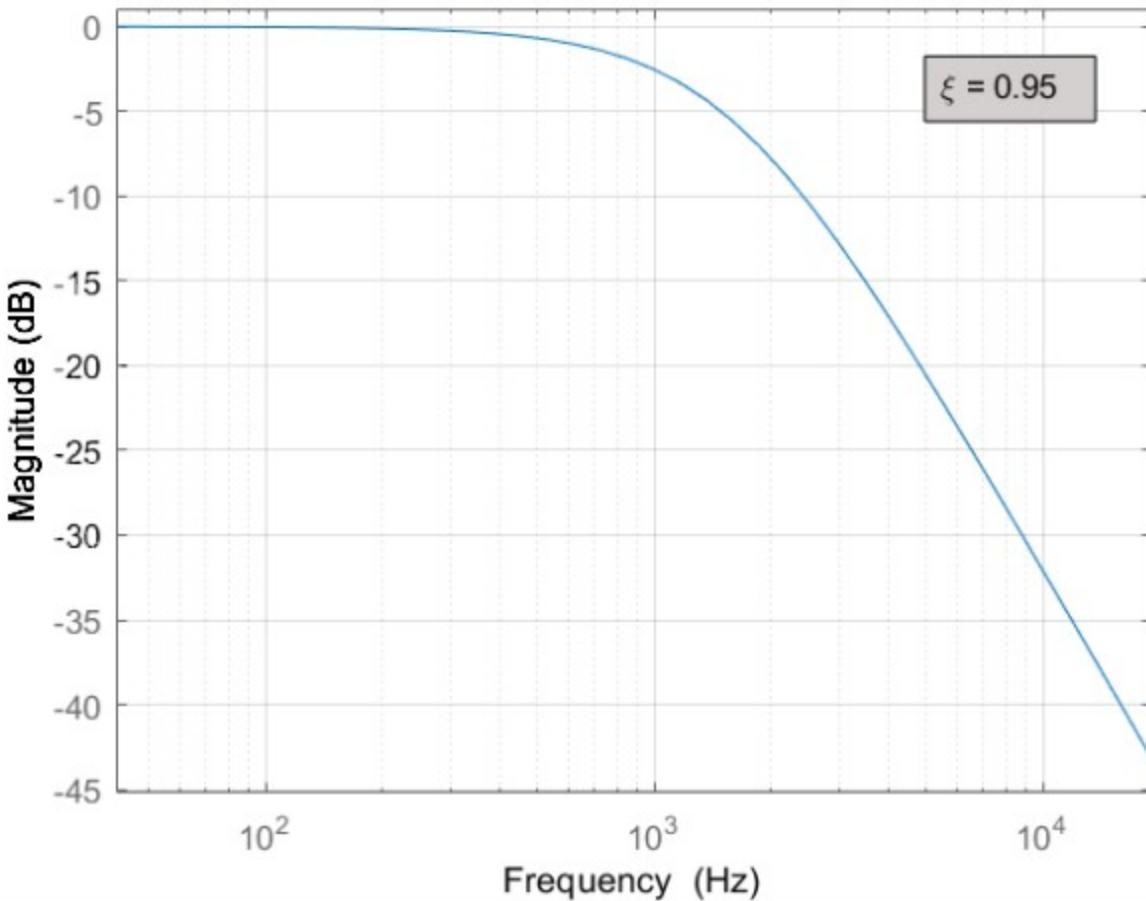
Gain (Magnitude) vs Frequency (Theoretical)



Gain (Phase) vs Frequency (Experimental)

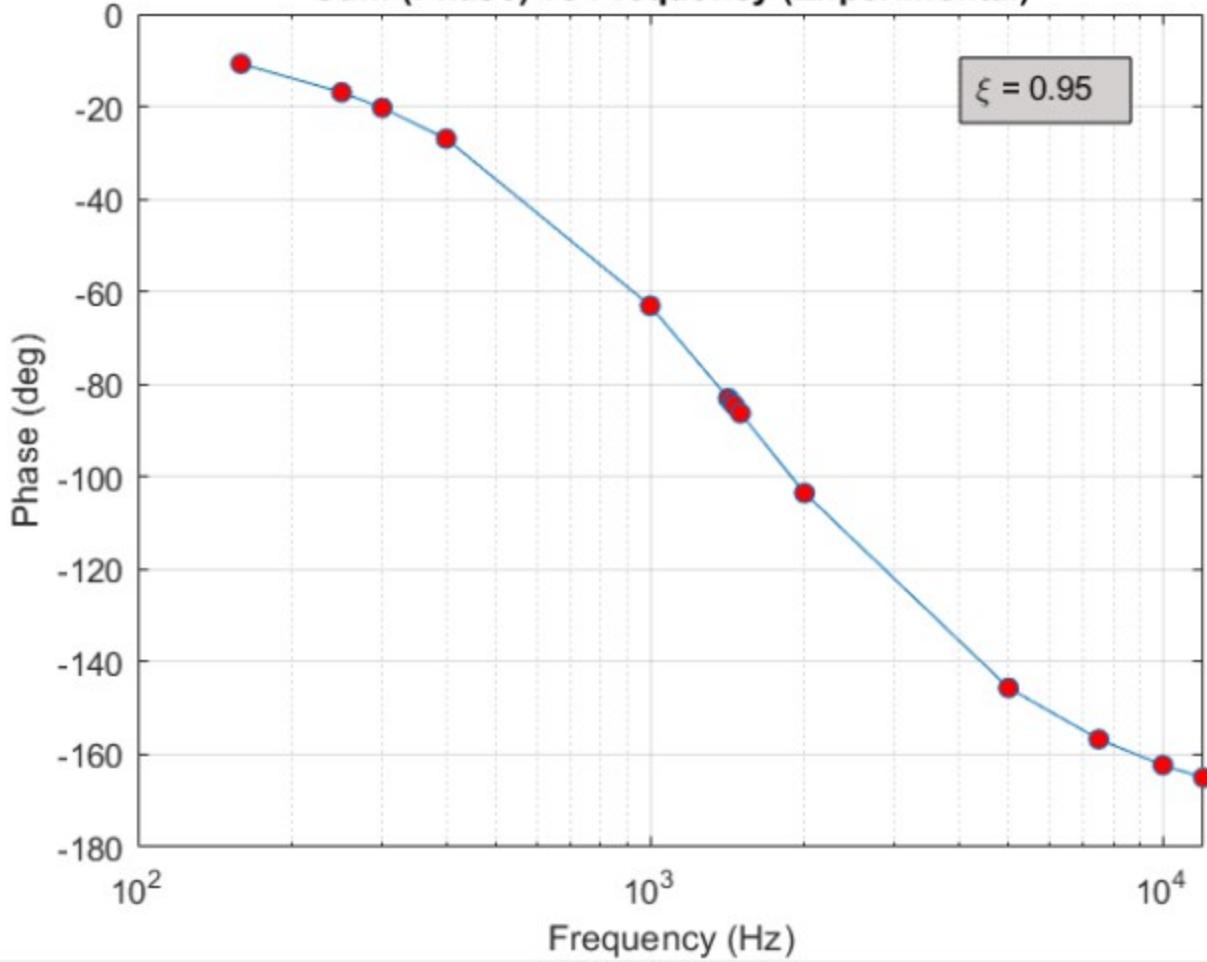

Gain (Phase) vs Frequency (Theoretical)

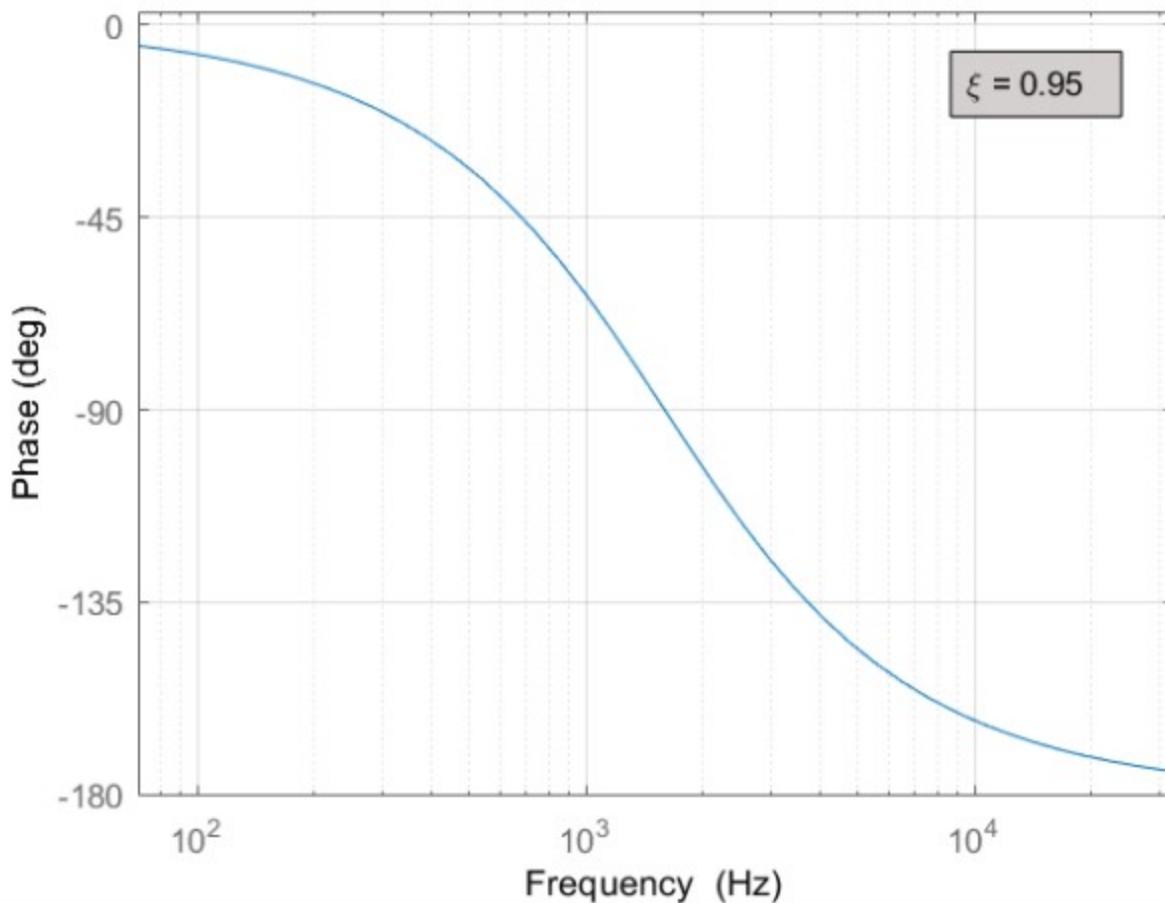


$$(4) g = 1.5 \quad (R = 3000 \Omega)$$

$$V_{in} = 5V$$


| Frequency (Hz) | V_c (V) | V_L (V) | V_R (V) | Gain (magnitude) (V_c/V_{in}) | Gain (phase) (degree) |
|-------------------|--------------|--------------|--------------|--------------------------------------|--------------------------|
| 100 | 4.920 | 0.020 | 0.931 | 0.987 | -10.640 |
| 150 | 4.829 | 0.048 | 1.449 | 0.967 | -16.780 |
| 250 | 4.612 | 0.114 | 2.176 | 0.924 | -25.710 |
| 300 | 4.471 | 0.159 | 2.533 | 0.895 | -30.300 |
| 400 | 4.147 | 0.263 | 3.139 | 0.832 | -38.760 |
| 1000 | 2.522 | 0.999 | 4.762 | 0.505 | -72.100 |
| 1420 | 1.859 | 1.486 | 4.986 | 0.372 | -85.440 |
| 1441 | 1.833 | 1.509 | 4.989 | 0.367 | -86.020 |
| 1460 | 1.810 | 1.530 | 4.992 | 0.363 | -86.480 |
| 1500 | 1.763 | 1.573 | 4.996 | 0.353 | -87.540 |
| 2000 | 1.308 | 2.074 | 4.941 | 0.262 | -98.480 |
| 5000 | 0.385 | 3.818 | 3.635 | 0.077 | -133.000 |
| 7500 | 0.195 | 4.360 | 2.767 | 0.039 | -146.000 |
| 10000 | 0.116 | 4.610 | 2.192 | 0.023 | -153.400 |
| 12000 | 0.082 | 4.719 | 1.870 | 0.017 | -157.400 |

* EXPERIMENTAL AND THEORETICAL FREQUENCY
RESPONSE PLOTS ATTACHED BELOW

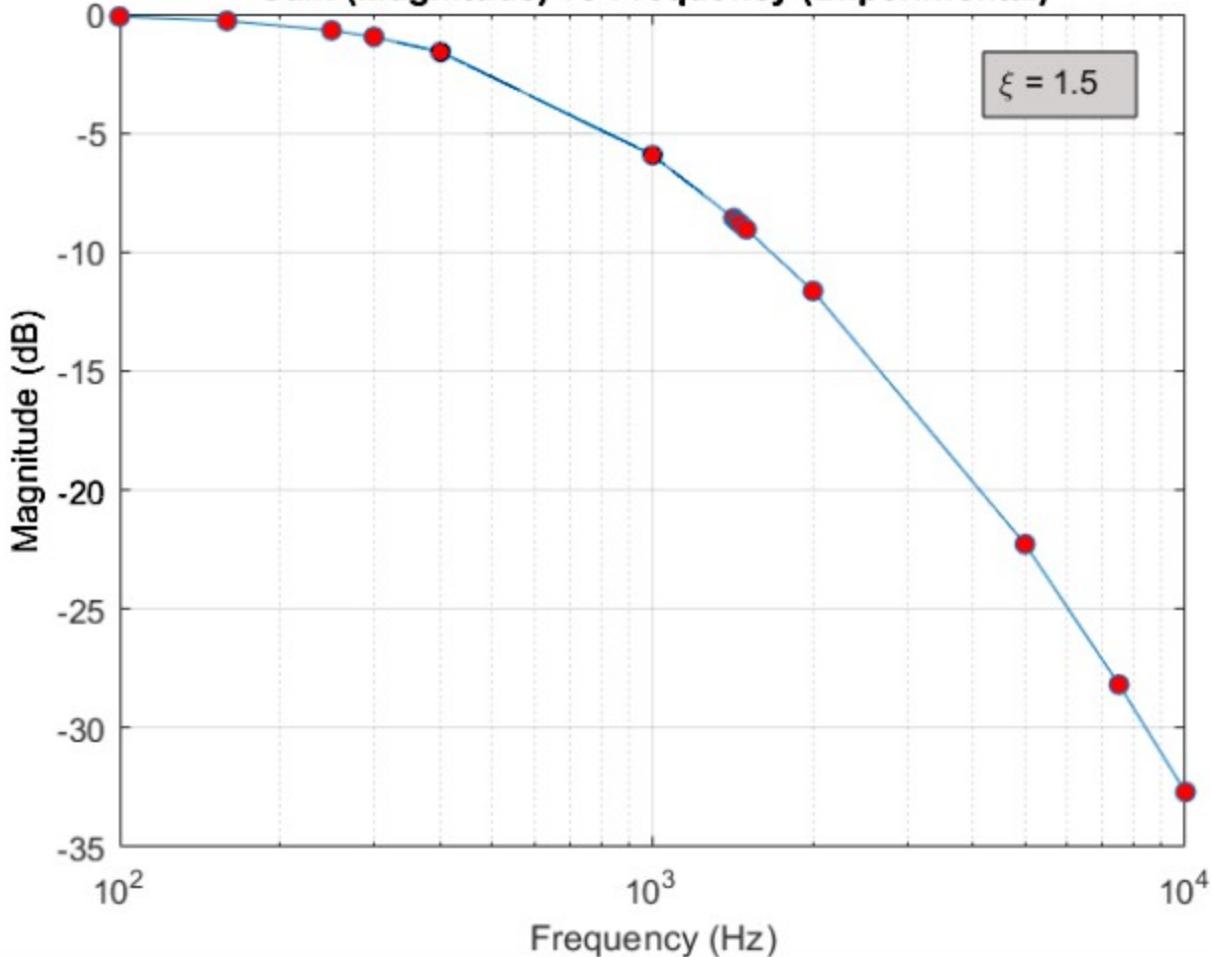
Gain (Magnitude) vs Frequency (Experimental)



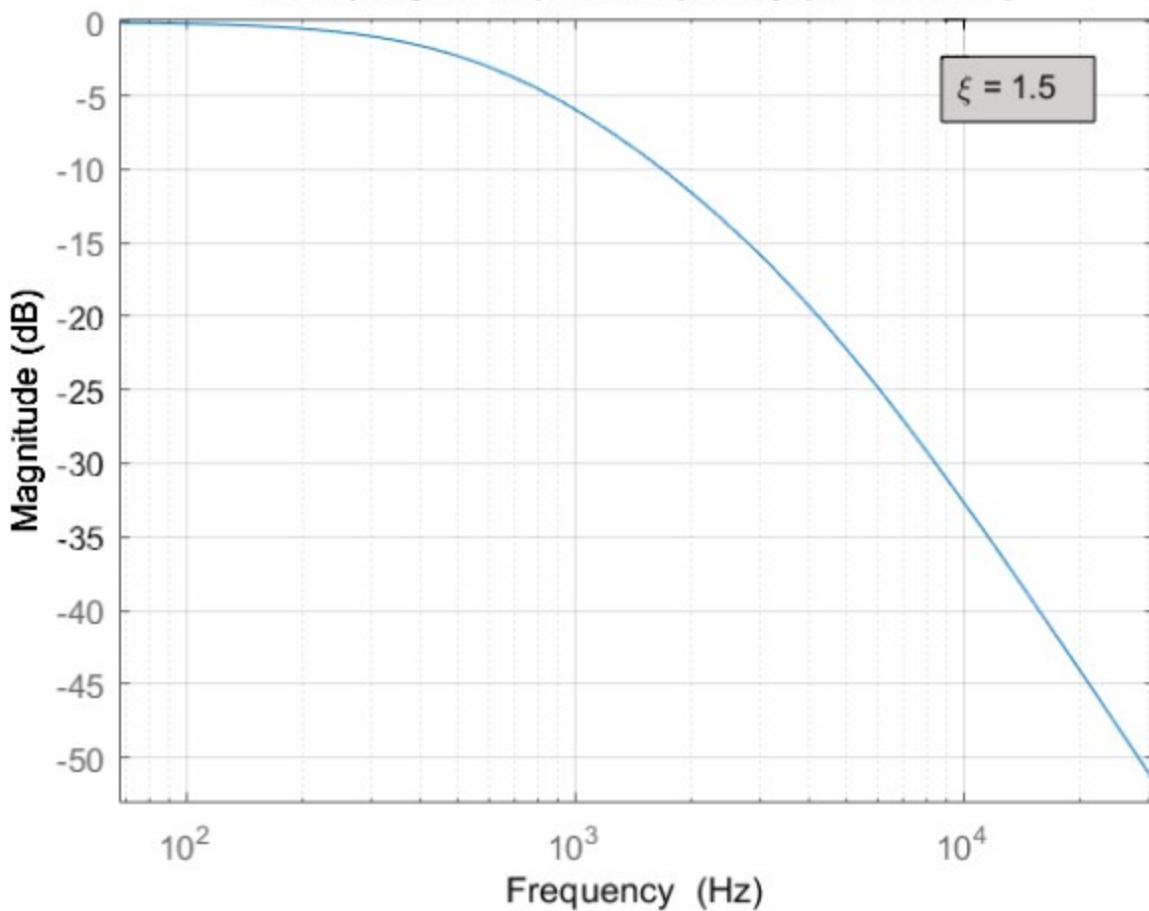
Gain (Magnitude) vs Frequency (Theoretical)



Gain (Phase) vs Frequency (Experimental)

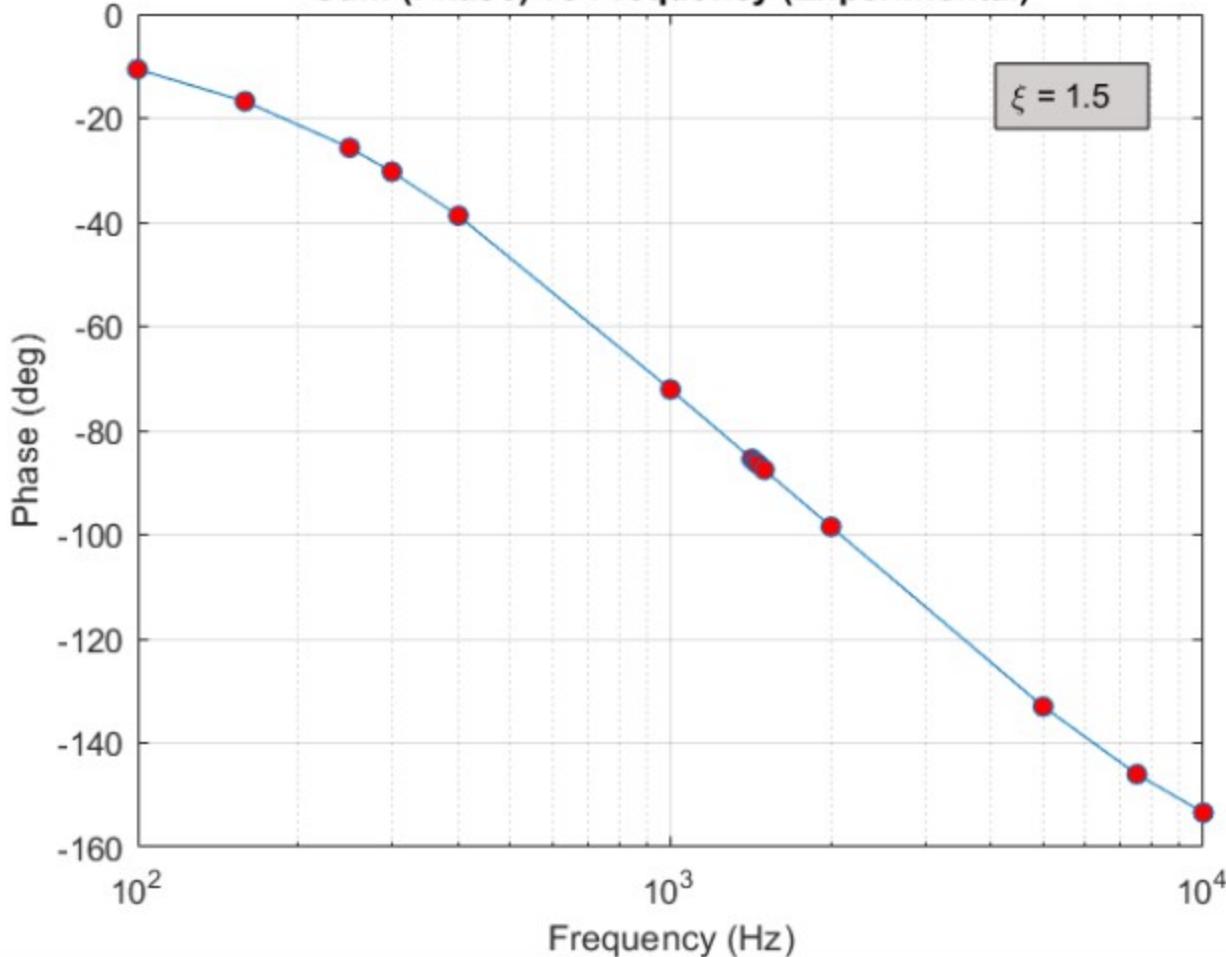

Gain (Phase) vs Frequency (Theoretical)

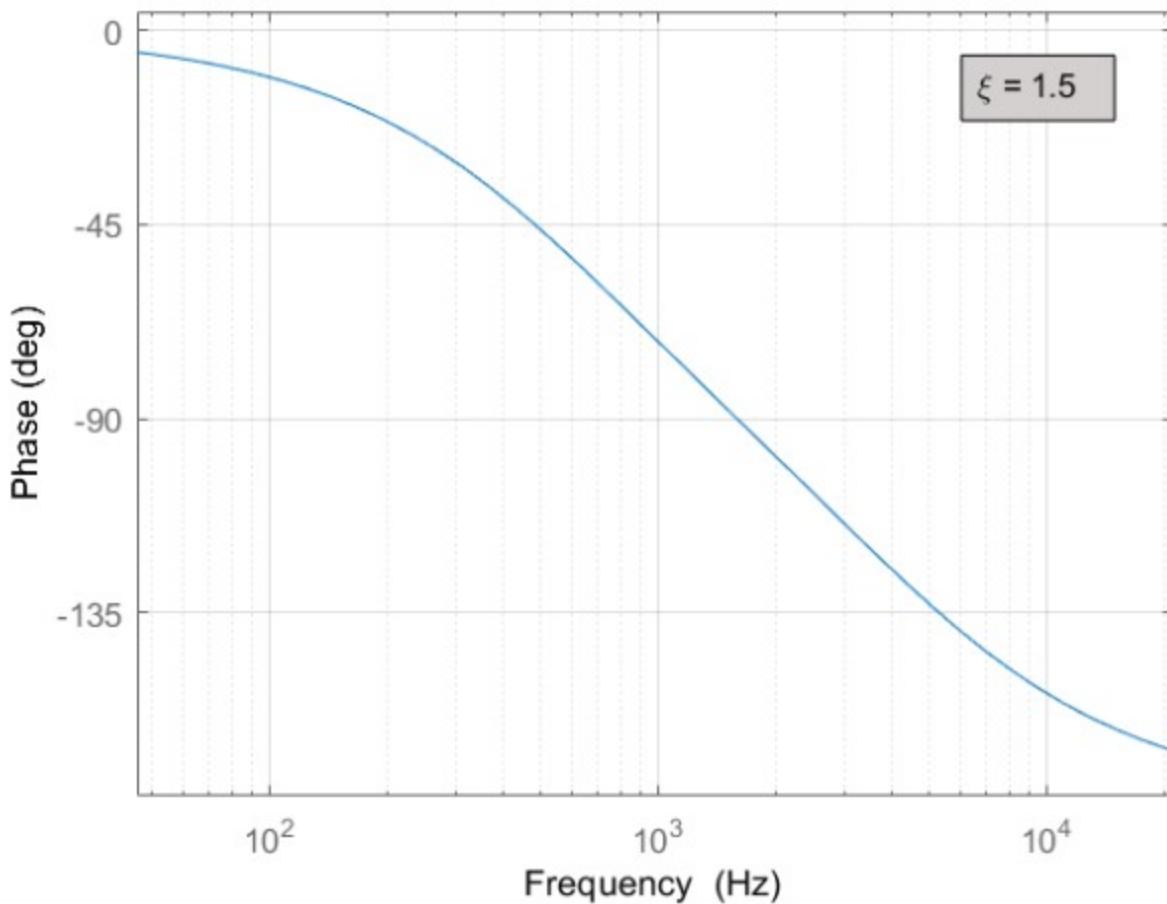

CALCULATIONS

NISARG UPADHYAYA
19CS30031 Nisarg.

$$L = 0.1 \text{ H}, C = 0.1 \mu\text{F} = 0.1 \times 10^{-6} \text{ F}$$

$$\omega_n = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^1 \times 10^{-7}}} = 10^4 \text{ rad/s}$$

$$2\xi\omega_n = \frac{R}{L} \Rightarrow R = (2L\omega_n)\xi = (2 \times 10^1 \times 10^4)\xi = (2000\xi)\Omega$$

① $\xi = 0.2 \Rightarrow R = (2000 \times 0.2) \Omega = 400 \Omega$

Experimental Meas. gain = 2.549
at $f_m = 1500 \text{ Hz}$

Theoretical Meas. gain = $\frac{1}{2\xi\sqrt{1-\xi^2}} = 2.552 \quad \left(\frac{1}{2 \times 0.2 \times \sqrt{1-0.04}} \right)$

at $f_m = \frac{1}{2\pi} \omega_n \sqrt{1-2\xi^2} = 1527 \text{ Hz} \quad \left(\frac{10^4}{2\pi} \times \sqrt{1-0.08} \right)$

$$\Rightarrow \% \text{ error (meas gain)} = \frac{|2.552 - 2.549|}{2.552} \times 100 = 0.12\%$$

$$\Rightarrow \% \text{ error } (f_m) = \frac{|1527 - 1500|}{1527} \times 100 = 1.77\%$$

② $\xi = 0.7 \Rightarrow R = (2000 \times 0.7) \Omega = 1400 \Omega$

Experimental Meas. gain = 1.000 at $f_m = 250 \text{ Hz}$

Theoretical Meas. gain = $\frac{1}{2\xi\sqrt{1-\xi^2}} = 1.000 \quad \left(\frac{1}{2 \times 0.7 \times \sqrt{1-0.49}} \right)$

at $f_m = \frac{1}{2\pi} \omega_n \sqrt{1-2\xi^2} = 225 \text{ Hz} \quad \left(\frac{10^4}{2\pi} \times \sqrt{1-0.98} \right)$

$$\Rightarrow \% \text{ error } (\underline{f_m}) = \frac{|225 - 250|}{225} \times 100 = 11.11\%$$

\Rightarrow The experimental meas gain is in agreement with the theoretical meas gain.

As the experiment has been carried out using simulation the measurement error reduces significantly. In real experiment the measuring devices have a certain error associated with them, also the precision of the readings is much higher in simulation compared to the real experiment.

Further, the signal generator and the passive components of the circuit are ideal and exact in simulation. In the real experiment there are bound to be certain fluctuations with the signal generator and the passive elements (R-L-C) are also non-ideal.

It can be observed that as the peak of the frequency response curve gets less and less sharp it becomes difficult to find the frequency at which the maximum gain occurs due to two reasons. For a wide range of frequency near the peak the gain remains almost constant. Also, the variation in gain is so less that it becomes experimentally difficult to observe it.

Frequency response analysis has important industrial applications in design of filters which are extensively used in audio and communication devices for attenuating noise from unwanted frequencies. It is also used in design of loudspeakers whereby it is important in determining the quality and loudness of sound over a wide range of frequency. A good speaker should have a high-response in the audible range (20-20K) Hz.