

EXPERIMENT 1 (B)

NISARG UPADHYAYA
19CS30031

RECIPROCITY THEOREM


⇒ AIM

Verification of reciprocity theorem.


⇒ THEORY

Consider a passive linear bilateral two-port network and two different types of connections.

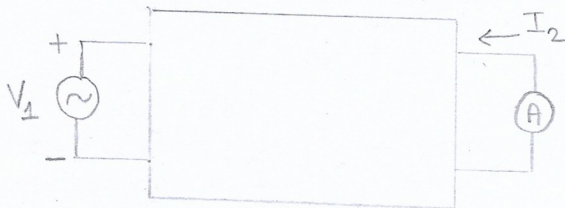① Voltage V_1 is applied across port 1 and current I_2 is measured at port 2



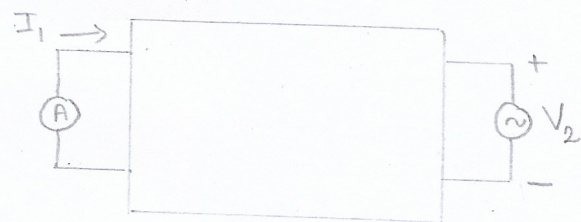② Voltage V_2 is applied across port 2 and current I_1 is measured at port 1



According to reciprocity theorem

$$\frac{I_1}{V_2} = \frac{I_2}{V_1}$$

⇒ OBSERVATION TABLE

V_s (V)	I_3 (A)	$\frac{V_s}{I_3}$ (V/A)	V_s' (V)	I_1' (A)	$\frac{V_s'}{I_1'}$ (V/A)
220	0.506	434.78	110	0.252	436.51

$$I_1 = 1.108 \text{ A}$$

$$I_2 = 0.570 \text{ A}$$

$$I_3 = 0.506 \text{ A}$$

$$I_4 = 0.538 \text{ A}$$

$$I_5 = 0.063 \text{ A}$$

$$I_1' = 0.252 \text{ A}$$

$$I_2' = 0.631 \text{ A}$$

$$I_3' = 0.805 \text{ A}$$

$$I_4' = 0.379 \text{ A}$$


$$I_5' = 0.174 \text{ A}$$


$$V_1 = 53.82 \text{ V}$$

$$V_2 = 25.32 \text{ V}$$

$$V_3 = 69.43 \text{ V}$$

$$V_4 = 37.87 \text{ V}$$

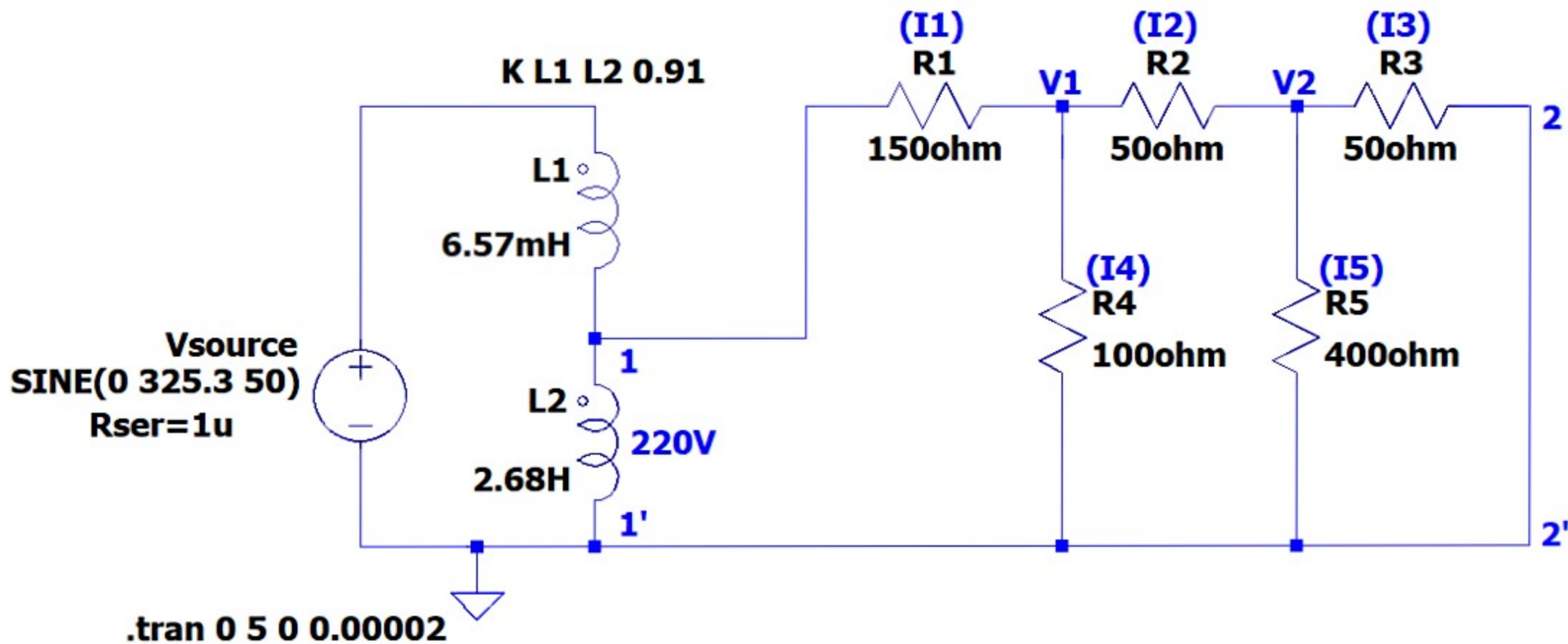

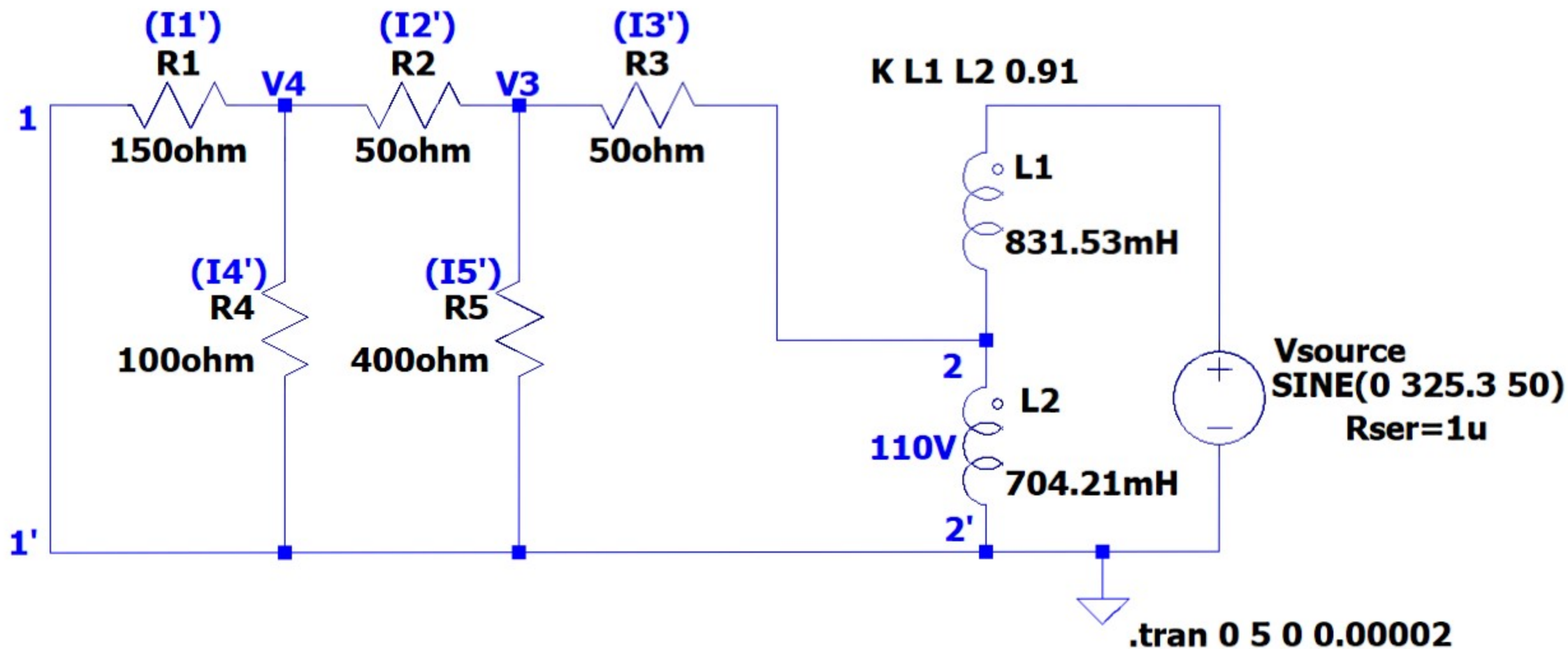

⇒ CALCULATIONS AND INFERENCE

$$\frac{V_s}{I_3} = \frac{220}{0.506} = 434.78 \text{ V/A} \quad , \quad \frac{V_{s'}}{I_1'} = \frac{110}{0.252} = 436.50 \text{ V/A}$$

It can be seen that $\frac{V_s}{I_3} \approx \frac{V_{s'}}{I_1'}$ which is in agreement with the reciprocity theorem.

⇒ DISCUSSION AND COMMENTS

Reciprocity theorem was successfully verified.

A direct consequence of the reciprocity theorem ($\frac{I_1}{V_2} = \frac{I_2}{V_1}$) is that if we take $V_1 = V_2$ then $I_1 = I_2$. In simple words if we have a voltage source V in branch 1 and a current I in branch 2 then we can say that placing the voltage source V in branch 2 will cause a current I to flow in branch 1, i.e., voltage and current are swapped.

One must always remember that reciprocity theorem can only be applied to passive linear bilateral networks only.