

Damping coefficient: ζ , Natural frequency: ω_n & Damped
natural frequency: ω_d

Tapas Kumar Bhattacharya

Department of Electrical Engineering
I.I.T Kharagpur

September 26, 2020

TAPAS

This is to be read as continuation to the previous lecture on the second order system.

1 R-L-C series circuit switched on to a DC voltage

Let the the circuit shown in figure is initially relaxed. At $t = 0$, DC voltage V is switched on. We want to find out voltage across the capacitor $v(t)$ and current $i(t)$ in the circuit for $t \geq 0$.

$$\text{KVL equation: } L \frac{di}{dt} + Ri + v = V$$

$$\text{Now, } i = C \frac{dv}{dt}$$

$$\text{so, } LC \frac{d^2v}{dt^2} + RC \frac{dv}{dt} + v = V$$

$$\text{or, } \frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{1}{LC} v = \frac{1}{LC} V$$

We shall replace the parameter values of the above equation by two new variables ω_n and ζ as follows:

$$\omega_n = \frac{1}{\sqrt{LC}}$$

$$\text{and } \frac{R}{L} = 2\zeta\omega_n$$

$$\text{New equation: } \frac{d^2v}{dt^2} + 2\zeta\omega_n \frac{dv}{dt} + \omega_n^2 v = V$$

It will be shown that the physical interpretation of the response can now be made in terms of ζ (called damping coefficient) and ω_n (called the undamped natural frequency of the system).

$$\text{characteristic equation: } m^2 + 2\zeta\omega_n m + \omega_n^2 = 0$$

$$\text{characteristic roots: } m_{1,2} = -\zeta\omega_n \pm \left(\sqrt{\zeta^2 - 1} \right) \omega_n$$

1.1 Case-1: when roots are complex

Roots will be complex if $\zeta < 1$ and can be written as:

$$m_{1,2} = -\zeta\omega_n \pm j \left(\sqrt{1 - \zeta^2} \right) \omega_n = -\zeta\omega_n \pm j\omega_d$$

$$\text{where, } \omega_d = \left(\sqrt{1 - \zeta^2} \right) \omega_n$$

$$\text{It may be noted: } \omega_d^2 + (\zeta\omega_n)^2 = \omega_n^2$$

$$\text{Defining } \tan \theta = \frac{\omega_d}{\zeta\omega_n}$$

The figure 1 is very handy to remember relationship among ω_n , $\zeta\omega_n$ and ω_d and the angle θ .

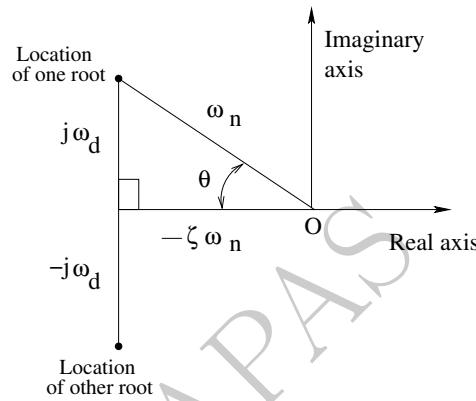


Figure 1

$$\therefore \text{ Natural response: } v_n(t) = Ae^{(-\zeta\omega_n + j\omega_d)t} + Be^{(-\zeta\omega_n - j\omega_d)t}$$

$$\text{forced response: } v_f(t) = V$$

$$\therefore v(t) = Ae^{(-\zeta\omega_n + j\omega_d)t} + Be^{(-\zeta\omega_n - j\omega_d)t} + V$$

$$\text{and } i(t) = C \frac{dv}{dt} = CA(-\zeta\omega_n + j\omega_d)e^{(-\zeta\omega_n + j\omega_d)t} + CB(-\zeta\omega_n - j\omega_d)e^{(-\zeta\omega_n - j\omega_d)t}$$

Now apply the initial conditions: $v(0^-) = v(0^+) = 0$ and $i(0^-) = i(0^+) = 0$ to generate the following two equations for getting constants A and B .

$$\begin{aligned} A + B &= -V \\ (-\zeta\omega_n + j\omega_d)A + (-\zeta\omega_n - j\omega_d)B &= 0 \end{aligned}$$

solving we get:

$$\begin{aligned} A &= \frac{j(\zeta\omega_n + j\omega_d)}{2\omega_d} V = Re^{j\theta} \text{ say} \\ \text{where } R &= \frac{\sqrt{(\zeta\omega_n)^2 + \omega_d^2}}{2\omega_d} V \text{ and } \theta = \tan^{-1} \frac{\omega_d}{\zeta\omega_n} + \frac{\pi}{2} \\ \text{and } B &= \frac{-j(\zeta\omega_n - j\omega_d)}{2\omega_d} V = A^* = Re^{-j\theta} \\ v(t) &= Re^{j\theta} e^{(-\zeta\omega_n + j\omega_d)t} + Re^{-j\theta} e^{(-\zeta\omega_n - j\omega_d)t} + V \\ \text{or, } v(t) &= Re^{-\zeta\omega_n t} [e^{j(\omega_d t + \theta)} + e^{-j(\omega_d t + \theta)}] V + V \\ \text{or, } v(t) &= 2Re^{-\zeta\omega_n t} \cos(\omega_d t + \theta) + V \end{aligned}$$

Putting values of R and θ from above:

$$\begin{aligned} \text{or, } v(t) &= \frac{\sqrt{(\zeta\omega_n)^2 + \omega_d^2}}{\omega_d} V e^{-\zeta\omega_n t} \cos\left(\omega_d t + \tan^{-1} \frac{\omega_d}{\zeta\omega_n} + \frac{\pi}{2}\right) + V \\ \text{or, } v(t) &= V - \frac{\sqrt{(\zeta\omega_n)^2 + \omega_d^2}}{\omega_d} V e^{-\zeta\omega_n t} \sin\left(\omega_d t + \tan^{-1} \frac{\omega_d}{\zeta\omega_n}\right) \\ \text{but } \omega_d^2 + (\zeta\omega_n)^2 &= \omega_n^2 \\ \therefore v(t) &= V - \frac{\omega_n}{\omega_d} V e^{-\zeta\omega_n t} \sin\left(\omega_d t + \tan^{-1} \frac{\omega_d}{\zeta\omega_n}\right) \\ \therefore v(t) &= V - \left(\frac{V}{\sqrt{1 - \zeta^2}}\right) e^{-\zeta\omega_n t} \sin\left(\omega_d t + \tan^{-1} \frac{\omega_d}{\zeta\omega_n}\right) \\ \therefore v(t) &= V - V_{\text{peak}} e^{-\zeta\omega_n t} \sin\left(\omega_d t + \tan^{-1} \frac{\omega_d}{\zeta\omega_n}\right) \\ \text{where: } V_{\text{peak}} &= \left(\frac{V}{\sqrt{1 - \zeta^2}}\right) \end{aligned}$$

The exponentially decaying sinusoidal terms will ultimately vanish and final voltage across the capacitor will be V . The amplitude of the sinusoid is being modulated by $e^{-\zeta\omega_n t}$. Figures 2 and 3 show respectively the step response of a second order system for $\zeta = 0.5$ and $\zeta = 0.3$. With lesser

value of ζ , the system becomes more oscillatory with higher value of overshoot.

For $\omega_n = 2$ & $\zeta = 0.5$

$$v(t) = 5 - 5.77e^{-t} \sin(1.732t + 60^\circ)$$

For $\omega_n = 2$ & $\zeta = 0.3$

$$v(t) = 5 - 5.24e^{-0.6t} \sin(1.91t + 72.54^\circ)$$

$$v(t) = 5 - 5.77e^{-t} \sin(1.732t + 60^\circ)$$

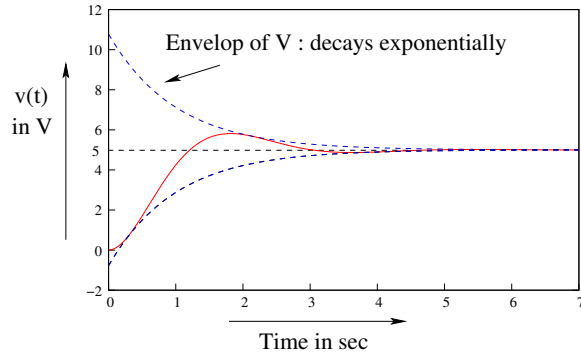


Figure 2: With $\zeta = 0.5$ & $\omega_n = 2$

$$v(t) = 5 - 5.24e^{-0.6t} \sin(1.91t + 72.54^\circ)$$

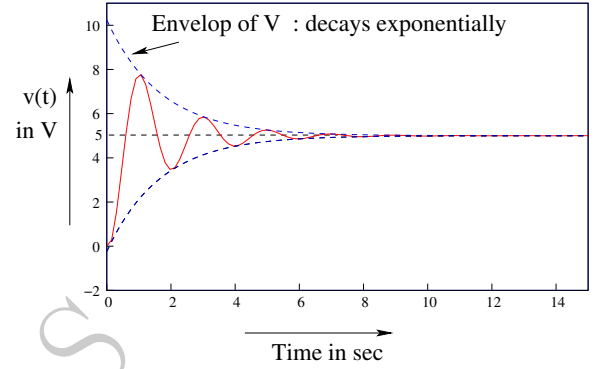


Figure 3: With $\zeta = 0.3$ & $\omega_n = 2$

1.2 Case-2: when roots are real and equal

We have:

$$\text{characteristic equation: } m^2 + 2\zeta\omega_n m + \omega_n^2 = 0$$

$$\text{characteristic roots: } m_{1,2} = -\zeta\omega_n \pm \left(\sqrt{\zeta^2 - 1}\right) \omega_n$$

$$\text{roots are equal if : } \zeta = 1$$

$$\text{characteristic roots: } m_1 = m_2 = -\zeta\omega_n = m$$

Therefore solution for $v(t)$ in this case will be:

$$\begin{aligned}
 v(t) &= (A + Bt)e^{-\zeta\omega_n t} + V \\
 \text{initial conditions: } v(0) &= V \text{ and } i(0) = 0 \text{ give} \\
 A + V &= 0 \text{ or } A = -V \\
 \text{and } -\zeta\omega_n A + B &= 0 \text{ or} \\
 \text{or } B &= -\zeta\omega_n V \\
 \therefore v(t) &= V - Ve^{-\zeta\omega_n t} - \zeta\omega_n Vte^{-\zeta\omega_n t} \\
 \text{current can be obtained from: } i(t) &= C \frac{dv}{dt}
 \end{aligned}$$

Here $v(t)$ will reach the final value of V without suffering any oscillation. Under this condition the system is said to be *critically damped*.

1.3 Case-3: when roots are real and distinct

We have:

$$\begin{aligned}
 \text{characteristic equation: } m^2 + 2\zeta\omega_n m + \omega_n^2 &= 0 \\
 \text{characteristic roots: } m_{1,2} &= -\zeta\omega_n \pm \left(\sqrt{\zeta^2 - 1}\right)\omega_n \\
 \text{roots are real and distinct if : } \zeta &> 1 \\
 \text{characteristic roots: } m_1 &= -\zeta\omega_n + \left(\sqrt{\zeta^2 - 1}\right)\omega_n \\
 \text{and } m_2 &= -\zeta\omega_n - \left(\sqrt{\zeta^2 - 1}\right)\omega_n \\
 \text{Note: } m_1 &> m_2 \\
 \text{and } m_1 - m_2 &= 2\sqrt{\zeta^2 - 1}
 \end{aligned}$$

Therefore solution for $v(t)$ in this case, will be:

$$\begin{aligned}
 v(t) &= Ae^{m_1 t} + Be^{m_2 t} + V \\
 \text{initial conditions: } v(0) &= V \text{ and } i(0) = 0 \text{ give} \\
 A + B + V &= 0 \text{ or } A + B = -V \\
 \text{and } m_1 A + m_2 B &= 0 \\
 \text{Solving, we get: } A &= \frac{m_2 V}{(m_1 - m_2)} \\
 \text{and } B &= -\frac{m_1 V}{(m_1 - m_2)} \\
 \therefore v(t) &= \frac{m_2 V}{(m_1 - m_2)} e^{m_1 t} - \frac{m_1 V}{(m_1 - m_2)} e^{m_2 t} + V \\
 \text{or, } v(t) &= V + \frac{-\zeta \omega_n - \left(\sqrt{\zeta^2 - 1}\right) V}{2\sqrt{\zeta^2 - 1}} e^{(-\zeta \omega_n + \sqrt{\zeta^2 - 1} \omega_n)t} \\
 &\quad - \frac{-\zeta \omega_n + \left(\sqrt{\zeta^2 - 1}\right) \omega_n V}{2\sqrt{\zeta^2 - 1}} e^{(-\zeta \omega_n - \sqrt{\zeta^2 - 1} \omega_n)t}
 \end{aligned}$$

current can be obtained from: $i(t) = C \frac{dv}{dt}$