

**Answer ALL the questions on the question paper itself in the spaces provided.
Do all rough work on on the blank page included in the questions paper.**

1. Consider the following incompletely specified finite state machine.

PS	NS,z			
	I_1	I_2	I_3	I_4
A	B,0	—,—	—,—	E,1
B	A,0	C,—	—,—	—,—
C	C,0	A,1	D,1	E,—
D	—,—	B,—	—,—	A,—
E	C,—	B,1	F,—	—,0
F	F,1	A,—	E,—	B,—

- (a) Minimise the above FSM showing the steps 10
- (b) Choose a state and input encoding for the minimised states 5
- (c) Construct the optimised next state and the output functions for the minimised FSM for the chosen state encoding 5×3
- (d) The minimised FSM has to be realised using JK flip flops; construct the required excitation functions for the flip flops 5×2

