


EXPERIMENT 3 (2)

NISARGI UPADHYAYA
19CS30031 Niraj.

OBJECTIVE

Experimental verification of Fourier Coefficients of a square wave signal using passive network.

CIRCUIT DIAGRAM

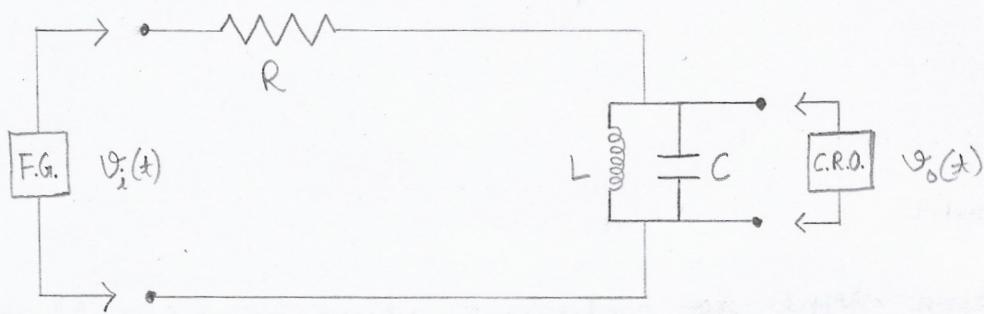

THEORY

FOURIER THEOREM: A periodic signal can be written as a sum of sine and cosine waves.

$$x(t) = a_0 + \sum_{n=1}^{\infty} a_n \cos(nwt) + \sum_{n=1}^{\infty} b_n \sin(nwt)$$

$$a_0 = \frac{1}{T} \int x(t) dt$$


$$a_n = \frac{2}{T} \int x(t) \cos(nwt) dt \quad \forall n=1, 2, 3, \dots$$

$$b_n = \frac{2}{T} \int x(t) \sin(nwt) dt \quad \forall n=1, 2, 3, \dots$$

If $x(t)$ is even, $b_n = 0 \quad \forall n$.

If $x(t)$ is odd, $a_n = 0 \quad \forall n$.

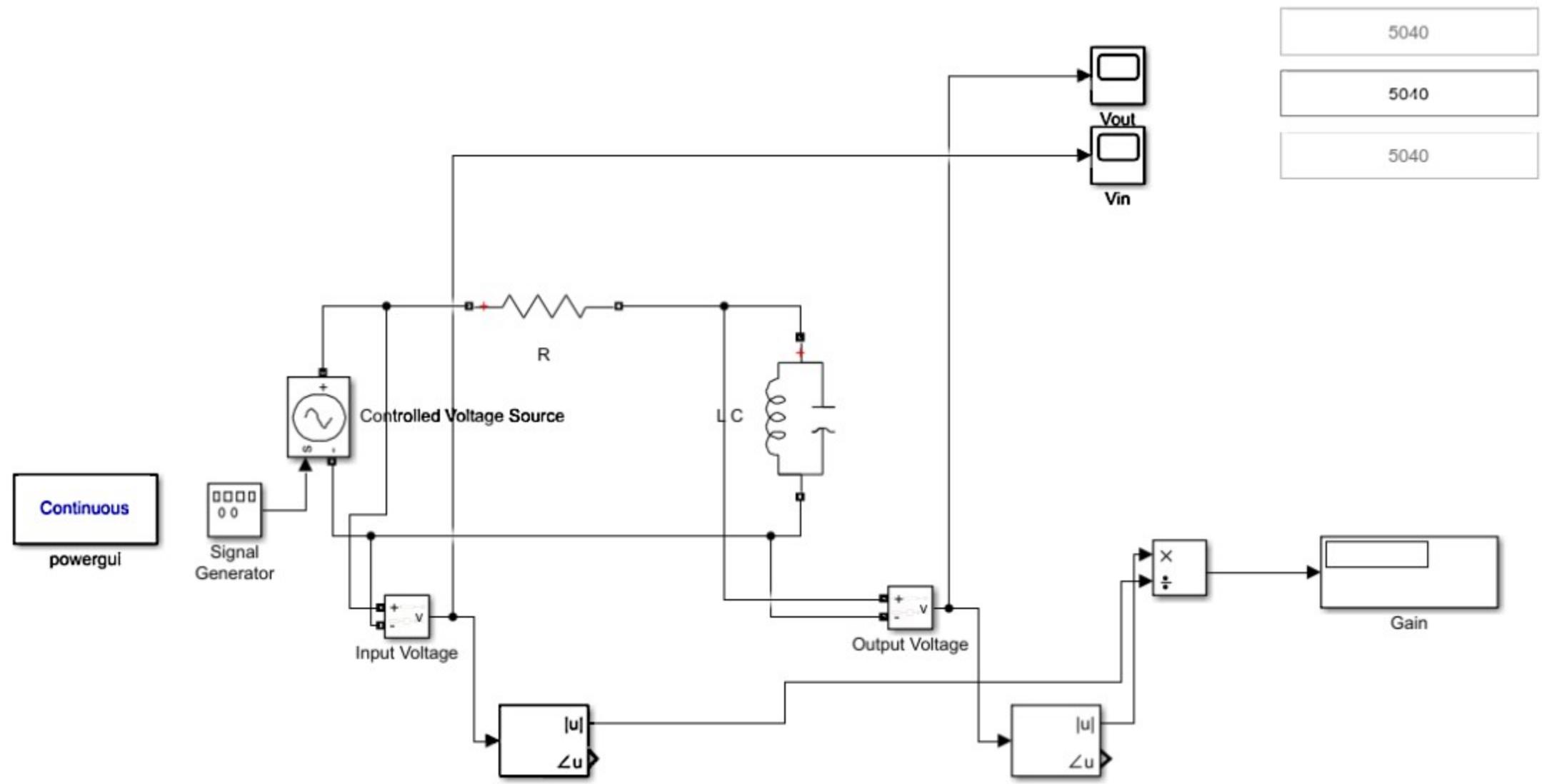If $x(t)$ is half wave symmetric $a_0 = 0$
 $a_n = b_n = 0 \quad \forall \text{ even } n$.



- | | | |
|-----------------------------|-----------|-------------|
| ① Signal Generator | ⑥ Fourier | ⑪ Edit |
| ② Controlled Voltage Source | ⑦ Divide | ⑫ power GUI |
| ③ Series RLC branch | ⑧ Add | |
| ④ Parallel RLC branch | ⑨ Display | |
| ⑤ Voltage measurement | ⑩ Scope | |

PART 1

SIMULINK PROCEDURE

- ① Set the simulation type to continuous using powerGUI block
- ② Set the solver to ode23t in model configuration parameters
- ③ Set the wave form to sine and amplitude to 3V in signal generator.
- ④ Set the frequency of signal generator and Fourier blocks to 100Hz using edit block and run the simulation.
- ⑤ Measure V_{out} using scope and gain will be visible on display too.
- ⑥ Repeat steps 4-5 for different frequencies from 100Hz to 100 KHz (uniformly distributed).
- ⑦ Plot the approximate frequency response on a semi log plot using MATLAB and compare with theoretical plot.

CALCULATIONS

For the given circuit, $V_{out}(s) = I(s) \times \left(L_s \parallel \frac{1}{C_s} \right)$

$$\text{and } I(s) = \frac{V_{in}(s)}{R + \left(L_s \parallel \frac{1}{C_s} \right)}$$

$$\therefore \text{We have the transfer function } G(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{\left(L_s \parallel \frac{1}{C_s} \right)}{R + \left(L_s \parallel \frac{1}{C_s} \right)}$$

$$G(s) = \frac{Ls \cdot \frac{1}{Cs}}{Ls + \frac{1}{Cs}}$$

$$R + \frac{Ls \cdot \frac{1}{Cs}}{Ls + \frac{1}{Cs}}$$

$$G(s) = \frac{\frac{L}{C}}{RLs + \frac{R}{Cs} + \frac{L}{C}}$$

$$G(s) = \frac{Ls}{RLCs^2 + Ls + R}$$

For $L = 10\text{mH}$, $R = 100\text{k}\Omega$, $C = 100\text{nF}$

$$G(s) = \frac{10^{-2}s}{10^{-4}s^2 + 10^{-2}s + 10^5}$$

* OBSERVATION TABLE AND PLOTS

ATTACHED BELOW

OBSERVATION TABLEV_{in} = 3V


NISARG UPADHYAYA

19CS30031


Nisarg/

Frequency (Hz)	Output Amplitude (V)	Gain Magnitude	Magnitude (in dB)
100	0.0002	0.0001	-84.0574
500	0.0010	0.0003	-69.9761
1000	0.0020	0.0007	-63.6858
2500	0.0063	0.0021	-53.5929
5000	0.6738	0.2246	-12.9718
7500	0.0115	0.0038	-48.3451
10000	0.0060	0.0020	-53.9231
25000	0.0021	0.0007	-63.2989
50000	0.0010	0.0003	-69.8483
100000	0.0005	0.0002	-75.9393

Frequency Response (Experimental)

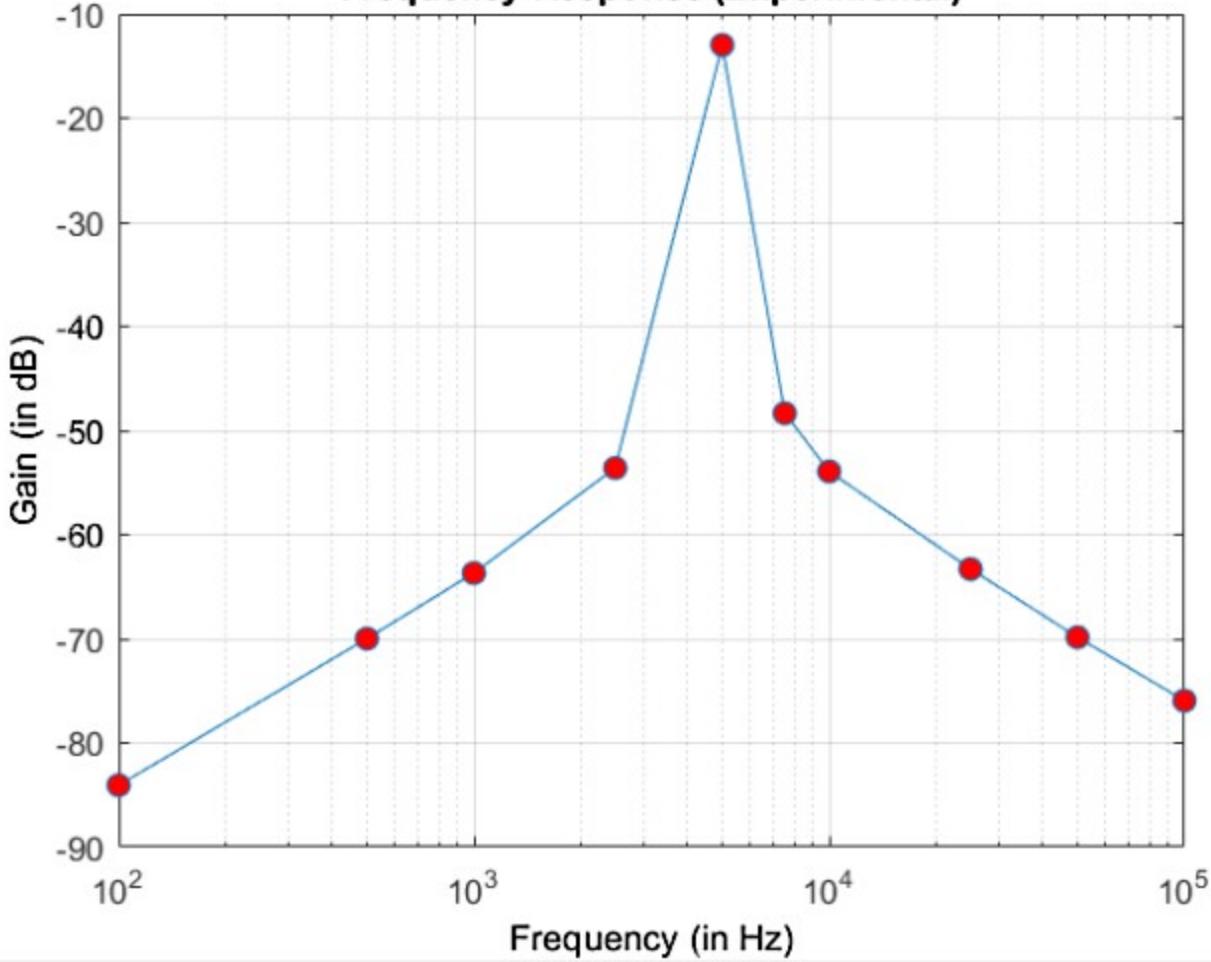

Frequency Response (Theoretical)

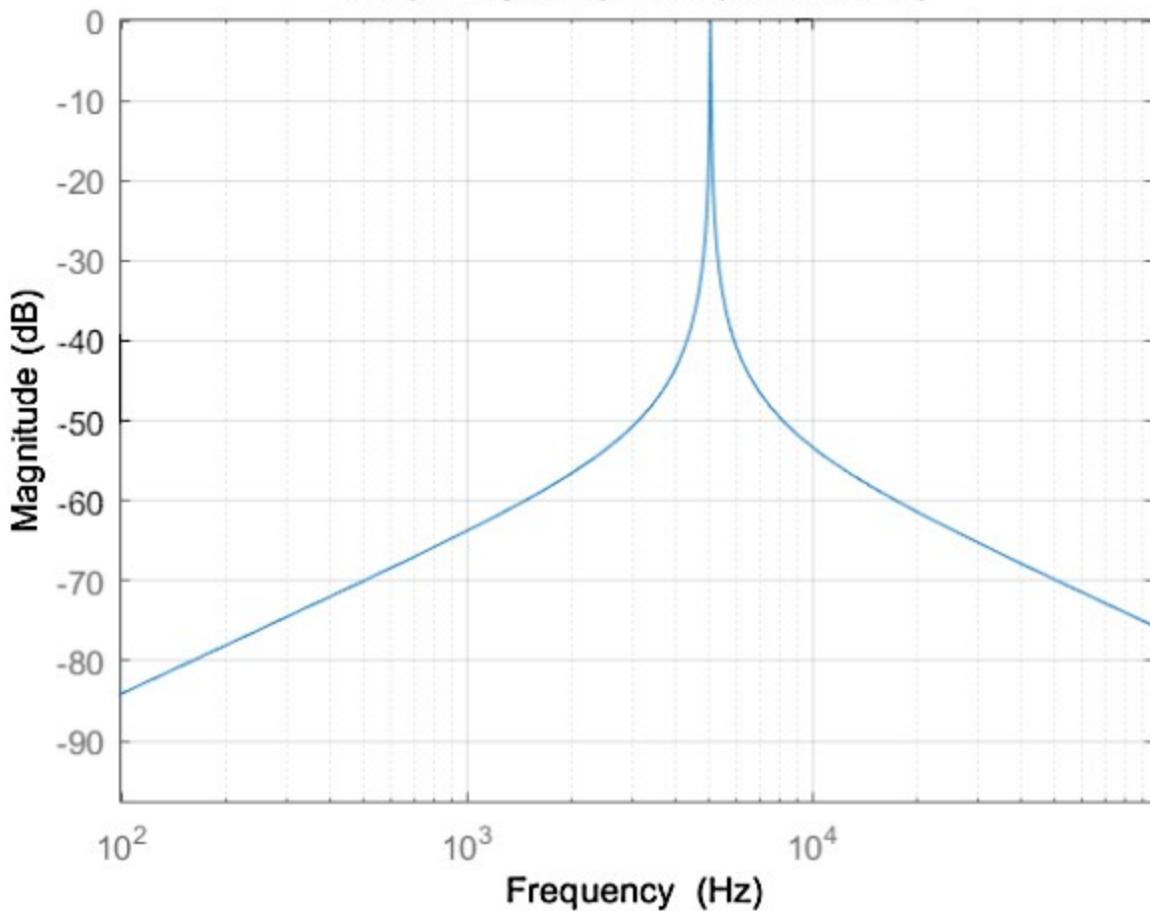

PART 2

NISARGI UPADHYAYA
19CS30031 Nisarg.

SIMULINK PROCEDURE

- ① Set the waveform to square and amplitude to 3V in signal generator.
- ② Set the frequency near the resonance frequency of the circuit (i.e., around 5 kHz).
- ③ Fine tune the frequency using the edit block and run the simulation for different frequencies.
- ④ Using scope measure the amplitude of $v_o(t)$ and fine tune to get the frequency at which the amplitude becomes highest.
- ⑤ Repeat steps 3-4 for different combinations of L & C (keeping the resonance frequency same, i.e., $LC = \text{constant}$).
- ⑥ The highest amplitude of $v_o(t)$ is the fundamental Fourier series coefficient.

OBSERVATION TABLE

Frequency (Hz)	Output Amplitude (V)		
	$L=10\text{mH}, C=100\text{nF}$	$L=20\text{mH}, C=50\text{nF}$	$L=100\text{mH}, C=10\text{nF}$
5000	0.940	1.594	3.560
5010	1.220	2.142	3.690
5020	1.880	2.868	3.760
5030	3.410	3.704	3.811
5032	3.689	3.780	3.814
5033	3.755	3.792	3.816
5034	3.757	3.794	3.820
5035	3.697	3.780	3.818
5036	3.590	3.753	3.810
5040	2.457	3.523	3.806

CALCULATIONS

NISARG UPADHYAYA
19CS30031 Nisarg..

Frequency at which max amplitude occurs = 5034 Hz

$$\text{Average max amplitude} = \frac{(3.757 + 3.794 + 3.820)}{3} = 3.790 \text{ V}$$

$(V_o(t))$

This is the fundamental fourier series coefficient of the square wave signal. $\Rightarrow b_1 (\text{experimental}) = 3.79$

$$\begin{aligned}
 b_1 (\text{theoretical}) &= \frac{2}{T} \int_{-\frac{T}{2}}^{\frac{T}{2}} x(t) \sin(\omega t) dt \\
 &= \frac{2}{T} \left[3 \int_0^{\frac{T}{2}} \sin(\omega t) dt - 3 \int_{\frac{T}{2}}^T \sin(\omega t) dt \right] \\
 &= \frac{2}{T} \left[6 \int_0^{\frac{T}{2}} \sin(\omega t) dt \right] \\
 &= \frac{12}{T} \left[\frac{-\cos(\omega t)}{\omega} \right]_0^{\frac{T}{2}} \\
 &= \frac{12}{\left(\frac{2\pi}{\omega} \right)} \times \left(\frac{2}{\omega} \right) = \frac{12}{\pi} = 3.82
 \end{aligned}$$

$$\therefore \% \text{ error} = \frac{|3.82 - 3.79|}{3.82} \times 100 = 0.74\%$$


SIMULINK PROCEDURE

- ① To get the third harmonic fourier series coefficient fine tune the circuit as done in PART 2 but this time around one third the resonance frequency (i.e., around 1670 Hz).
- ② For this case the output amplitude varies periodically. When the amplitude of $v_o(t)$ is highest open its scope and turn on "cursor measurements". Zoom in to a suitable time interval and measure the amplitudes at consecutive maxima and minima to get the average amplitude of $v_o(t)$.
- ③ This is the third harmonic fourier series coefficient.
- ④ Repeat the above steps around one fifth the resonance frequency (i.e., around 1 kHz) to get the fifth harmonic coefficient.

OBSERVATION TABLEFOR 3rd HARMONIC

Frequency (Hz)	Output Amplitude (V)	At $f = 1678 \text{ Hz}$			
		No.	MAXIMA	MINIMA	PEAK TO PEAK (MAX-MIN)
1660	0.21				
1670	0.41				
1675	0.90				
1676	1.02	1	1.172	-1.215	2.387
1677	1.19	2	1.245	-1.204	2.449
1678	1.24	3	1.187	-1.240	2.427
1679	1.17				* PLOT ATTACHED BELOW
1680	1.00				
1690	0.29				


Vout for f=1678Hz

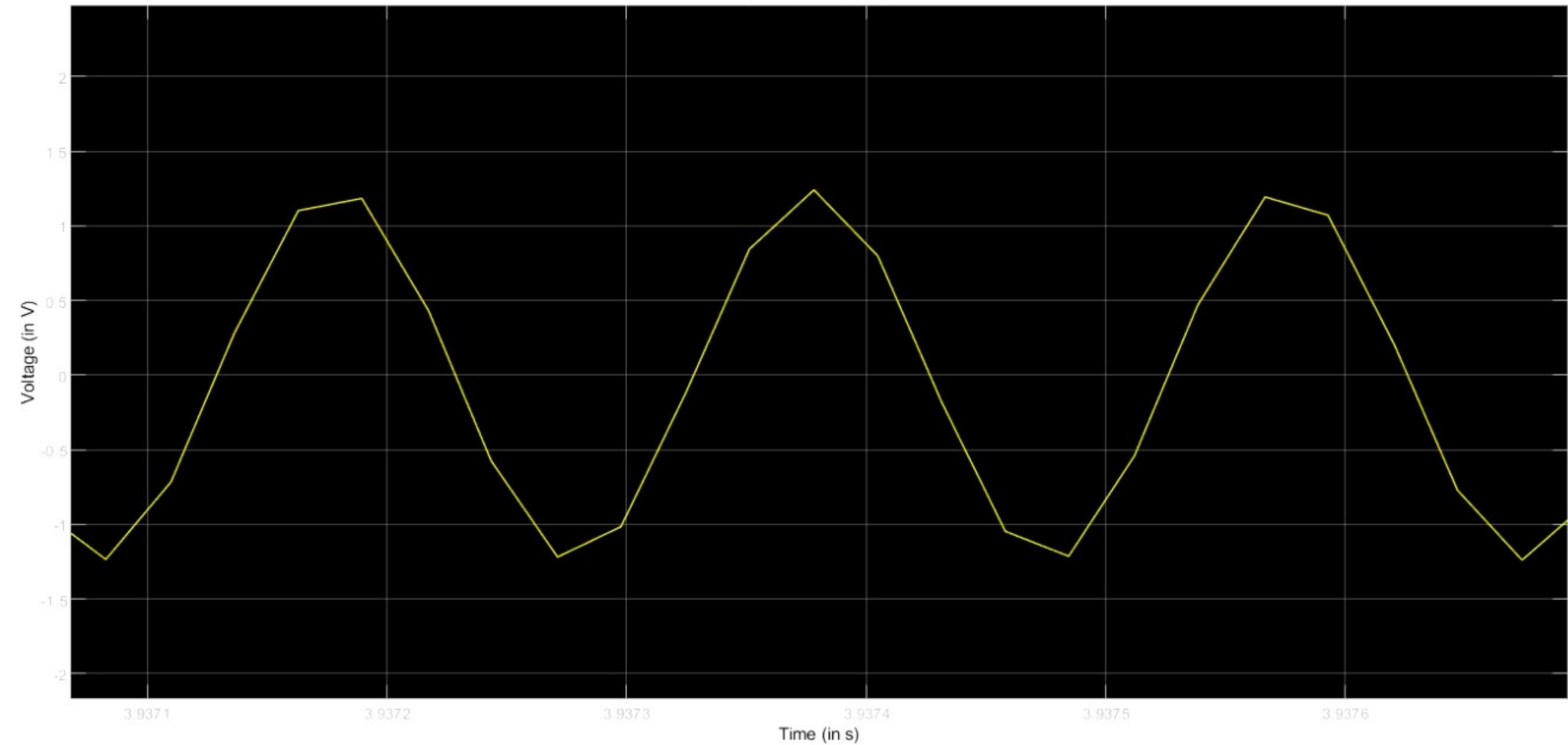

FOR 5th HARMONIC

Frequency (Hz)	Output Amplitude (V)	At $f = 1007 \text{ Hz}$			
		Sr.	Amplitude (V)	PEAK TO PEAK (MAX-MIN)	
		No.	MAXIMA	MINIMA	
1000	0.26				
1005	0.56				
1006	0.69	1	0.715	-0.738	1.453
1007	0.74	2	0.716	-0.692	1.408
1008	0.63	3	0.743	-0.725	1.468
1009	0.45	4	0.689	-0.721	1.410
1010	0.42	5	0.725	-0.719	1.444
1020	0.09			* PLOT ATTACHED BELOW	

Vout for f=1007Hz

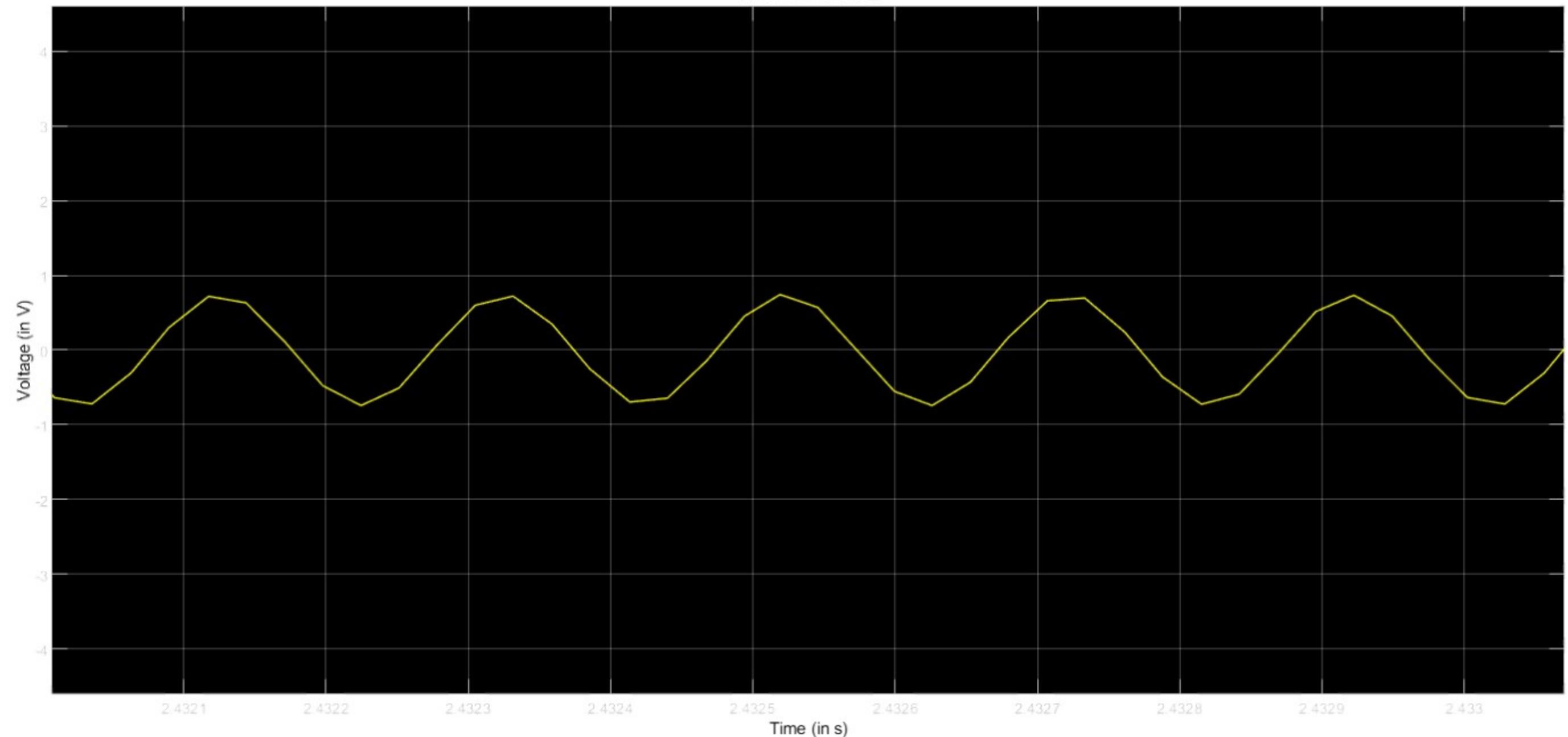

CALCULATIONS

NISARG UPADHYAYA
19CS30031 Nisarg.

① 3rd

HARMONIC

Frequency at which max amplitude occurs = 1678 Hz

$$\text{Average max amplitude (PEAK-TO-PEAK)} = \frac{(2.387 + 2.449 + 2.427)}{3} = 2.421$$

$$\text{Average max amplitude} = \frac{\text{PEAK-TO-PEAK}}{2} = \frac{2.421}{2} = 1.211$$

This is the third harmonic fourier series coefficient of the square wave signal. $\Rightarrow b_3(\text{experimental}) = 1.21$

$$\begin{aligned}
 b_3(\text{theoretical}) &= \frac{2}{T} \int_{(T)} x(t) \sin(3\omega t) dt \\
 &= \frac{2}{T} \left[3 \int_0^{\frac{T}{2}} \sin(3\omega t) dt - 3 \int_{\frac{T}{2}}^T \sin(3\omega t) dt \right] \\
 &= \frac{2}{T} \left[6 \int_0^{\frac{T}{2}} \sin(3\omega t) dt \right] \\
 &= \frac{12}{T} \left[\frac{-\cos(3\omega t)}{3\omega} \right]_0^{\frac{T}{2}} \\
 &= \frac{4}{\left(\frac{2\pi}{\omega}\right)} \times \left(\frac{2}{\omega}\right) = \frac{4}{\pi} = 1.27
 \end{aligned}$$

$$\therefore \% \text{ error} = \frac{|1.27 - 1.21|}{1.27} \times 100 = 4.72 \%$$

(2) 5th HARMONIC

NISARG UPADHYAYA
19CS30031 Nisarg.

Frequency at which max amplitude occurs = 1007 Hz

Average max amplitude (PEAK-TO-PEAK) = $\frac{(1.453 + 1.408 + 1.468 + 1.410 + 1.444)}{5}$
~~Max = (Peak + Peak) / 2 (as it is a square wave)~~

$$= 1.437$$

Average max amplitude = $\frac{\text{PEAK-TO-PEAK}}{2} = \frac{1.437}{2} = 0.718$

This is the fifth harmonic fourier series coefficient of the square wave signal. $\Rightarrow b_5(\text{experimental}) = 0.72$

$$\begin{aligned} b_5(\text{theoretical}) &= \frac{2}{T} \int_{(T)} x(t) \sin(5\omega t) dt \\ &= \frac{2}{T} \left[3 \int_0^{\frac{T}{2}} \sin(swt) - 3 \int_{\frac{T}{2}}^T \sin(swt) dt \right] \\ &= \frac{2}{T} \left[6 \int_0^{\frac{T}{2}} \sin(swt) dt \right] \\ &= \frac{12}{T} \cdot \frac{[-\cos(swt)]_0^{\frac{T}{2}}}{5\omega} \\ &= \frac{12}{\left(\frac{2\pi}{\omega}\right)} \times \left(\frac{2}{5\omega}\right) = \frac{12}{5\pi} = 0.76 \end{aligned}$$

% error = $\frac{|0.76 - 0.72|}{0.76} \times 100 = 5.26\%$

DISCUSSION

NISARG UPADHYAYA
19CS30031 Nitrogy.

Experimentally there will always be error in the coefficients obtained and their theoretical values because even after fine tuning the circuit there will be a small difference between the input frequency and the resonating frequency of the circuit. Also it is very difficult to generate an ideal square wave signal. The transition from +ve to -ve amplitude in reality always takes a small finite amount of time.

As the experiment has been carried out through simulation the circuit elements are ideal and the signal generator generates a stable input waveform which is not the case in the real experiment in lab. However, even in the simulation care should be taken that the time step is set according to the frequency at which we are operating to get accurate readings.

Fourier series have a wide range of applications in field such as signal processing, approximation theory (used to approximate signals / functions as polynomials of sine and cosine) and also for audio compression. The fact that Fourier series converge quite fast helps in storing data of signals in a finite and compact memory space.