

# Maximum Power Transfer Theorem

Department of Electrical Engineering  
Indian Institute of Technology Kharagpur

Autumn 2020

**Objective:** Verification of Maximum Power Transfer theorem.

## 1 Theory

Maximum power is transferred from a source of given voltage and an initial impedance to the load impedance  $Z_L = R_L + jX_L$  in a circuit (Figure 1) under three different conditions.

### 1.1 When only $X_L$ is adjustable

Under this condition the power consumed by the load ( $I^2 R_L$ ) is maximum, when  $I$  the RMS current is maximum, since  $R_L$  is constant.

$$I = \frac{V_s}{(R_i + jX_i) + (R_L + jX_L)} \quad (1)$$

$$\Rightarrow |I|_{max} = \frac{V_s}{R_i + R_L} \text{ when } X_L = -X_i. \quad (2)$$

This means that if the load reactance  $X_L$  is made equal in magnitude and opposite in sign to the internal reactance  $X_i$ , the power transferred is maximum.

### 1.2 When only $R_L$ is adjustable:

From Equation 1 in Section 1.1, one may write,

$$\begin{aligned} P &= |I|^2 R_L \\ &= \frac{V_s^2 R_L}{(R_i + R_L)^2 + (X_i + X_L)^2}. \end{aligned} \quad (3)$$

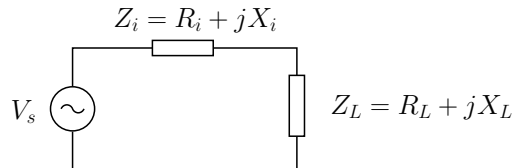


Figure 1: Circuit 1.

Differentiating Equation 3 *w.r.t.*  $R_L$  and equating to zero, one obtains,

$$R_L = \sqrt{R_i^2 + (X_i + X_L)^2}. \quad (4)$$

### 1.3 When both $R_L$ and $X_L$ are adjustable:

Under this condition, both Equations 2 and 4 are valid simultaneously and one obtains,

$$R_L = R_i, X_L = -X_i. \quad (5)$$

## 2 Procedure

### 2.1 First Part

1. Take a suitable set of values of  $V_s$ ,  $R_i$  and  $X_i$  as shown in Figure 2. You can choose  $X_i$  to be inductive (assume the resistive loss of the coil to be negligible).
2. Next choose a suitable load resistance  $R_L$  and a variable capacitance  $C_L$  such that the critical value  $C_0$  of  $C_L$ , ( $C_0 = \frac{1}{4\pi^2 f^2 L_i}$ ) falls within the range of the values of  $C_L$ , ~~available (decade box) in steps.~~  
This is to ensure that for a particular frequency, we can obtain the condition:

$$|X_C| = |X_L|, \text{ or } , \frac{1}{\omega C_L} = \omega L_i, \quad (6)$$

for some value of  $C_L$  within the range provided.

Now for different value of  $C_L$  note down  $V_3$  and  $V_1$ ,

$$P_L = I^2 R_L = I \cdot I R_L = \frac{V_1}{100} \cdot V_3 = K \cdot V_1 V_3, \text{ where } K = \frac{1}{100} = \frac{1}{R_i}. \quad (7)$$

Enter the values of the voltage for different 8 values of  $C_L$  and obtain the set corresponding to the maximum value of  $(V_1 V_3)$ . Verify that for this set  $V_2 = V_4$ .

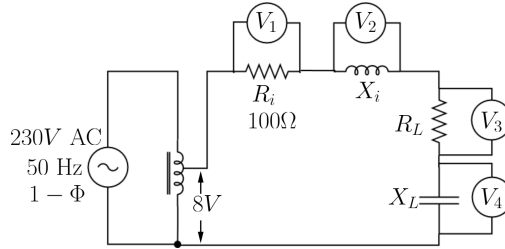


Figure 2: Circuit 2.

Enter the data in the following table:

Sl. No.	$C_L$	$V_1$	$V_3$	$(V_1 \cdot V_3)$	Maximum $(V_1 \cdot V_3)$
1					
2					
3					
4					
5					
6					
7					
8					

Table 1: Experiment observation table.

## 2.2 Second Part

Repeat the procedure of Section 2.1, with  $C_L$  fixed and  $R_L$  varied. At the point of maximum power, check

$$R_L = \sqrt{R_i^2 + (X_i + X_L)^2}. \quad (8)$$

## 2.3 Third Part

Repeat the procedure of Section 2.2, varying both  $R_L$  &  $C_L$  and obtain the maximum power condition. Check under this condition:

$$V_{RL} = V_{Ri} \quad i.e. \quad V_1 = V_3 \quad (9)$$

$$\text{and, } V_{XL} = V_{Xi} \quad i.e. \quad V_2 = V_4. \quad (10)$$

---