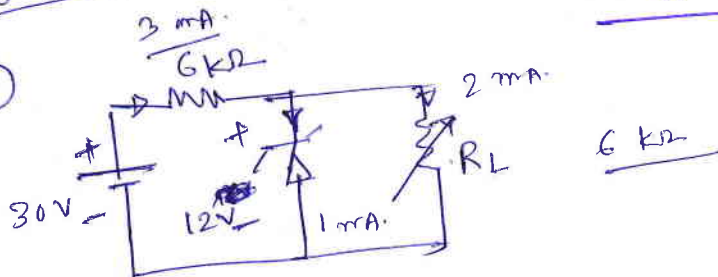


①




Current through $6k\Omega$ resistor $= \frac{30-12}{6k\Omega} = 3mA$.

min. $1mA$ current through Zener, so, $2mA$ current through R_L .
min. value of R_L should be such that drop across it should be at least $12V$.

So, min. value $= 6k\Omega$

Range $5.9k\Omega$ to $6.1k\Omega$

②

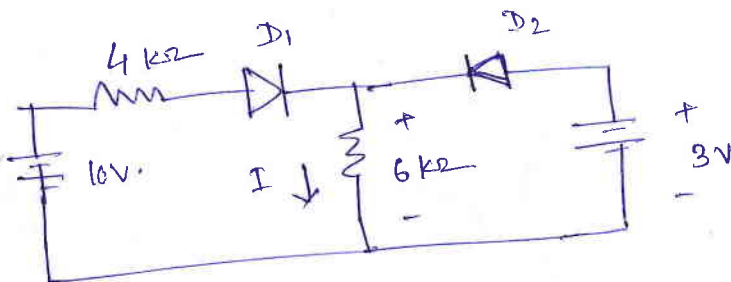

check other possibilities, D_1 & D_2 both ON.

Not possible.

D_2 ON, D_1 OFF

not possible.

Range 0.9 to $1.05mA$

Diodes are ideal

So, $I_s = 0$, (Reverse bias current)

assume D_1 is ON, D_2 is OFF

$I = 1mA$

Drop across $6k\Omega = 6V$.


D_2 reverse bias, as assumed.

Some of you have considered

$V_f = 0.7V$

$0.93mA$

③

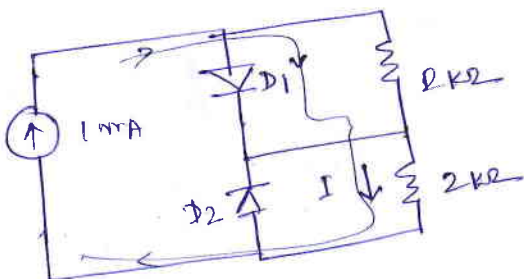

D_1 forward bias, current through $D_1 = 1mA$, voltage drop $= 0$ as $id = 0$.


D_2 can't conduct $1mA$ current the current will flow through $2k\Omega$ resistor.

So, $I = 1mA$

Range 0.95 to $1.05mA$

④

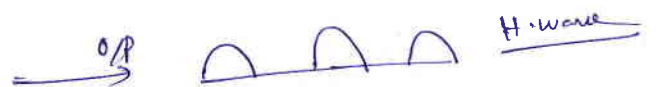$200 \sin 300t V$ i.e. $V_m \sin \omega t$



Average value $= \frac{V_m}{\pi} = \frac{200}{3.14} = 63.69V$

Range $61V$ to $65V$

Set-A

SET-A PAGE-2

⑤ $f = 60 \text{ Hz.}$

$R_L = 10 \text{ k}\Omega$

$V_r = 0.2 \text{ V.}$

$$V_r = \frac{V_m}{2fRC} \quad ; \quad C = \frac{V_m}{2fR V_r} = \frac{10}{2 \times 60 \times 10 \times 10^3 \times 0.2}$$

$= 41.6 \text{ MF.}$


Range 40 MF to 43 MF

⑥ Every 10°C rise in temp., I_s doubles.

$$\frac{I_s'}{I_s} = 2^{\frac{\Delta T}{10}} = 100, \quad \text{find } \Delta T, \quad \Delta T = 66.67^\circ\text{C.}$$

Range $65 - 68^\circ\text{C}$

⑦

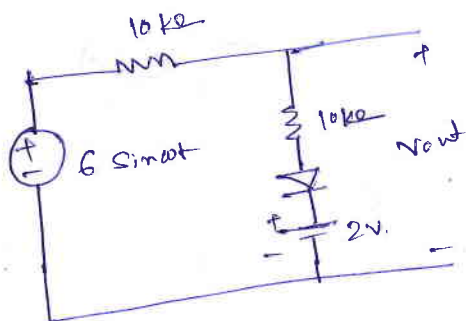

Diode is ON, for positive half-cycle of input.

max. input = 6V, $I = 0.2 \text{ mA.}$


$$\text{Current} = \frac{(6 - 2\text{V})}{(10 + 10)\text{k}} = 0.2 \text{ mA}$$

$$\text{max. } V_{out} = 10 \text{ k}\Omega \times 0.2 \text{ mA} + 2 \text{ V.}$$

$= 4 \text{ V.}$

Range 3.5V to 4.5V

⑧

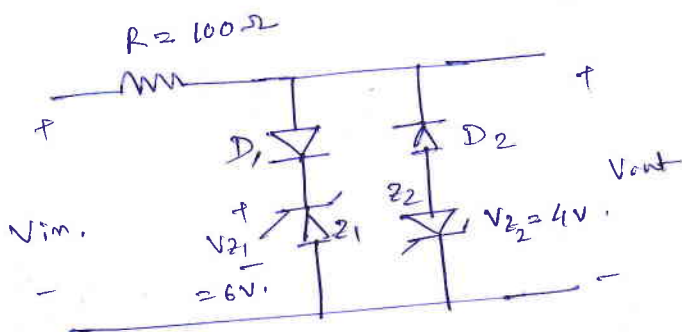

$V_m = 5 \text{ V.}$

D_1 ON, D_2 OFF

Z_1 is not in break down

$\therefore V_{out} = V_m = 5 \text{ V.}$

Range 4.8 V to 5.2 V

⑨

F.W. bias $V_m = 0.15 \text{ V.}$

$$I_F = I_s \exp\left(\frac{0.15}{0.026}\right); m=1$$

Reverse bias

$I_R = -I_s$

$$\frac{I_F}{I_R} = \frac{I_s \exp\left(\frac{0.15}{0.026}\right)}{-I_s} = -320.29,$$

Range

310 to 330

both '+' and '-'

Set - A

Set - A Page - 3

(10)

Conductivity (σ) = $nq\mu$

Resistivity (ρ) = $\frac{1}{\sigma} = \frac{1}{nq\mu}$

$$= \frac{1}{2.3 \times 10^{15} \times 1.6 \times 10^{-19} \times 1350}$$

$\approx 2 \text{ cm}$

1.9 to 2.1 cm range.

(11)

Voltage applied = 5V.

Distance = 2 cm.

Field = $\frac{5}{2} = 2.5 \text{ V/cm}$.

(E)

$n = 10^{16} \text{ cm}^{-3}$


$\mu_n = 2500 \text{ cm}^2/\text{V-s}$.

$J_n = nq\mu_n E$

$= 10^{16} \times 1.6 \times 10^{-19} \times 2500 \times 2.5$

Range 9 A/cm^2 to 11 A/cm^2 $= 10 \text{ A/cm}^2$

(12)

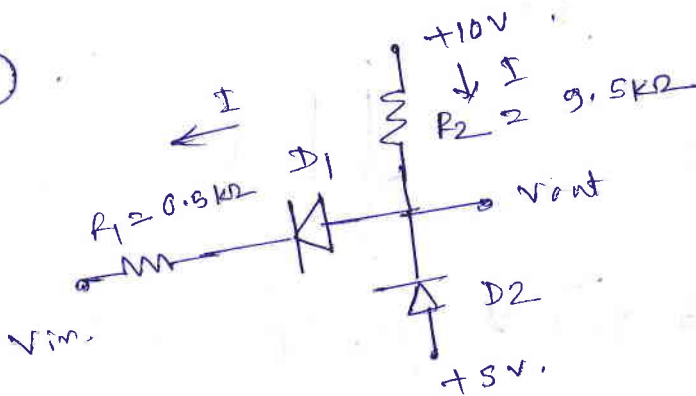

When, $V_{in} = 10 \text{ V}$.
 D_2 is OFF

$V_{out} = 10 - 9.5 \times I$

$10 = 9.5I - 0.6 - 0.5I - V_{in} = 0$

$\therefore I = \frac{9.4 - V_{in}}{10}$


$V_{out} = 10 - 9.5 \times \frac{9.4 - V_{in}}{10}$

for $V_{in} \geq 9.4 \text{ V}$.

$V_{out} = 10 \text{ V}$.

Range 9.4 V to 10.5 V .

13

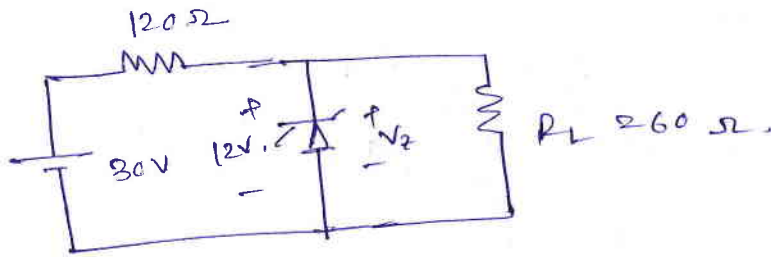

Voltage drop across $R_L = 10V$, $< V_Z$, Zener is not on.

No current through Zener.

Power dissipation across Zener

$= 0$

Power dissipation is "Zero"

$$\frac{V_m \sin \omega t}{10 \sin 87.74^\circ V}$$


14

Voltage at transformer secondary

Full wave rectifier, $V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{10}{\sqrt{2}} = 7.07 V$

Range 6.95V to 7.2V

15

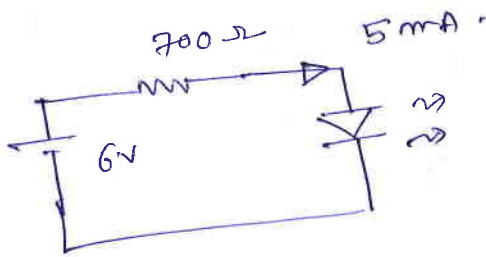

Voltage drop across LED

$= 6V - 5mA \times 700\Omega$

$= 2.5V$

Power dissipation $= 2.5V \times 5mA$

$= 12.5mW$

Cut-in voltage = 1V

~~Voltage drop across LED $= 6 - 700 \times 5$~~

~~$= 6 - 0.7 \times 5$~~

~~$= 2.5V$~~

~~$= 2.5V \times 5mA$~~

~~$= 12.5mW$~~

Range




12 to 13mW

Range (31-32)

Set-B

① Avg. value $= \frac{V_m}{\pi} = \frac{100}{3.14} = 31.84 \text{ V.}$ (B-4 in Set-A)

②

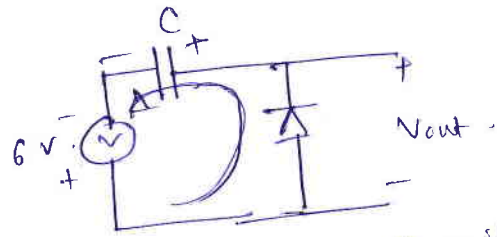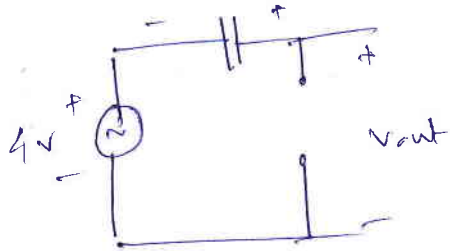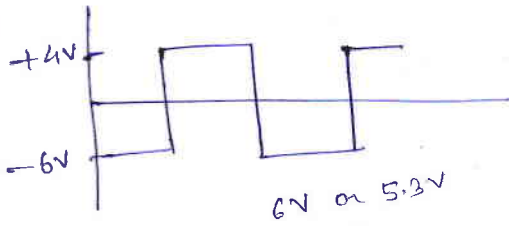

During (+) half., Capacitor charged with 6 V or 5.3 V. (Considering $V_f = 0.7 \text{ V}$)

$V_{out} (\text{max}) = 10 \text{ V or } 9.3 \text{ V.}$
Range (9 to 10 V.)

③ (B-5 in Set-A)

$C_r = \frac{V_m}{2fR V_f} = \frac{10 \text{ V}}{2 \times 50 \times 10^3 \times 0.3}$
 $= 33.36 \text{ } \mu\text{F.}$

Range (31 - 35) μF

④

$N_D = 10^{15} \text{ cm}^{-3}$

$n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$


additional doping $N_A = 1 \times 10^{18} \text{ cm}^{-3} \gg N_D$

$P = 1 \times 10^{18} \text{ cm}^{-3}$

$m = \frac{n_i^2}{P} = \frac{2.25 \times 10^{20}}{1 \times 10^{18}} = 2.25 \times 10^2 = 225 \text{ cm}^{-3}$

Range (220 to 230)

⑤

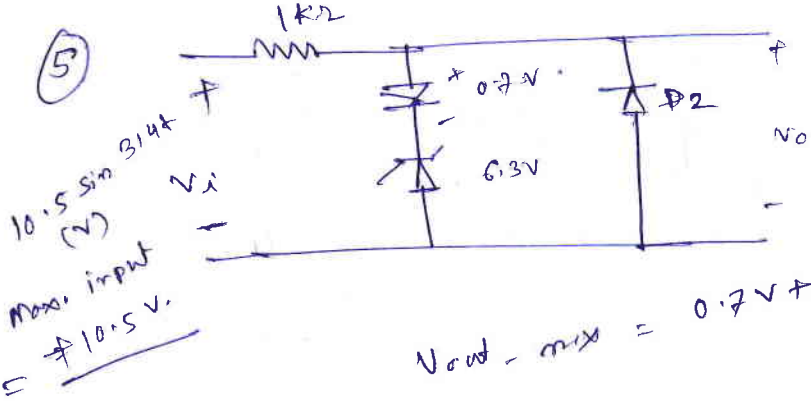

$10.5 \sin 314t$
(V)
Max. input
 $= \pm 10.5 \text{ V.}$

$V_{out} - \text{max} = 0.7 \text{ V} + 6.3 \text{ V} = 7 \text{ V.}$
Range (6.5 to 7.5 V.)

Range (0.9 to 1.1 mA)

⑥

1 mA
(B-3 in Set-A)

(B-6 in Set-A)

$$\frac{I_{s'}}{I_s} = 2^{\Delta T/10} = 200$$

$$\frac{\Delta T}{10} \log 2 = 2.30$$

$$\Delta T = \frac{2.30 \times 10}{\log 2}$$

$$\Delta T = 76.40$$

range (75 to 78)

(8) $I = 1 \text{ mA.}$

(B-2 in set-A)



range (0.9 to 1.1)

(9) $V_{out} = 5.5 \text{ V.}$

(B-8 in set A)

(~~5.2 to 6.8~~) (5.2 to 5.8)

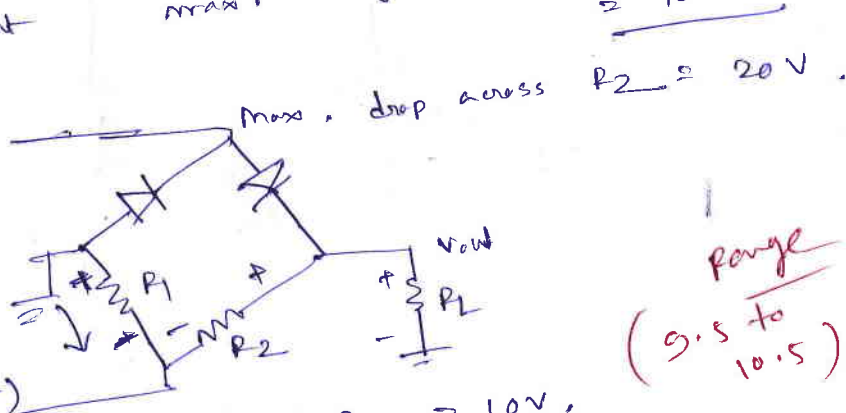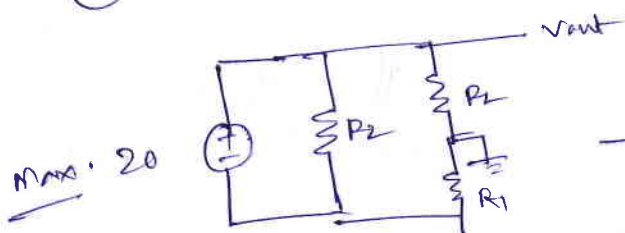
(10) the circuit can be redrawn as (in forward bias)
max. voltage drop across $R_2 = R_1$
 $= 10 \text{ V.}$



PIV = drop across R_2 - drop across $R_1 = 10 \text{ V.}$

range (9.5 to 10.5)

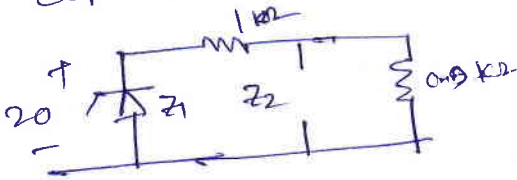(11) Remove Zener diodes, find current $= \frac{35}{0.5 + 1 + 0.9} = 14.58 \text{ mA.}$
drop across $(1\text{K} + 900\Omega)$ is more than 20 V. , 20 V zener is in breakdown.



drop across $0.9 \text{ K}\Omega$ resistor
 $= 9.47 < 10 \text{ V.}$

Ans. 9.47 V.

Z_2 is not in breakdown

(9.2 to 9.8) V

(12) $D_p = 15 \text{ cm}^2/\text{s.}$

$$\frac{D_m}{D_p} = \frac{D_p}{M_p} = \frac{V_T}{M_p} = 0.0259 \text{ V.}$$

$$M_p = \frac{D_p}{0.0259} = \frac{15}{0.0259} = 579.15 \text{ cm}^2/\text{V-s.}$$

(560 to 590) range

Set-B

SET-B

PAGE-7

(13)


D_1 and D_2 is in parallel, so, D_2 will turn on as $V_f = 0.3V$.

$$I_R = \frac{10 - 0.3}{330\Omega} A$$

$$= 29.39 \text{ mA}$$

Range 29 to 30

(14)

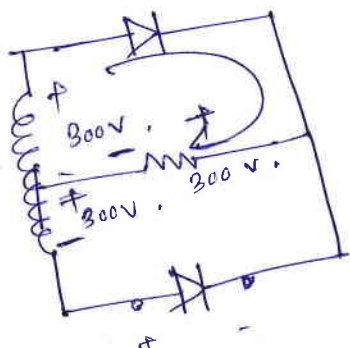

$$PIV = 2V_s - V_f = 600V - 0.3V = 599.3V$$

Range (599 to 600V)

(15)

$$10 \sin(377t) \text{ in } V$$

$$V_m \sin \omega t$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{10}{\sqrt{2}} = 7.07 V$$

Range (7.0 to 7.15)

$$= 3t$$

Set-C

SET-C

PAGE-8

① $N_D = 10^{15} \text{ cm}^{-3}$, $n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$

additional doping $N_A = 2 \times 10^{18} \text{ cm}^{-3}$. $\gg N_D$ and n_i

so, $P = 2 \times 10^{18} \text{ cm}^{-3}$.

$$n = \frac{n_i^2}{P} = \frac{2.25 \times 10^{20}}{2 \times 10^{18}} = 1.125 \times 10^2 = 112.5 \text{ cm}^{-3}$$

Range 105 - 125 cm⁻³

② Drop across $R_L = \frac{60}{60+120} \times 30 = 10 \text{ V}$.

$V_Z = 11 \text{ V}$.

so, Zener is not in breakdown.

↓
no current through Zener.

power dissipation = 0

③ $N_A = 12.5 \text{ Sim wt}$
↓
 $V_{im} = 12.5 \text{ V}$.

$V_F = 0.6 \text{ V}$, $V_Z = 6.3 \text{ V}$.


Max. voltage drop = ~~9.3~~ $6.3 + 0.6 = 6.9 \text{ V}$.

Range (6.5 to 7.5 V)

④ Same as B-7 ~~Set-A~~

Ans 4V

Range 3.5 V to 4.5 V.

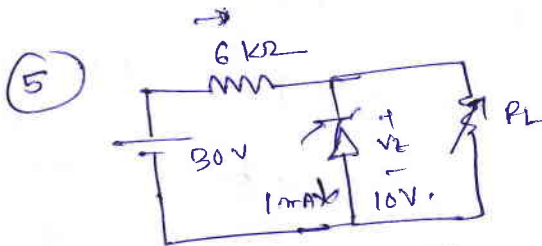

Current through $6 \text{ k}\Omega = \frac{30-10}{6 \text{ k}\Omega} = 3.33 \text{ mA}$

Current " $R_L = (3.33 - 1) = 2.33 \text{ mA}$,

Min. value of R_L should be such that $2.33 \times R_L = 10 \text{ V}$,
 $R_L = 4.29 \text{ k}\Omega$

Range 4.1 to 4.45 kΩ

⑥ Only Ge diode is on.

$$I_R = \frac{10 - 0.35}{330 \Omega} = 29.24 \text{ mA}$$

Range 29 to 30 mA


⑦ $\mu_m = 1500 \text{ cm}^2/\text{V-s}$ Set A - e Power - 9
 $E = 5/2 = 2.5 \text{ V/cm}$ $n = 10^{16} \text{ cm}^{-3}$
 $J = nq\mu_mE$
 $= 10^{16} \times 1.6 \times 10^{19} \times 1500 \times 2.5$
 $= 6 \text{ A/cm}^2$
Range 5 - 7 A/cm²

⑧ $\frac{I_{\text{forward}}}{I_{\text{reverse}}} = \frac{1}{1} \exp\left(\frac{0.2}{0.026}\right)$
 $= 2191$
Range 2100 - 2800

⑨ $V_{\text{out}} = 10 \text{ V}$ (B-12, plz see Set-A)
Range 9.5 to 10.5 V.

⑩ $V_{\text{in}} = V_m \sin \omega t$ $V_m = 30 \text{ V}$ (max. input voltage)
 $\text{PIV} = 15 \text{ V}$ (for details pls. see B-10 Set-B)
Range 14.5 V to 15.5 V.

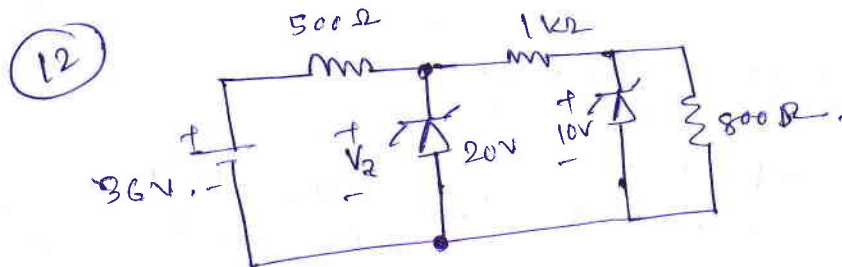⑪ $\mu_m = 1250 \text{ cm}^2/\text{V-s}$ $N_D = n = 4.3 \times 10^{15} \text{ cm}^{-3}$
 $\rho = \frac{1}{\sigma} = \frac{1}{nq\mu_m} = \frac{1}{4.3 \times 10^{15} \times 1.6 \times 10^{19} \times 1250} = 1.16 \text{ } \Omega\text{-cm}$
Range 1 to 1.3 } \Omega\text{-cm}



Remove all Zener diodes
 Find current $= \frac{36}{0.5 + 1 + 0.8}$
 $= 15.65 \text{ mA}$
 drop across $(1 + 0.8) \text{ k}\Omega$

$= 28 \text{ V} > 20 \text{ V}$

20 V Zener is in breakdown

So, current through $800 \Omega = 11.1 \text{ mA}$

drop across $= 11.1 \times 0.8 = 8.88 \text{ V}$ 10V Zener not in breakdown

Range 8.3 V. to 9.3 V.

13

14

please see Q-2, Set-A

Ans 1 mA

range 0.9 to 1.05 mA

15

LED cut-in voltage = 1 V.
 Current through LED = 5 mA.

$$\text{Voltage drop across LED} = 6V - \overset{\text{K}\Omega}{0.7} \times 5 \text{ mA} \\ = 6 - 3.5 = \underline{2.5 \text{ V}}$$

$$\text{Power dissipation} = 2.5 \text{ V} \times 5 \text{ mA} = \underline{12.5 \text{ mW}}$$

range 12 to 13 mW

$$V_b = \frac{V_m}{\sqrt{2}} = 1.91$$

$$I_k = I_s \left(e^{\frac{K V_b}{T}} - 1 \right)$$