



(b)  $f(a, b, c, d, e) = \sum_m(0, 4, 6, 7, 8, 12, 14, 16, 18, 19, 20, 24, 26, 28)$  [on-set] +  $\sum_D(2, 3, 10, 15, 22, 23, 27, 30)$  [don't care set] for 2-level realisation using XOR and AND gates (negated literals permitted).

A 4x8 grid representing a truth table for a 4-bit function  $f$ . The columns are labeled with 3-bit inputs  $c, d, e$  (000 to 100) and the rows are labeled with 2-bit inputs  $a, b$  (00 to 10). The grid is currently empty.

[illegible]