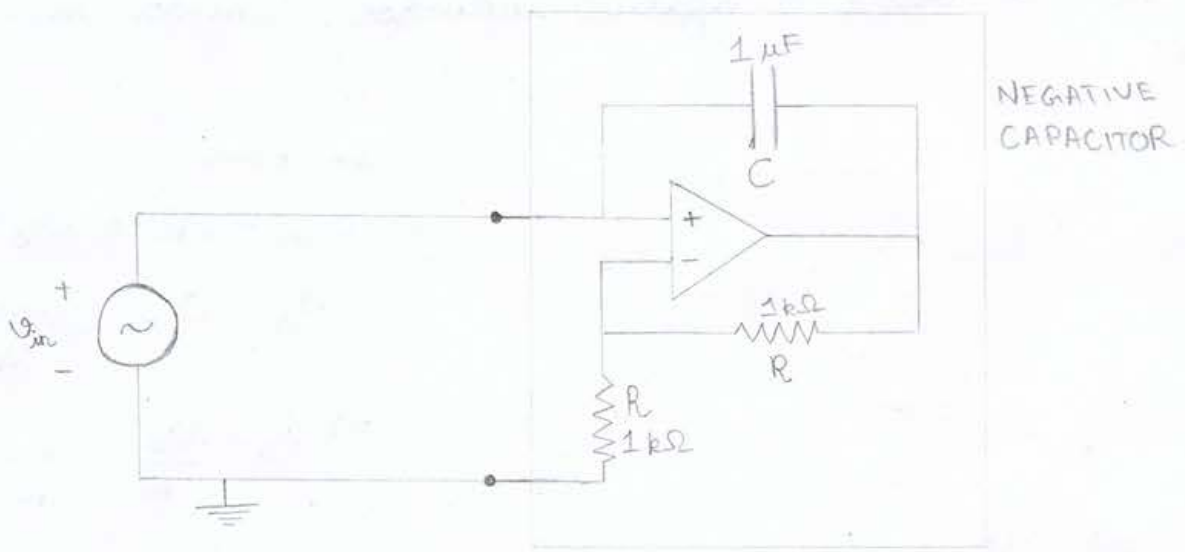


EXPERIMENT 5

① NEGATIVE IMPEDANCE CONVERTOR

OBSERVATION TABLE ($C = 1 \mu F$)

| Frequency (Hz) | Applied voltage magnitude (V) | Current magnitude (A) | Phase of current w.r.t the voltage (degrees) | Calculated complex impedance (Ω) |
|-------------------|-------------------------------------|-----------------------------|--|---|
| 100 | 5 | 3.14×10^{-3} | -90 | 1592.36j |
| 200 | 5 | 6.28×10^{-3} | -90 | 796.18j |
| 300 | 5 | 9.42×10^{-3} | -90 | 530.79j |
| 400 | 5 | 1.26×10^{-2} | -90 | 396.83j |
| 500 | 5 | 1.57×10^{-2} | -90 | 318.47j |
| 1000 | 5 | 3.14×10^{-2} | -90 | 159.24j |
| 2000 | 5 | 6.28×10^{-2} | -90 | 79.62j |
| 3500 | 5 | 1.10×10^{-1} | -90 | 45.45j |
| 5000 | 5 | 1.57×10^{-1} | -90 | 31.85j |
| 6500 | 5 | 2.04×10^{-1} | -90 | 24.51j |
| 8000 | 5 | 2.51×10^{-1} | -90 | 19.92j |
| 10000 | 5 | 3.14×10^{-1} | -90 | 15.92j |


Nisarg

VARIAION OF IMPEDANCE (MAGNITUDE) WITH FREQUENCY

SCALE

x-axis: 1 unit = 0.5 kHz

y-axis: 1 unit = 100 Ω

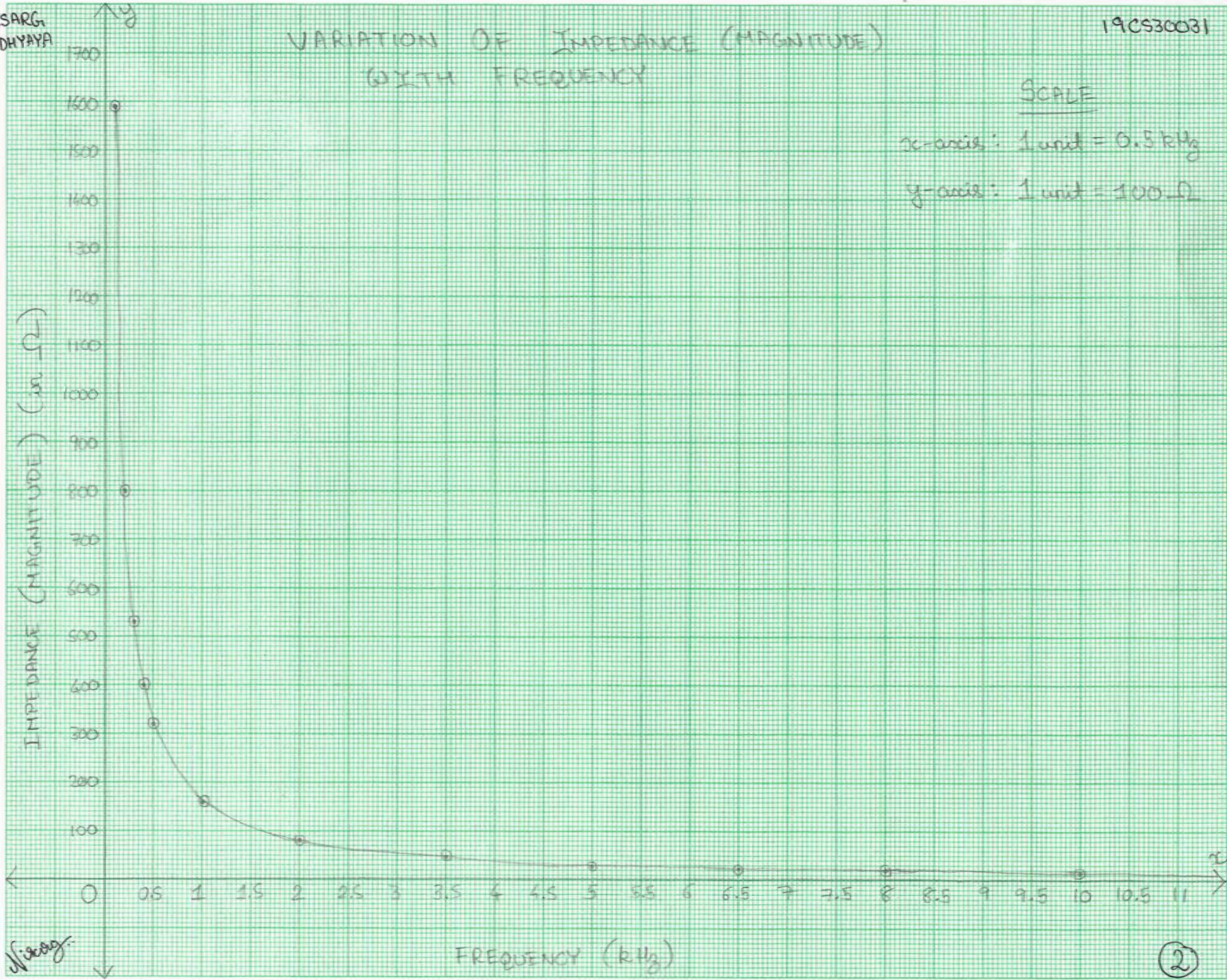

Wing.


VARIAION OF IMPEDANCE (ANGLE) WITH FREQUENCY

19CG930031

SCALE

x-axis : 1 unit = 0.5 kHz


y-axis : 1 unit = 10°

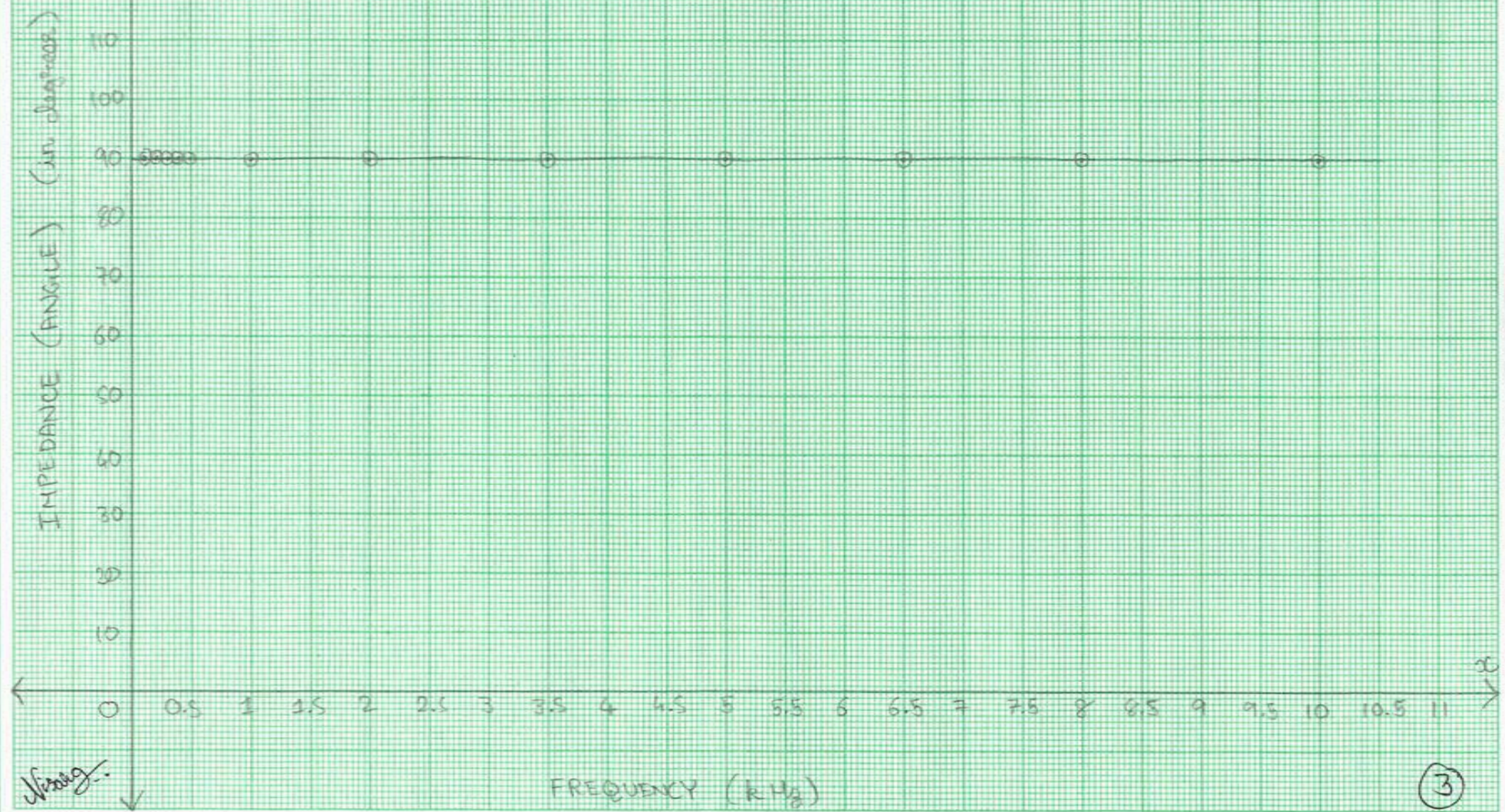

Wavy

It is indeed possible to create an inductor using a capacitor using this negative impedance converter with some slight modifications.

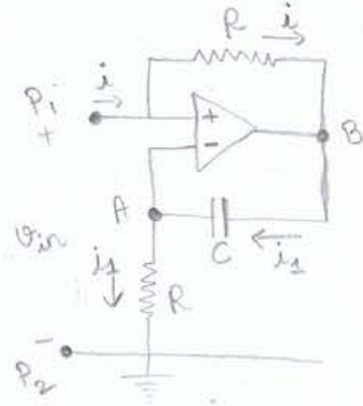First, we will create a negative inductor. Consider the following circuit:



We have

$$\Rightarrow V_{in} - iR = V_B$$

$$\Rightarrow V_A = V_{in} \text{ (virtual short)}$$

$$\Rightarrow i_1 = \frac{V_A}{R} = \frac{V_{in}}{R}$$


$$\Rightarrow V_A + \frac{i_1}{Cs} = V_B$$

$$\Rightarrow V_{in} + \frac{V_{in}}{RCs} = V_{in} - iR$$


$$\Rightarrow \frac{V_{in}}{i} = Z_{in} = \underline{\underline{-R^2Cs}}$$

If we take $R^2C = L$ then $Z_{in} = -Ls$ which is nothing but a negative inductor.

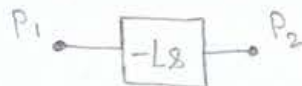We can assume the above to be a two terminal network



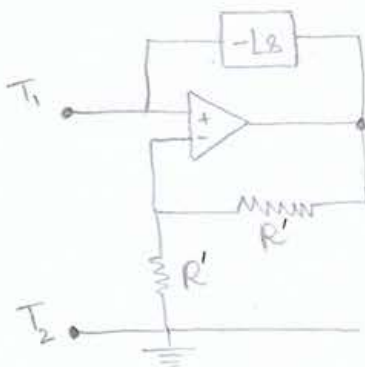
Now using our initial negative impedance converter we can change this to a positive inductor.




Now, the following network between T_1 & T_2 behaves as a positive inductor with inductance

$$\underline{\underline{L = R^2C}}$$

② GYRATOR

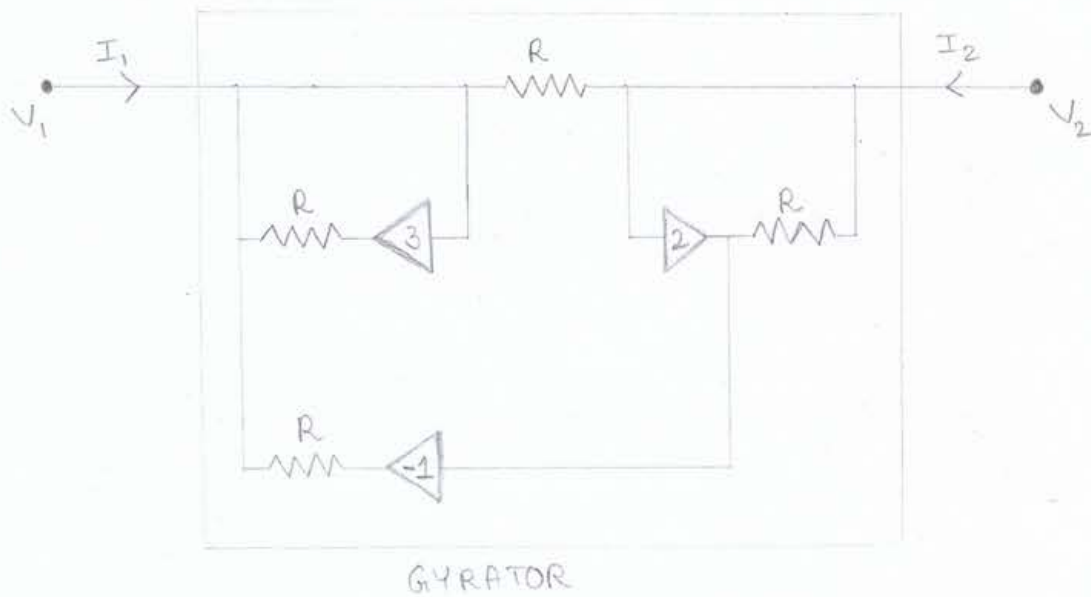

SIMULATING INDUCTOR USING A CAPACITOR

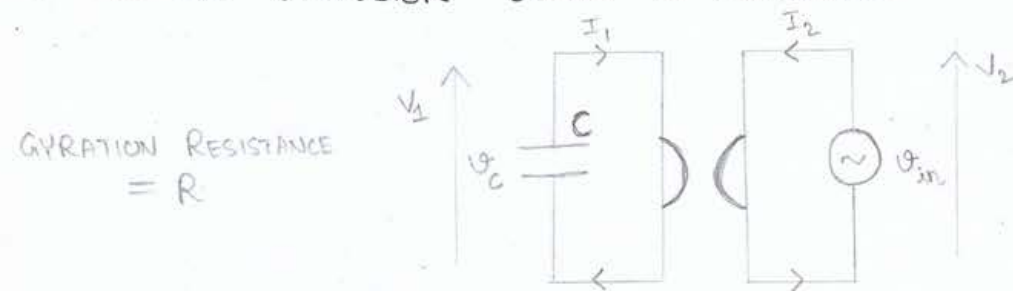

For a gyrator we can write $V_2 = RI_1$ and $V_1 = -RI_2$

Now $V_2 = V_{in}$ and $V_1 = V_C = \frac{-I_1}{Cs}$

Hence $V_1 = -RI_2 = \frac{-I_1}{Cs} \Rightarrow I_1 = RCs I_2$

$\Rightarrow V_2 = V_{in} = RI_1 = R^2 Cs I_2$

$\Rightarrow Z_{in} = \frac{V_{in}}{I_2} = R^2 Cs$

If we take $R^2 C = L$ then Z_{in} can be treated as an inductor, whose inductance $L = R^2 C$.

OBSERVATION TABLE ($C = 1\mu F$, $R = 1k\Omega$)

| Frequency (Hz) | Applied voltage magnitude (V) | Current magnitude (A) | Phase of current w.r.t the voltage (degrees) | Calculated complex impedance (Ω) |
|-------------------|-------------------------------------|-----------------------------|--|---|
| 100 | 5 | 7.96×10^{-3} | -90 | 628.14j |
| 500 | 5 | 1.59×10^{-3} | -90 | 3144.65j |
| 1000 | 5 | 7.96×10^{-4} | -90 | 6281.41j |
| 2000 | 5 | 3.98×10^{-4} | -90 | 12562.81j |
| 3000 | 5 | 2.65×10^{-4} | -90 | 18867.92j |
| 4000 | 5 | 1.99×10^{-4} | -90 | 25125.63j |
| 5000 | 5 | 1.59×10^{-4} | -90 | 31446.54j |
| 6000 | 5 | 1.33×10^{-4} | -90 | 37593.98j |
| 7000 | 5 | 1.14×10^{-4} | -90 | 43859.65j |
| 8000 | 5 | 9.95×10^{-5} | -90 | 50251.26j |
| 9000 | 5 | 8.84×10^{-5} | -90 | 56561.09j |
| 10000 | 5 | 7.96×10^{-5} | -90 | 62814.07j |

Nisarg

VARIATION OF IMPEDANCE (MAGNITUDE) WITH FREQUENCY

19CS30031

IMPEDANCE (MAGNITUDE) (in $k\Omega$)


SCALE

x-axis: 1 unit = $0.5 kHz$

y-axis: 1 unit = $4 k\Omega$

FREQUENCY (kH_z)

Wavy

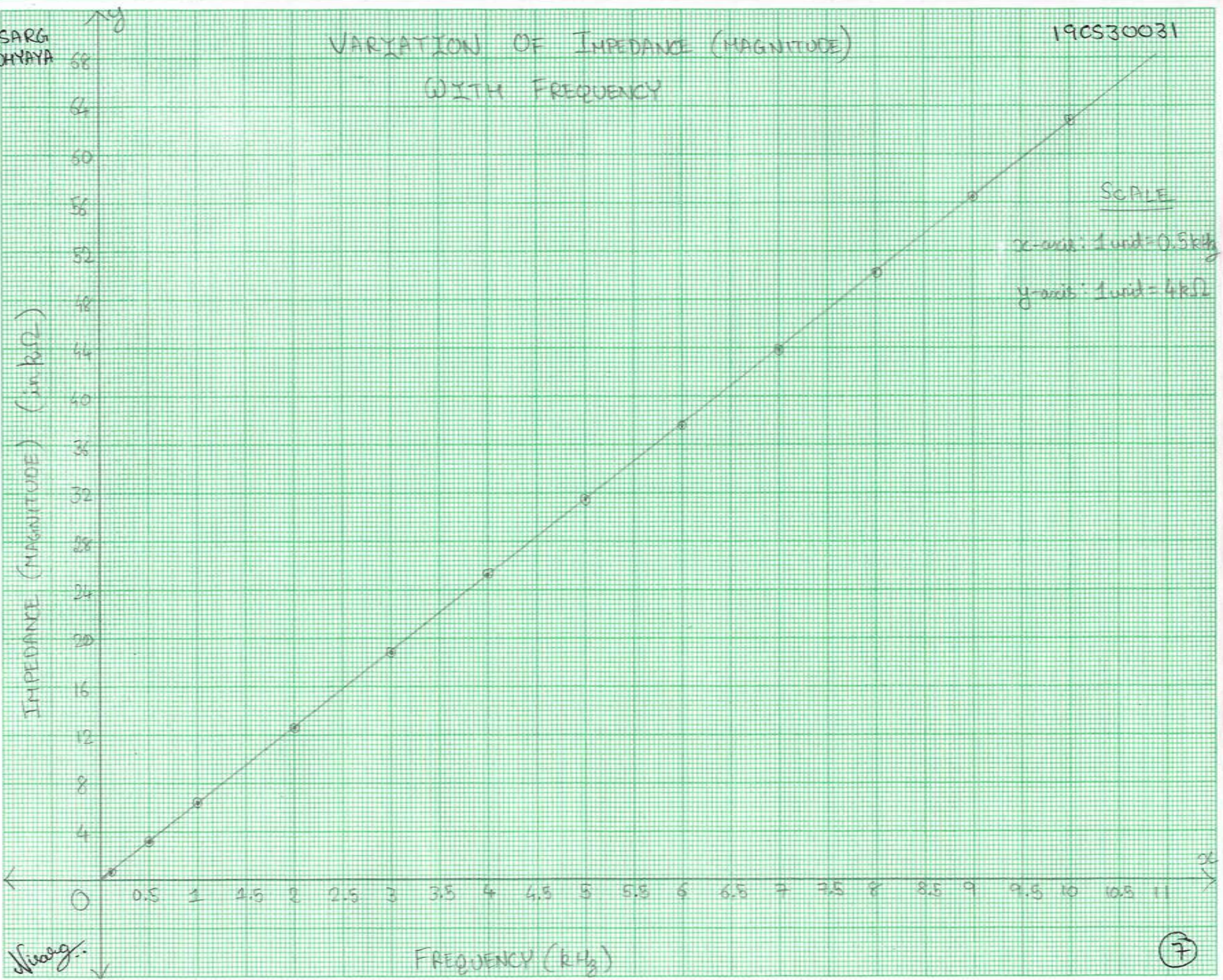


VARIATION OF IMPEDANCE (ANGLE) WITH FREQUENCY

SCALE


x-axis: 1 unit = 0.5 kHz

y-axis: 1 unit = 10°

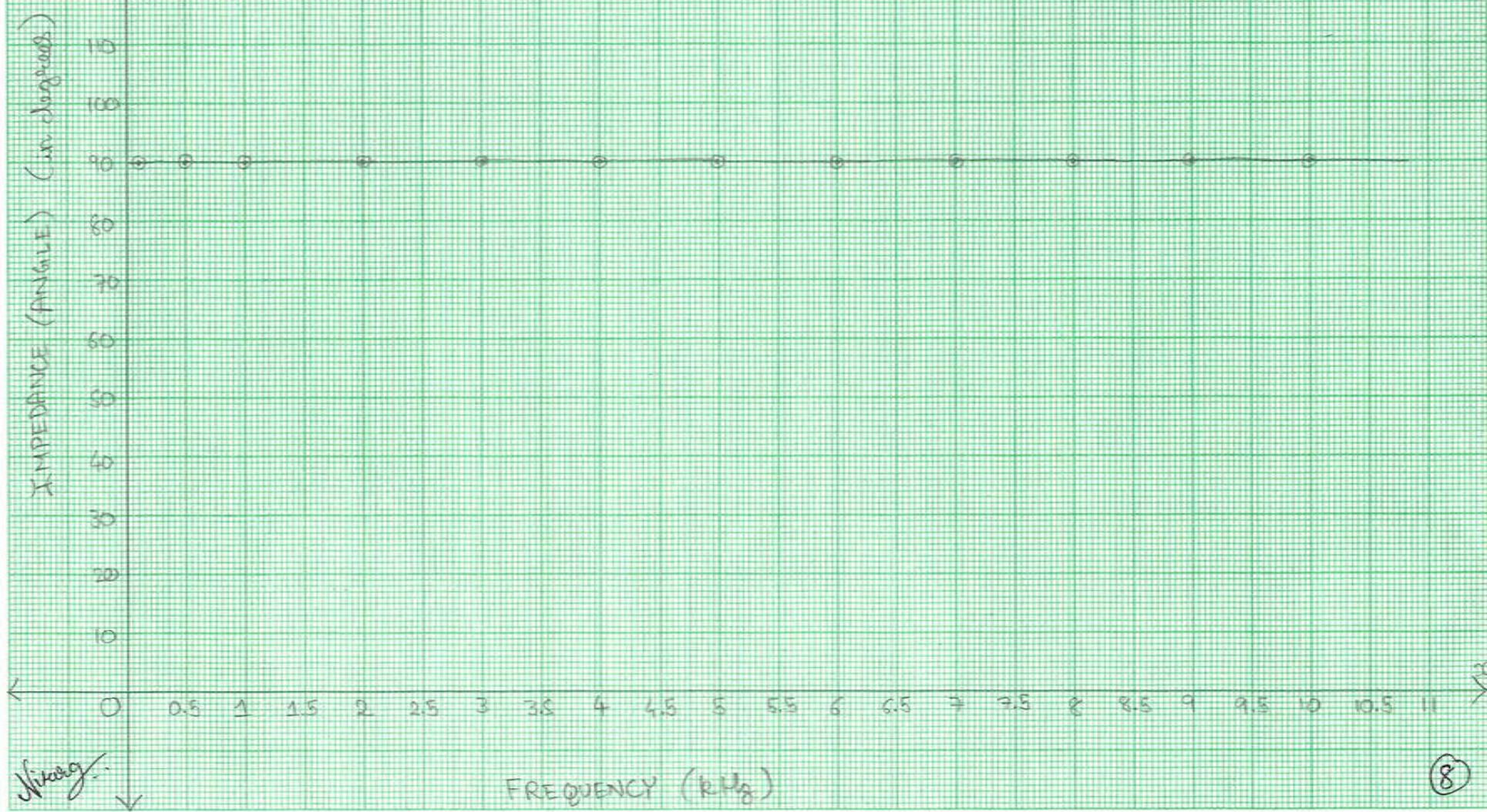

Nisarg

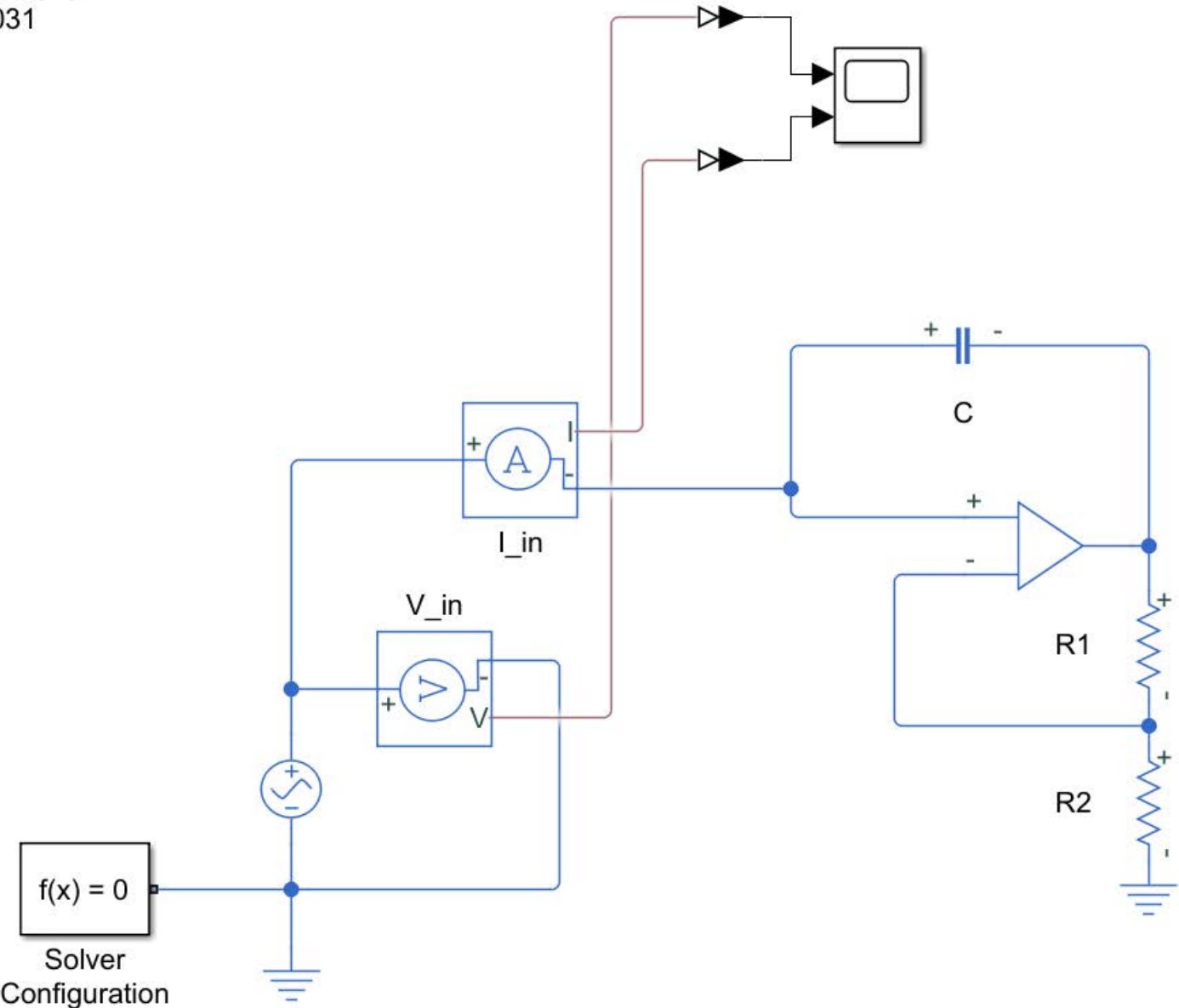Name: Nisarg Upadhyaya
Roll No: 19CS30031



Name: Nisarg Upadhyaya
Roll No: 19CS30031

